

CONTENTS

Chapter 1: SIGNALS AND COMMUNICATIONS	1-1
1.1. Frequency	1-1
1.2. Oscillators	1-3
1.3. Modulation	1-5
1.4. Amplifiers	1-7
1.5. Mixers	1-8
1.6. Filters	1-9
1.7. Receivers	1-11
1.8. TRC-10	1-12
1.9. Bibliography	1-14
1.10. Laboratory exercises	1-14
1.11. Problems	1-15
Chapter 2: CIRCUIT THEORY PRIMER	2-1
2.1. Energy sources	2-1
2.2. Resistors	2-3
2.2.1. Resistive circuits	2-5
2.3. Analysis of electrical circuits	2-5
2.4. Capacitors	2-8
2.4.1. Power and energy in capacitors	2-10
2.4.2. RC circuits	2-11
2.5. Diodes	2-15
2.5.1. Diodes as rectifiers	2-17
2.5.1. Zener diodes as voltage sources	2-19
2.6. Inductors	2-20
2.7. Transformers	2-23
2.8. Circuit protection devices	2-24
2.8.1. Varistors	2-24
2.8.2. PTC Thermistors	2-25
2.8.3. Circuit protection	2-25
2.8. Bibliography	2-26
2.9. Laboratory exercises	2-26
2.10. Problems	2-34
Chapter 3: AUDIO CIRCUITS	3-1
3.1. Linear circuits	3-1
3.1.1. Power	3-4
3.2. Impedance and Transfer Function	3-5
3.3. Sources and Equivalent Circuits	3-10
3.4. Operational amplifiers	3-15
3.5. OPAMP circuits	3-20
3.5.1. Offset voltage in OPAMPs	3-21
3.5.2. OPAMP Linear Voltage Regulator	3-23
3.6. Bibliography	3-26

3.7. Laboratory exercises	3-26
3.8. Problems	3-42
 Chapter 4: TUNED CIRCUITS	 4-1
4.1. Parallel resonance	4-1
4.1.1. Energy in tuned circuits	4-2
4.1.2. Quality of resonance	4-4
4.2. Series tuned circuits	4-8
4.3. Equivalence of series and parallel RLC circuits	4-10
4.4. Real inductors	4-12
4.4.1. Air core inductors	4-14
4.4.2. Powdered iron core inductors	4-14
4.4.3. Core losses	4-15
4.4.4. Copper losses	4-16
4.4.5. RF choke inductors	4-17
4.5. RF Amplification using OPAMPs	4-19
4.5.1. OPAMP Open Loop Frequency Response	4-19
4.5.2. Voltage gain and power gain	4-22
4.5.3. Slew Rate	4-22
4.5.4. Input Bias Current	4-23
4.6. Maximum power transfer	4-23
4.7. Bibliography	4-25
4.8. Laboratory exercises	4-25
4.9. Problems	4-34
 Chapter 5: FILTERS	 5-1
5.1. Motivation	5-1
5.2. Polynomial filters	5-3
5.2.1. Butterworth filters	5-3
5.2.2. Harmonic filter	5-6
5.2.3. Butterworth HPF	5-8
5.2.4. Butterworth BPF	5-9
5.3. Impedance matching	5-11
5.3.1. Transformers	5-11
5.3.2. Real transformers	5-12
5.3.3. Matching by resonant circuits	5-15
5.3.4. Impedance inverters	5-15
5.4. Crystal filters	5-16
5.4.1. Quartz crystals	5-17
5.4.2. IF ladder filter	5-18
5.5. Bibliography	5-21
5.6. Laboratory exercises	5-21
5.7. Problems	5-31
 Chapter 6: DIODES IN TELECOMMUNICATIONS	 6-1
6.1. Diode detector	6-1
6.1.1. Real diodes in envelope detectors	6-3

6.2. TX/RX switch	6-5
6.2.1. Diode biasing	6-6
6.2.2. PIN diode switch	6-8
6.2.3. RF gain control	6-11
6.3. Audio gain control	6-12
6.4. Bibliography	6-13
6.5. Laboratory exercises	6-14
6.6. Problems	6-19

Chapter 7: FREQUENCY CONVERSION 7-1

7.1. Amplitude modulators	7-1
7.1. Mixers in telecommunication circuits	7-2
7.1.1. Switch mixer	7-2
7.1.2. Double-balanced mixers	7-4
7.2. Analog multipliers	7-5
7.2.1. Conversion gain	7-7
7.3. Oscillators	7-7
7.3.1. Oscillator concept	7-8
7.3.2. Frequency control	7-10
7.4.3. Phase considerations in oscillators	7-11
7.4. Bibliography	7-12
7.5. Laboratory exercises	7-12
7.6. Problems	7-23

Chapter 8: ON THE AIR 8-1

8.1. Antenna concept	8-1
8.1.1. Radiation from an antenna	8-1
8.1.2. Receiving antenna	8-6
8.2. Antenna impedance	8-6
8.2.1. Self impedance	8-7
8.2.2. Mutual impedance	8-7
8.3. Half wave dipole	8-8
8.4. Monopole antenna	8-8
8.5. Antenna feeders	8-10
8.5.1. Balanced-unbalanced transformation	8-11
8.5.2. TRC-10 short dipole feeder	8-12
8.6. Using amateur frequency bands	8-14
8.7. Bibliography	8-14
8.8. Laboratory exercises	8-14
8.9. Problems	8-16

Appendix A: Circuit diagrams and PCB layout

Appendix B: List of components

Appendix C: Data sheets

Appendix D: Complex numbers