

series with
nt source in
lent circuits

circuits can be
cuit voltage
and (3) the
ned off.

uits can also
y solving for
nt analysis.

urface signal
 $v_x = v_{OC} i_{SC}/4$
matched.

the voltage,
ints depend
ers that are
ort interface
o solutions.

the circuit in

+
 v_x
-

the circuit in

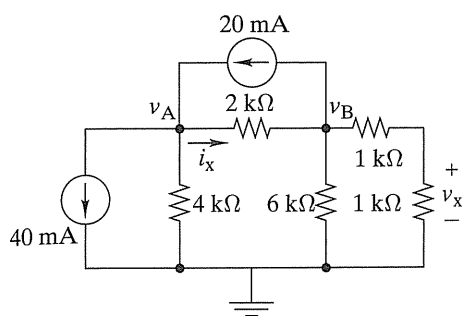


FIGURE P3-3

- 3-4 (a) Formulate node-voltage equations for the circuit in Figure P3-4.
(b) Use these equations to find v_x and i_x .

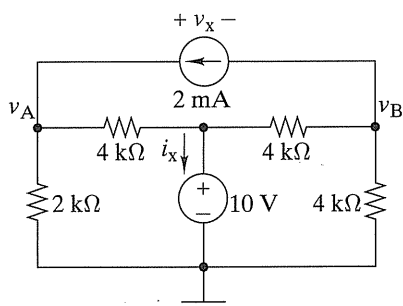


FIGURE P3-4

- 3-5 (a) Formulate node-voltage equations for the circuit in Figure P3-5.
(b) Solve for v_x and i_x when $R_1 = R_2 = R_3 = R_4 = 10 \text{ k}\Omega$, $v_s = 20 \text{ V}$, and $i_s = 2 \text{ mA}$.

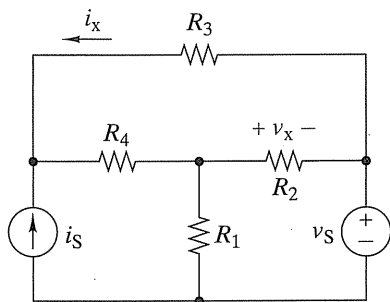


FIGURE P3-5

- 3-6 (a) Formulate node-voltage equations for the circuit in Figure P3-6.
(b) Solve for v_x and i_x when $R_1 = R_2 = R_3 = R_4 = R_5 = 10 \text{ k}\Omega$, and $v_s = 20 \text{ V}$.

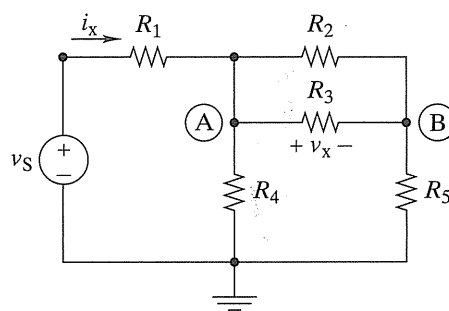


FIGURE P3-6

- 3-7 (a) Formulate node-voltage equations for the circuit in Figure P3-7.
(b) Solve for v_A , v_B , and v_C when $R_1 = 1 \text{ k}\Omega$, $R_2 = 2 \text{ k}\Omega$, $R_3 = 4 \text{ k}\Omega$, $R_4 = 2 \text{ k}\Omega$, and $i_{S1} = i_{S2} = 2 \text{ mA}$.

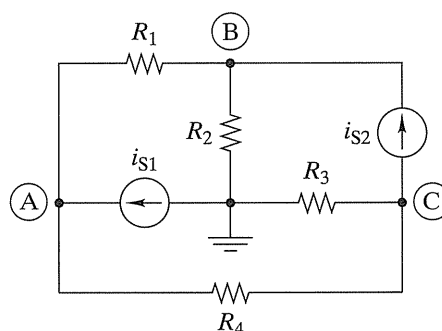


FIGURE P3-7

- 3-8 (a) Formulate node-voltage equations for the circuit in Figure P3-8.
(b) Solve for v_x and i_x when $R_1 = R_4 = 1 \text{ k}\Omega$, $R_2 = R_3 = 250 \Omega$, $R_x = 500 \Omega$, and $v_s = 15 \text{ V}$.

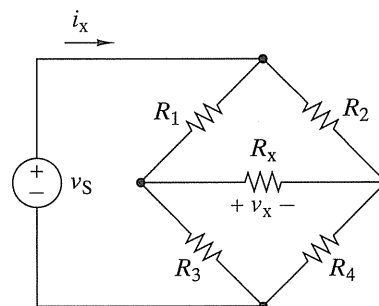


FIGURE P3-8

- 3-9 (a) Formulate mesh-current equations for the circuit in Figure P3-9.
(b) Use these equations to find v_x and i_x .

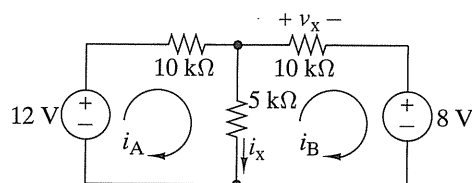


FIGURE P3-9

- 3-10 (a) Formulate mesh-current equations for the circuit in Figure P3-10.

(b) Use these equations to find v_x and i_x .

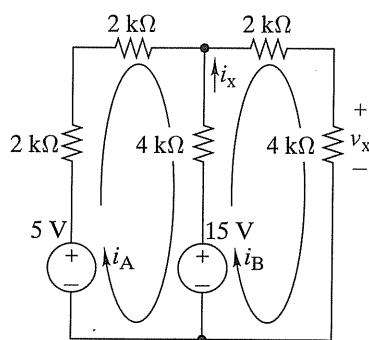


FIGURE P3-10

- 3-11 (a) Formulate mesh-current equations for the circuit in Figure P3-11.

(b) Use these equations to find v_x and i_x .

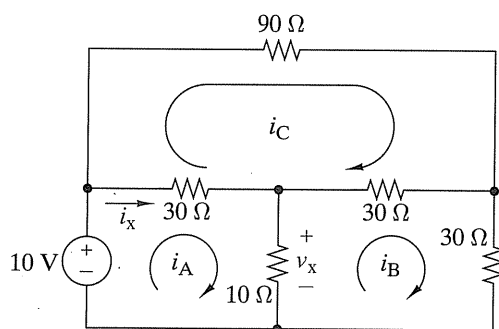


FIGURE P3-11

- 3-12 (a) Formulate mesh-current equations for the circuit in Figure P3-12.

(b) Solve for v_x and i_x when $R_1 = 200 \Omega$, $R_2 = 300 \Omega$, $R_3 = 50 \Omega$, $R_4 = 250 \Omega$, $R_5 = 200 \Omega$, $i_s = 50 \text{ mA}$, and $v_s = 15 \text{ V}$.

(c) Find the total power dissipated in the circuit.

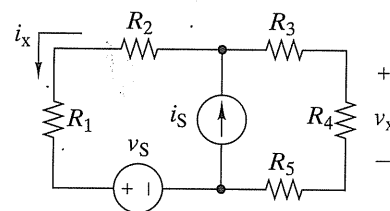


FIGURE P3-12

- 3-13 (a) Formulate mesh-current equations for the circuit in Figure P3-13.

(b) Solve for v_x and i_x when $R_1 = R_2 = 10 \text{ k}\Omega$, $R_3 = 2 \text{ k}\Omega$, $R_4 = 1 \text{ k}\Omega$, $i_s = 2.5 \text{ mA}$, $v_{s1} = 12 \text{ V}$, and $v_{s2} = 0.5 \text{ V}$.

(c) Find the power supplied by v_{s1} .

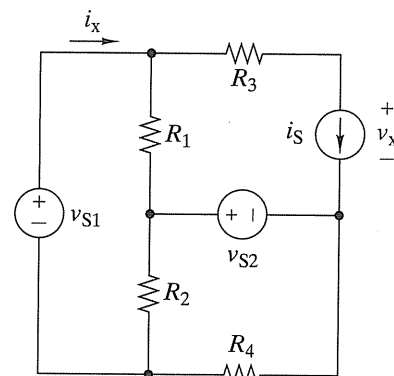


FIGURE P3-13

- 3-14 The circuit in Figure P3-14 seems to require two supermeshes since both current sources appear in two meshes. However, sometimes rearranging the circuit diagram will eliminate the need for a supermesh.

(a) Show that supermeshes can be avoided in Figure P3-14 by rearranging the connection of resistor R_6 .

(b) Formulate mesh-current equations for the modified circuit as redrawn in part (a).

(c) Solve for v_x when $R_1 = R_2 = R_3 = R_4 = 2 \text{ k}\Omega$, $R_5 = 1 \text{ k}\Omega$, $i_{s1} = 40 \text{ mA}$, and $i_{s2} = 20 \text{ mA}$.

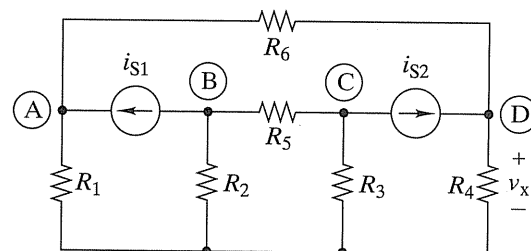


FIGURE P3-14

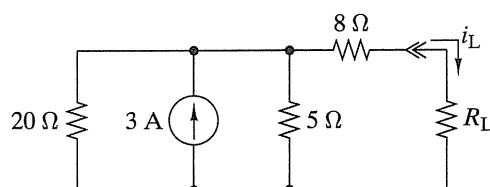


FIGURE P3-38

- 3-39 Find the Thévenin equivalent seen by R_L in Figure P3-39. Find the power delivered to the load when $R_L = 50 \text{ k}\Omega$ and $200 \text{ k}\Omega$.

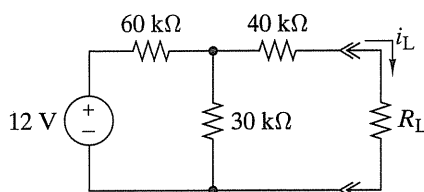


FIGURE P3-39

- 3-40 Find the Norton equivalent at terminals A and B in Figure P3-40.

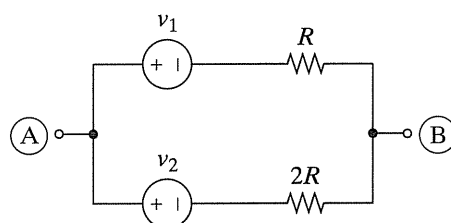


FIGURE P3-40

- 3-41 The purpose of this problem is to use Thévenin equivalent circuits to find the voltage v_x in Figure P3-41. Find the Thévenin equivalent circuit seen looking to the left of terminals A and B. Find the Thévenin equivalent circuit seen looking to the right of terminals A and B. Connect these equivalent circuits together and find the voltage v_x .

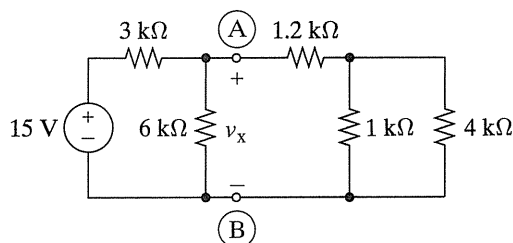


FIGURE P3-41

- 3-42 Figure P3-42 shows an active circuit with two accessible terminals. The output current is $i = 10 \text{ mA}$ when $v = 0$. The output voltage is $v = 6 \text{ V}$ when a $2.4 \text{ k}\Omega$ resistor is connected between the terminals. How much current would this source deliver to a 6-V battery?

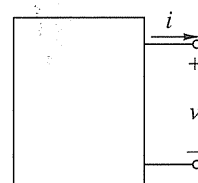


FIGURE P3-42

- 3-43 The $i-v$ characteristic of the active circuit in P3-42 is $5v + 500i = 60$. Find the output voltage when a $500 \text{ }\Omega$ resistive load is connected across the two accessible terminals.

- 3-44 Figure P3-42 shows a source circuit with two accessible terminals. Some voltage and current measurements at the accessible terminals are

$v(\text{V})$	-10	-5	0	+5	+10	12	13	14
$i(\text{mA})$	+5	+4	+3	+2	+1	0	-1	-2

- Use these data to plot the source $i-v$ characteristic.
- Develop a Thévenin equivalent circuit valid on the range $|v| < 10 \text{ V}$.
- Use the equivalent circuit to predict the source v and i_{sc} .
- Compare your results in part (c) with the given measurements and explain any differences.

- 3-45 The Thévenin equivalent parameters of a practical voltage source are $v_T = 25 \text{ V}$ and $R_T = 150 \text{ }\Omega$. Find the smallest load resistance for which the load voltage exceeds 15 V .

- 3-46 Use a sequence of source transformations to find the Thévenin equivalent at terminals A and B in Figure P3-46.

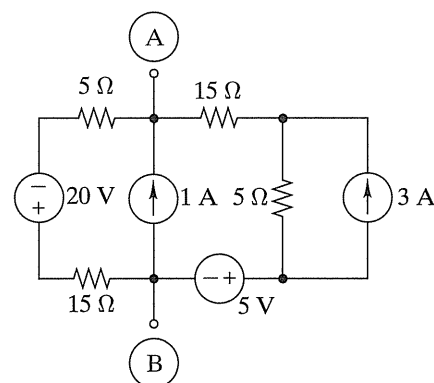


FIGURE P3-46

vo accessi-
mA when
a 2.4-k Ω
How much
y?

- 3-47 Select the value of R_L in Figure P3-47 so that $i_O = 80 \mu\text{A}$.

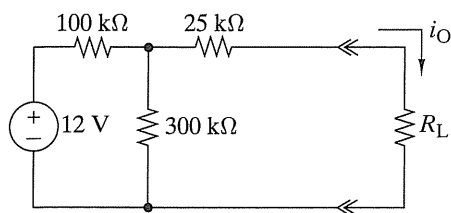


FIGURE P3-47

- 3-48 Find the Thévenin equivalent at terminals A and B in Figure P3-48.

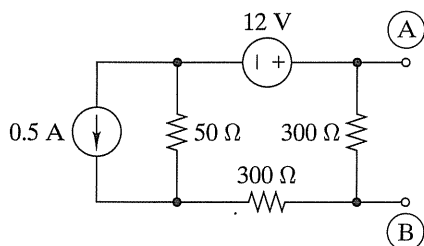


FIGURE P3-48

- 3-49 A nonlinear resistor is connected across a two-terminal source whose Thévenin equivalent is $v_T = 5 \text{ V}$ and $R_T = 500 \Omega$. The $i-v$ characteristic of the resistor is $i = 10^{-4}(\nu + 2\nu^{3.3})$. Plot the $i-v$ characteristic of the source and the resistor and graphically determine the voltage across and current through the nonlinear resistor.

- 3-50 A nonlinear resistor is connected across a two-terminal source whose Thévenin equivalent is $v_T = 10 \text{ V}$ and $R_T = 200 \Omega$. The $i-v$ characteristic of the resistor is $\nu = 4000 i^2$. Plot the $i-v$ characteristic of the source and the resistor and graphically determine the voltage across and current through the nonlinear resistor.

- 3-51 Find the Norton equivalent seen by R_L in Figure P3-51. Select the value of R_L so that 100 mW is delivered to the load.

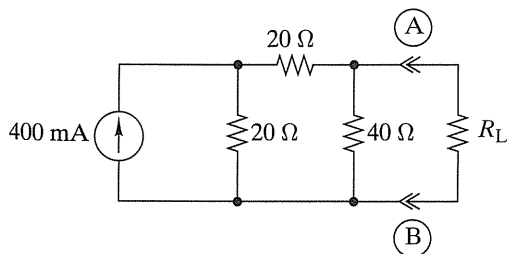


FIGURE P3-51

- 3-52 Find the Norton equivalent seen by R_L in Figure P3-52.

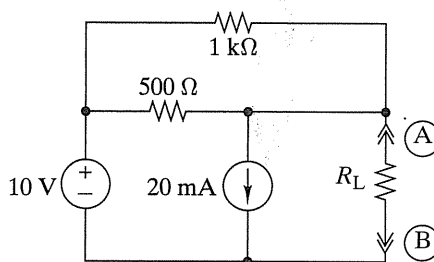


FIGURE P3-52

- 3-53 Find the Thévenin equivalent seen by R_L in Figure P3-53.

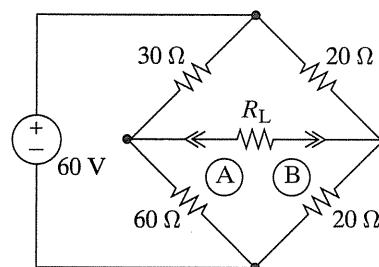


FIGURE P3-53

OBJECTIVE 3-4 MAXIMUM SIGNAL TRANSFER (SECT. 3-5)

Given a circuit containing linear resistors and independent sources:

- Find the maximum voltage, current, and power available at a specified pair of terminals.
- Find the resistive loads required to obtain the maximum available signal levels.

See Example 3-17 and Exercise 3-19

- 3-54 The resistance R in Figure P3-54 is adjusted until maximum power is delivered to the load consisting of R and the 6-k Ω resistor in parallel. Find the required value of R .

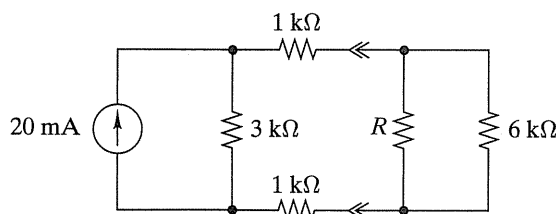


FIGURE P3-54