

analysis or design of complex OP AMP circuits can be based on these building blocks provided the interconnections are made between the output of one to the input of another.

- Important applications of OP AMPs include digital-to-digital converter, transducer interface circuits, and comparator circuits.

PROBLEMS

OBJECTIVE 4-1 LINEAR ACTIVE CIRCUITS (SECTS. 4-1, 4-2)

Given a circuit containing linear resistors, dependent sources, and independent sources, find selected output signal variables, input-output relationships, or input-output resistances. See Examples 4-2, 4-3, 4-4, 4-5, 4-6, 4-7, 4-8 and Exercises 4-1, 4-2, 4-3, 4-5, 4-6

- 4-1 Find the voltage gain v_O/v_S and current gain i_O/i_x in Figure P4-1 for $r = 4 \text{ k}\Omega$.

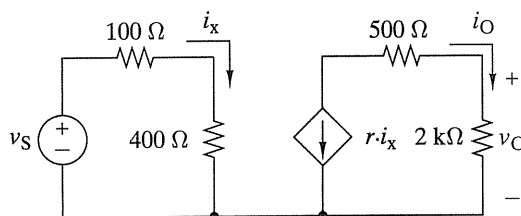


FIGURE P4-1

- 4-2 Find the voltage gain v_O/v_1 and the current gain i_O/i_S in Figure P4-2. For $i_S = 2 \text{ mA}$, find the power supplied by the input current source and the power delivered to the $2\text{-k}\Omega$ load resistor.

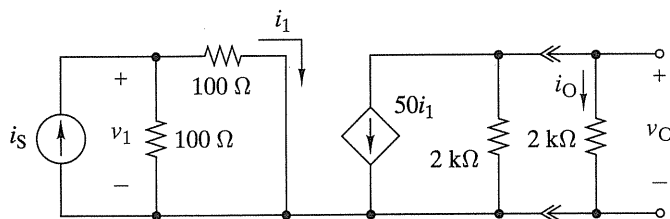


FIGURE P4-2

- 4-3 Find the voltage gain v_O/v_S and current gain i_O/i_x in Figure P4-3 for $g = 10^{-2} \text{ S}$.

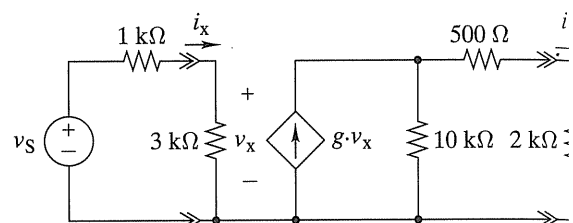


FIGURE P4-3

- 4-4 Find the voltage gain v_O/v_S and current gain i_O/i_x in Figure P4-4.

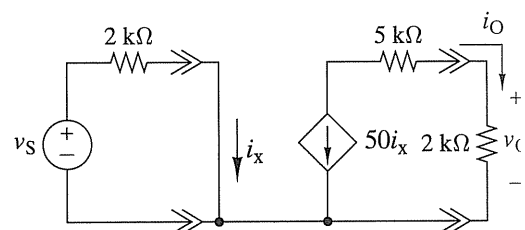


FIGURE P4-4

- 4-5 Find the current gain i_O/i_S in Figure P4-5.

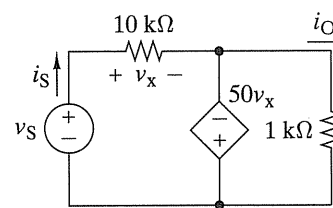


FIGURE P4-5

- 4-6 Find an expression for the current gain i_O/i_S in P4-6. Hint: Apply KCL at node A.

these four
en the out-
converters,

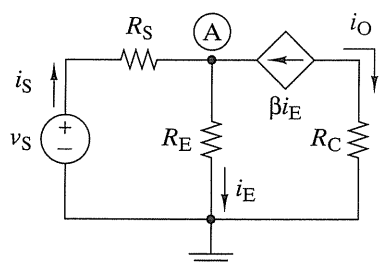


FIGURE P4-6

4-7 Find the voltage v_O in Figure P4-7.

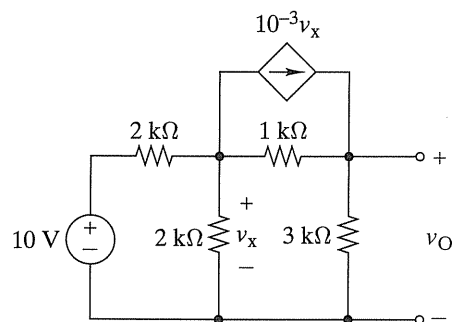


FIGURE P4-7

4-8 Find an expression for the current gain i_O/i_S in Figure P4-8.

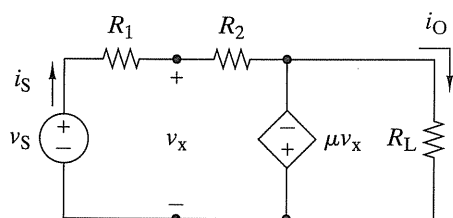


FIGURE P4-8

4-9 Find an expression for the voltage gain v_O/v_S in Figure P4-9.

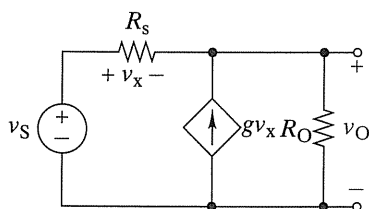


FIGURE P4-9

4-10 Find an expression for the voltage gain v_O/v_S in Figure P4-10.

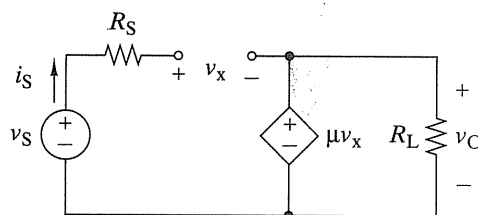


FIGURE P4-10

4-11 Find an expression for the voltage gain v_O/v_S in Figure P4-11.

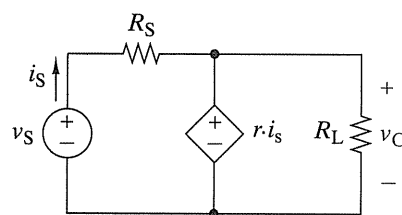


FIGURE P4-11

4-12 Find R_{IN} in Figure P4-12.

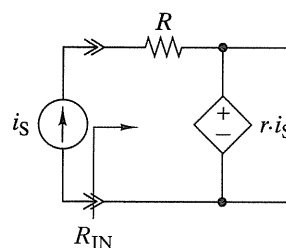


FIGURE P4-12

4-13 Find R_{IN} in Figure P4-13.

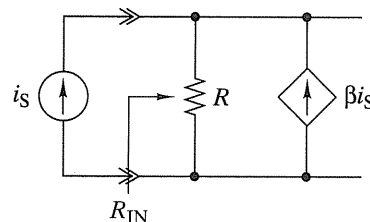


FIGURE P4-13

P4-16 are
V. Select a
tion mode

P4-18 are
 $v_S = 0.8$ V.

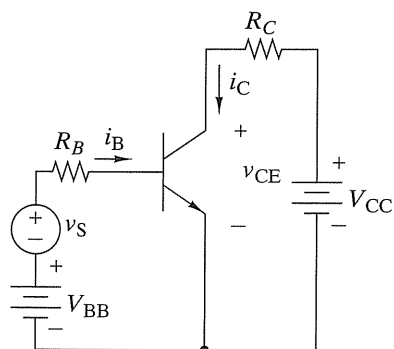


FIGURE P4-20

OBJECTIVE 4-3 OP AMP CIRCUIT ANALYSIS (SECTS. 4-4, 4-5)

Given a circuit consisting of linear resistors, OP AMPs, and independent sources, find selected output signals or input-output relationships.

See Examples 4-13, 4-14, 4-16, 4-17, 4-18, 4-19 and Exercises 4-10, 4-11, 4-12, 4-13, 4-15

4-21 Find v_O in terms of v_S in Figure P4-21.

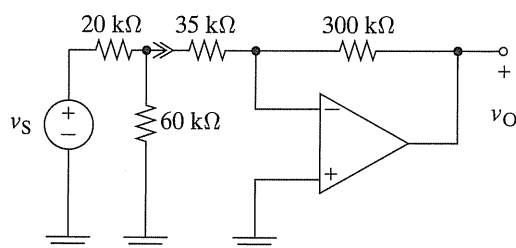


FIGURE P4-21

4-22 What is the range of the gain v_O/v_S in Figure P4-22?

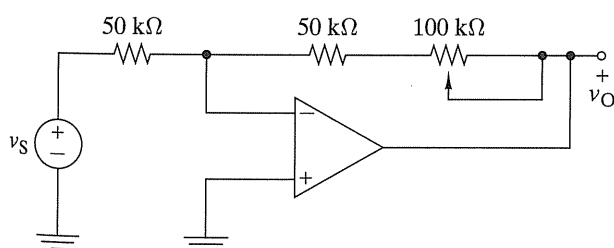


FIGURE P4-22

4-23 (a) Find v_O in terms of v_S in Figure P4-23.

(b) Find i_O for $v_S = 1.5$ V.

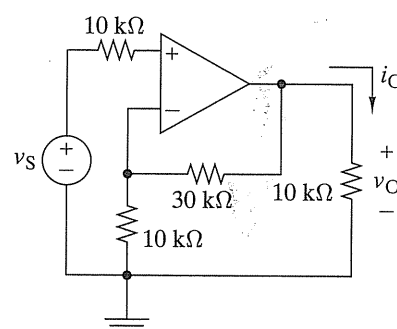


FIGURE P4-23

4-24 (a) Find v_O in terms of v_S in Figure P4-24.

(b) Find i_O for $v_S = 2$ V.

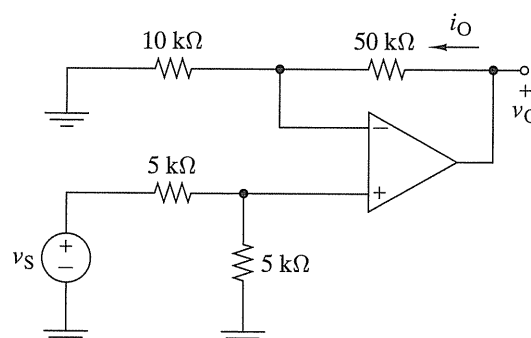


FIGURE P4-24

4-25 What is the gain v_O/v_S in Figure P4-25 when the switch is in position 1? Repeat for positions 2 and 3.

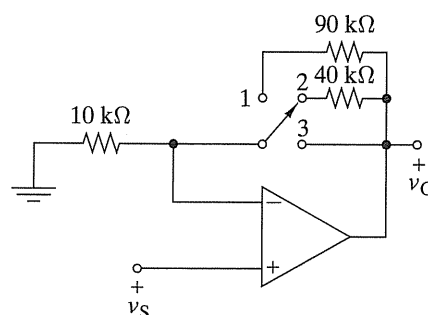


FIGURE P4-25

4-26 Find v_O in terms of the inputs v_1 and v_2 in Figure P4-26.

PROBLEMS

OBJECTIVE 5-1 BASIC WAVEFORMS (SECTS. 5-2, 5-3, 5-4)

Given an equation, graph, or word description of a linear combination of step, ramp, exponential, or sinusoid waveforms:

- Construct an alternative description of the waveform.
- Find the parameters or properties of the waveform.
- Construct new waveforms by summing, integrating, or differentiating the given waveform.

See Examples 5-1, 5-2, 5-3, 5-5, 5-6, 5-7, 5-8, 5-9 and Exercises 5-1, 5-2, 5-3, 5-4, 5-5, 5-6, 5-7

5-1 Sketch the following waveforms:

(a) $v_1(t) = -2u(t+1) + 4u(t-1)$ V

(b) $v_2(t) = u(t+2) - 2u(t)$ V

(c) $v_3(t) = \int_{-\infty}^t v_1(x) dx$

(d) $v_4(t) = \int_{-\infty}^t v_2(x) dx$

5-2 Sketch the following waveforms:

(a) $v_1(t) = 1 - u(t) - 2u(t-1)$ V

(b) $v_2(t) = -u(t+3) + 3u(t+1) - 2u(t)$ V

5-3 Sketch the following waveforms:

(a) $v_1(t) = -2r(t+1) + 2r(t-1)$ V

(b) $v_2(t) = r(t+1) - 2r(t-1) + r(t-3)$ V

(c) $v_3(t) = \frac{dv_1(t)}{dt}$

(d) $v_4(t) = \frac{dv_2(t)}{dt}$

5-4 Express the following signals as a sum of singularity functions.

(a) $v_1(t) = \begin{cases} 2 & t < 1 \\ -5 & 1 \leq t < 2 \\ 0 & 2 \leq t \end{cases}$

(b) $v_2(t) = \begin{cases} 0 & t < 0 \\ -4t & 0 \leq t < 2 \\ -12 + 2t & 2 \leq t < 6 \\ 0 & 6 \leq t \end{cases}$

5-5 Express the waveforms in Figure P5-5 as a sum of singularity functions.

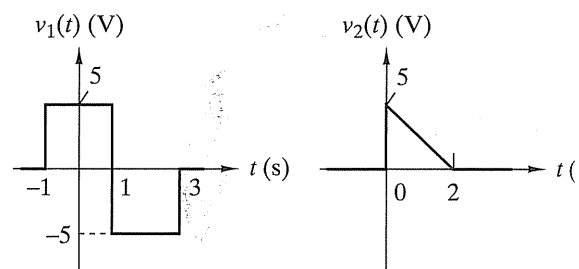


FIGURE P5-5

5-6 Write expressions for the derivatives of the waveforms in Figure P5-5.

5-7 A waveform $v(t)$ is zero for $t < 0$, rises linearly to 10 V at $t = 2$ s, remains at 10 V until $t = 4$ s, and abruptly drops to zero thereafter. Express the waveform as a sum of singularity functions.

5-8 Sketch the following exponential waveforms. Find amplitude and time constant of each waveform.

(a) $v_1(t) = [2e^{-10t}]u(t)$ V

(b) $v_2(t) = [10e^{-t/2}]u(t-1)$ V

(c) $v_3(t) = [5e^{-2(t-1)}]u(t-1)$ V

(d) $v_4(t) = [-10e^{-t/20}]u(t)$ V

5-9 Write expressions for the derivative ($t > 0$) and integral (from 0 to t) of the exponential waveform $v(t) = [0.5e^{-20t}]u(t)$ V.

5-10 An exponential waveform decays to 50% of its initial ($t = 0$) amplitude in 5 ms. Find the time constant of the waveform.

5-11 The amplitude of an exponential waveform is 5 V at $t = 0$ and 3.5 V at $t = 3$ ms. What is its amplitude at $t = 6$ ms?

5-12 Construct an exponential waveform that fits entirely within the unshaded region in Figure P5-12.

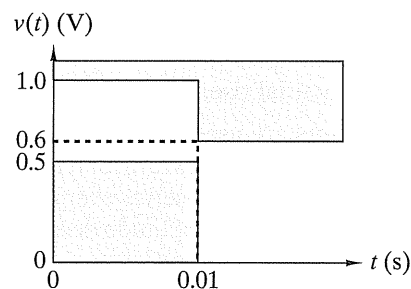


FIGURE P5-12

5-13 By direct substitution, show that the exponential function $v(t) = V_A e^{-at}$ satisfies the following first-order differential equation.

$$\frac{dv(t)}{dt} + av(t) = 0$$

5-14 Find the period, frequency, amplitude, time shift, and phase angle of the following sinusoids:

(a) $v_1(t) = 10 \cos(500\pi t) - 10 \sin(500\pi t)$ V

(b) $v_2(t) = -30 \cos(2000\pi t) + 20 \sin(2000\pi t)$ V

5-15 Find the amplitude and phase angle of the derivative of each sinusoid in Problem 5-14.

5-16 Write an expression for the sinusoid in Figure P5-16. What are the phase angle and time shift of the waveform?

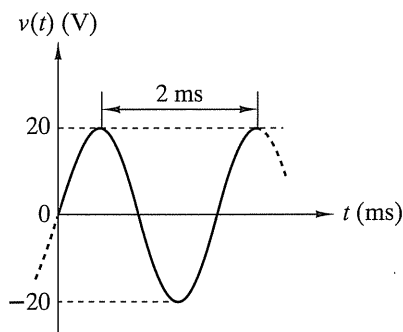


FIGURE P5-16

5-17 Find the Fourier coefficients, cyclic frequency, and radian frequency of the following sinusoids:

(a) $v_1(t) = 20 \cos(500\pi t + 180^\circ)$ V

(b) $v_2(t) = 20 \cos(500\pi t - 90^\circ)$ V

5-18 Find the sum of the two sinusoids in Problem 5-17.

5-19 Find the Fourier coefficients, cyclic frequency, and radian frequency of the following sinusoids:

(a) $v_1(t) = 30 \cos(2\pi 400t + 30^\circ)$ V

(b) $v_2(t) = 20 \cos(2000\pi t - 60^\circ)$ V

5-20 Find the time shift of each sinusoid in Problem 5-19.

OBJECTIVE 5-2 COMPOSITE WAVEFORMS (SECT. 5-5)

Given an equation, graph, or word description of a composite waveform:

- Construct an alternative description of the waveform.
- Find the parameters or properties of the waveform.
- Find new waveforms by integrating, or differentiating the given waveform.

See Examples 5-10, 5-11, 5-12, 5-13, 5-14, 5-15 and Exercises 5-8, 5-9

5-21 Sketch the following composite waveforms. What are the maximum and minimum values of each waveform?

(a) $v_1(t) = 10[1 - e^{-5t}]u(t)$ V

(b) $v_2(t) = 20[e^{-5t} - e^{-10t}]u(t)$ V

5-22 Sketch the following composite waveforms. What are the maximum and minimum values of each waveform?

(a) $v_1(t) = 20 - 10 \sin(10\pi t)$ V

(b) $v_2(t) = 10[e^{-5t} + \sin(10\pi t)]u(t)$ V

5-23 Sketch the damped ramp $v(t) = 20te^{-5t}u(t)$. Find the maximum value of the waveform and the time at which it occurs.

5-24 The value of the waveform $v(t) = (V_A - V_B e^{-\alpha t})u(t)$ is 5 V at $t = 0$, 8 V at $t = 5$ ms, and approaches 12 V as $t \rightarrow \infty$. Find V_A , V_B , and α then sketch the waveform.

5-25 Write an expression for the composite sinusoidal waveform in Figure P5-25.

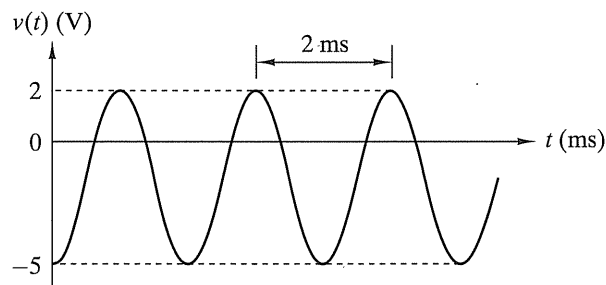


FIGURE P5-25

5-26 A waveform of the form $v(t) = 6 - 10 \sin(\beta t)$ periodically reaches a minimum every 4 ms. Find the values of V_{\max} , V_{\min} , and β ; then sketch the waveform.

5-27 Write an expression for the composite exponential waveform in Figure P5-27.

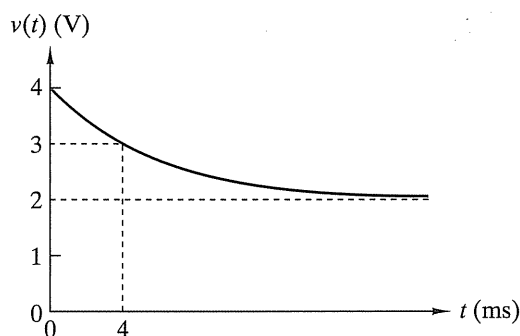


FIGURE P5-27

5-28 Sketch the double exponential $v(t) = 30(e^{-20t} - e^{-100t})u(t)$. Find the maximum value of the waveform and the time at which it occurs.

5-29 Write an expression for the damped sine waveform in Figure P5-29.