

# EEE411/EEE511 LAB # 7


## Voltage Controlled Oscillator (VCO)

### Preliminary Work:

In this experiment you will design and construct a voltage controlled oscillator (VCO) with an output buffer. The oscillator output frequency is controlled by the value of  $V_t$  ( $V_{tune}$ ). This is accomplished by changing the capacitance of  $D_{var}$  (Varactor diode) through changing its voltage (Please note that varactor diodes are specially manufactured diodes. Their reverse biased junction capacitance which varies with reverse bias voltage is used to obtain a voltage controlled capacitance). The resonance frequency of the tank circuit formed by the capacitance of  $D_{var}$  and  $L$  determines the frequency of operation. The differential pair ( $T_1$  and  $T_2$ ) serve as the gain block. The buffer transistor  $T_3$  isolates the circuit from the effects of the output load.

The output frequency range of this oscillator must cover the necessary range to be able to convert the RF input frequency range of the project receiver. The input frequency range of your receiver is 55 $\pm$ 1 MHz. Your mixer is going to convert the input signal from the lower side (i.e. the frequency of the mixer is lower than the frequency of the signal). Since your IF frequency is 10.7 MHz.

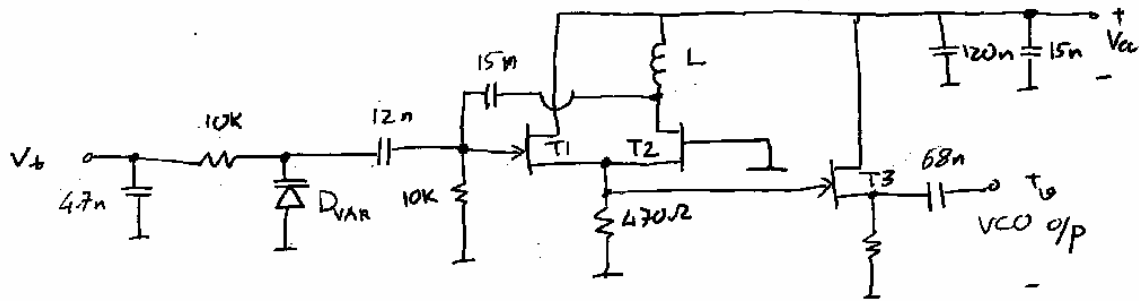1. Please find the value of  $L$  to satisfy this condition.  $T_1$ ,  $T_2$  and  $T_3$  are BF245C transistors, and the varactor diode is BB106. The varactor diode capacitance changes in the range 4-20pF for the voltage range of 0-20V.  $V_{cc}$  is 12 Volts.
2. Calculate the output frequency as a function of the capacitance of  $D_{var}$  for a number of capacitance values.
3. Check your design using SPICE in transient analysis for a number of varactor capacitance values (The same values as in step 2). For the simulation, use simple capacitor model to represent  $D_{var}$ .
4. Please bring the following instruments to the lab:
  - a. A soldering iron with a sharp, pointed soldering iron tip suitable for mounting SMD components.
  - b. A tweezer suitable for SMD mounting.



The circuit diagram of the VCO

### Lab Work:

1. In this experiment you are going to construct your circuit on a pre made PCB using surface mount components. The SMD components and the layout of the circuit will be given to you during the experiment. Do not forget to connect power supply decoupling capacitors to the DC power supplies. Measure the oscillation frequency range and amplitudes at a number of frequencies.
2. Plot o/p frequency vs.  $V_t$ .
3. Calculate and plot VCO gain which is also called modulation sensitivity ( $dfreq/dV_{bias}$ ) versus  $V_t$ .
4. Connect your VCO to the LO drive of the Mixer. Adjust the frequency of your VCO using a potentiometer. Connect the signal generator to the RF input. Adjust the frequency to 30MHz. Observe the o/p on the scope at the IF output before the 10.7 MHz filter by adjusting the VCO frequency using the potentiometer.
5. Take the scope to FFT mode (Math Menu). Scan the VCO frequency at the given frequency band. Observe the mixer o/p spectrum at that range.

### Discussion:

Compare your experimental results with your estimations and spice simulations. Comment on the results.

### SPICE Model of BF245C:

```
.MODEL BF245C NJF(Beta=1.5m Betatce=-.5 Rd=1 Rs=1 Lambda=3.8m Vto=-3.099
+ Vtotc=-2.5m Is=33.57f Isr=322.4f N=1 Nr=2 Xti=3 Alpha=311.7u
+ Vk=243.6 Cgd=3.35p M=.3622 Pb=1 Fc=.5 Cgs=3.736p Kf=13.56E-18
+ Af=1)
```

Note: You can use a different SPICE model file which you obtained from the web yourselves.