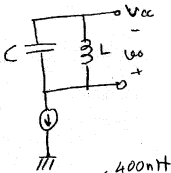


Question 1) (20 points)



The tank circuit which is shown above is to be used at a high frequency design. The self resonance of the inductor is 100 MHz. Please answer the following:

- (10 points) Can you make a 200 MHz resonant tank circuit using this inductor? If so, calculate the value of the capacitor to obtain the resonance frequency, *perhaps your answer*
- (10 points) Can you make a 50 MHz resonant tank circuit using this inductor? If so, calculate the value of the capacitor to obtain the resonance frequency, *explain your answer*

a-) No, because the inductor acts as a capacitor above its parallel resonance frequency

b-) Yes, the equivalent model of the inductor is ω_0 at self resonance is $628.3 \times 10^6 \text{ rad/sec}$

$$L = 400 \text{ nH} \quad \left\{ \right. \quad C_S = \frac{1}{\omega_0^2 L} = \frac{1}{(2\pi \times 100 \times 10^6)^2 \times 400 \times 10^{-9}} = 6.333 \times 10^{-12} \text{ F}$$


Four times C_L is needed to lower the parallel resonance to its half $\Rightarrow$ The total parallel capacitance

$$C_T = 25.33 \text{ pF}$$

The capacitance needed over the C_S is

$$\boxed{25.33 - 6.33 = 19 \text{ pF}}$$

Question 2) (30 points)

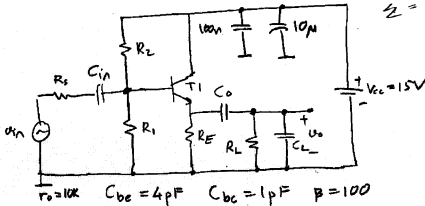


$$\begin{aligned} C_{be} &= 4 \\ C_{bc} &= 3 \\ C_L &= 4 \\ \Sigma &= 4 \end{aligned}$$

b-) bias 3

$$\begin{aligned} C_{in} &= 4 \\ C_{out} &= 4 \\ \Sigma &= 4 \end{aligned}$$

For the circuit given above, $R_s=0\Omega$, $R_1=1k\Omega$, $R_2=4k\Omega$, $R_E=660\Omega$, $V_T=0.7V$, $C_{in}=100nF$, $C_o=10\mu F$, $R_L=500\Omega$ and $C_L=100pF$. Assume that $R_1, R_2 \ll R_s$.

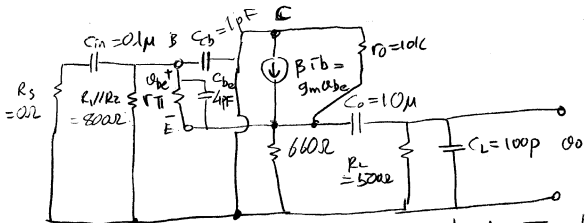- (15 points) Estimate the higher 3 dB cut-off frequency by the method of open-circuit time constants.
- (15 points) Estimate the lower 3 dB cut-off frequency by the method of short-circuit time constants.




a-) At high frequencies C_{in} & C_o are short. To calculate R_{be} , open circuit the high-frequency capacitors, and put V_T across B and E

$$I_E = \left(15 \times \frac{1}{1+4} - V_T \right) \left(660 \parallel \frac{1 \times 4}{5(\beta+1)} \right) = \frac{3-0.7}{660+8} = \frac{2.3V}{668\Omega}$$

$$= 3.44 \text{ mA}$$
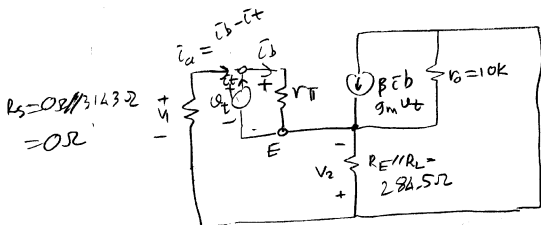
$$\frac{1}{g_m} = \frac{26}{3.44} = 7.56\Omega \quad r_{\pi} = \frac{\beta}{g_m} = \frac{100}{7.56} = 13.23k\Omega$$



$$R'_E = R_E // R_L // r_o = 276.6 \Omega$$

$$i_a = i_b - i_t \quad v_t = i_b r_{\pi} = v_1 + v_2 = -i_a R_s - (\beta + 1) i_b R'_E + i_t R'_E$$

$$v_t = i_b r_{\pi} = -i_b R_s + i_t R_s - (\beta + 1) i_b R'_E + i_t R'_E$$

$$i_b = (r_{\pi} + R_s + (\beta + 1) R'_E) i_t \Rightarrow i_b = \frac{R_s r_{\pi} R'_E}{r_{\pi} + R_s + (\beta + 1) R'_E} i_t$$

$$R_{be} = \frac{v_t}{i_t} = \frac{i_b r_{\pi}}{i_t} = \frac{(R_s + R'_E) r_{\pi}}{r_{\pi} + R_s + (\beta + 1) R'_E} \quad \frac{i_t}{i_b} = \frac{276.6 \times 756}{756 + 101 \times 276.6} = 7.35 \Omega$$

$$\tau_{be} = 7.3 \times 4 \times 10^{-12} = 29.2 \text{ psec} \approx 29.2 \text{ nsec}$$

R_{cb} is a capacitor connected between base & the ground.
 Therefore it sees the amplifier input impedance in parallel with $R_s \Rightarrow 29.1 \text{ psec}$

$$R_{cb} = \underbrace{R_s // R_1 // R_2}_{0.8 \Omega} // (r_{\pi} + (\beta + 1) (R_E // R_L // r_o))$$

$$\Rightarrow R_{cb} = 0 // (756.8 + 101 \times 276.6) \approx 0.8 \Omega$$

$\hookrightarrow$ large compared to 0.8Ω

$$\tau_{bc} = 0 \text{ sec}$$

(2-a) continued

C_L sees R_{CL}

$$R_{CL} = r_o \parallel R_L \parallel R_E \parallel \left(\frac{r_{\pi}}{\beta+1} + \frac{R_3 \parallel R_1 \parallel R_2}{\beta+1} \right)$$

$\cong 1/g_m$ $\cong 0$

$$= (276.6 \Omega) \parallel \left(\frac{1}{g_m} + \frac{0}{101} \right) = 276.6 \parallel \left(\frac{26}{3.44} + 0 \right)$$

$$= 276.6 \parallel 7.5 \quad \quad \quad = 276.6 \parallel 7.5 \cong 7.3 \Omega$$

$$\approx \left(\frac{1}{g_m} + \frac{R_3}{\beta+1} \right)$$

$$\tau_{CL} = 7.3 \Omega \times 100 \times 10^{-12} = 730 \text{ psec} = 0.730 \text{ nsec}$$

$$\Sigma \tau = \tau_{be} + \tau_{cb} + \tau_{CL} = 0.029 \text{ nsec} + 0 + 0.73 \text{ nsec}$$

0.759 nsec

$$\omega_{3dB} = 1317 \text{ Mrad/sec}$$

$$f_{3dB} = 209.7 \text{ MHz}$$

(2-b)

$$b-) R_{Cin} = R_s + (r_{\pi} + (\beta + 1)(R_E \parallel r_o \parallel R_L)) \parallel \underbrace{R_1 \parallel R_2}_{500\Omega}$$

$$= 0 + (756 + 104 \times 276) \parallel 500$$

$$\rightarrow 28692 \parallel 500 = 778\Omega$$

$$R_{Co} = R_E \parallel r_o \parallel \left(\frac{1}{g_m} + \frac{R_s}{\beta + 1} \right) + R_L$$

$R_s = 0$

$$660 \parallel 10000 \parallel (756 + 500) \approx 507.6$$

$$\tau_{Cin} = 778 \times 10^{-7} = 0.778 \times 10^{-4} \text{ sec}$$

$$\tau_{Co} = 507.6 \times 10^{-5} \text{ sec}$$

$$\frac{1}{\tau_{Co}} + \frac{1}{\tau_{Cin}} = 197 \text{ rad/sec} + 12853 \text{ rad/sec} = 13050 \text{ rad/sec}$$


$$f_{3dB} = 2077 \text{ Hz}$$

2-a) alternative solution

$$R_{be} = \frac{R_E' r_{\pi}}{r_{\pi} + (\beta + 1)R_E'} \quad \text{for } R_s = 0$$

$$= \frac{1}{\frac{r_{\pi}}{R_E' r_{\pi}} + \frac{\beta R_E'}{R_E' r_{\pi}} + \frac{R_E'}{R_E' r_{\pi}}} = \frac{1}{\frac{1}{R_E'} + g_m + \frac{1}{r_{\pi}}}$$

Question 3) (26 points)

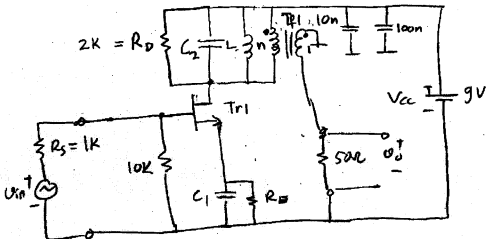

At the tuned circuit given above, $C_{gd}=1\text{pF}$, $C_{gs}=3\text{pF}$, $g_m=10\text{mS}$, $C_1=100\text{nF}$, $R_E=120\Omega$. Design the tuned circuit by:

- (6 points) By finding the transformer ratio, n (T_n is an ideal transformer), to present matched impedance to the drain of the tank circuit.
- (6 points) By choosing C_2 such that it is 3 times the reflected miller capacitance to the drain,
- (6 points) By choosing L to operate at 40 MHz,
- (8 points) Verify your design by calculating the 3dB BW of the gate circuit? Comment on the result.

$$a-) n^2 50 = 2000 \Rightarrow n = \frac{2000}{50} = 40 \Rightarrow n = 6.35$$

$$b-) C_{\text{miller}} = C_{gd} \times (1 + R_s g_m) = 1\text{pF} \times 11 = 11\text{pF}$$

$$C_2 = 3 \times 11\text{pF} = 33\text{pF}$$

$$c-) C_{\text{total}} = 33\text{pF} + 11\text{pF} = 44\text{pF}$$

$$L_3 = \frac{1}{\omega_0^2 C_{\text{drain}}} = \frac{1}{(2\pi \times 40 \times 10^6)^2 \times 44 \times 10^{-12}} = 360\text{nH}$$

$$d-) C_{\text{in}} = (1 + R_L g_m) C_{gd} = 1\text{pF} (1 + 10) = 11\text{pF} + 3\text{pF} = 14\text{pF}$$


$$\omega_{3\text{dB}} = \frac{1}{14 \times 10^{-12} \times 100000} = 71.43\text{Mrad/sec} \Rightarrow f_{3\text{dB}} = 11.37\text{MHz}$$

T. Reyhan

EEE411MT-2008-11-23-2013

$\Rightarrow$ Input BW does not match the tank circuit design!

Question 4) (24 points)

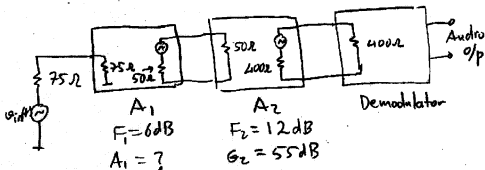

Two amplifiers and a demodulator is cascaded as shown in the figure given above. Please answer the following:

- (8 points) What should be the minimum gain of A1 so that the overall noise figure of the cascaded amplifier is less than or equal to 7dB.
- (8 points) Calculate the minimum signal level at the input of the cascaded amplifier in dBm, so that the cascaded amplifier can deliver a S/N ratio = 12dB at its output to the demodulator if the bandwidth of the demodulator is 100kHz?
- (8 points) What is the noise temperature of the cascaded amplifier?

a-) $7\text{dB} \Rightarrow 5\text{ times}$, $6\text{dB} \Rightarrow 4\text{ times}$, $12\text{dB} \Rightarrow 16\text{ times}$

$$F_{12} = 5 = 4 + \frac{F_2 - 1}{G_1} \Rightarrow G_1 = \frac{15}{1} = 15$$

$$G_1 = 10 \times \log_{10} 15 = 11.76\text{dB} \approx 11.7\text{dB}$$

b-) $S_{\text{required}} = F k T_0 B \times (S/N_{\text{required}})$

$$= 5 \times 1.38 \times 10^{-23} \times 290 \times 10^5 \times 16 = 3.2 \times 10^{-14} \text{ Watts}$$

$$= 3.2 \times 10^{-11} \text{ mW}$$

$$= 10 \log_{10} 3.2 \times 10^{-11} = -104.9\text{dBm}$$

c-) $(F-1)290 = T_n = (5-1) \times 290 = 4 \times 290 = 1160\text{K}$