


HW#3 Solutions 2008

EE 411/511

(1)

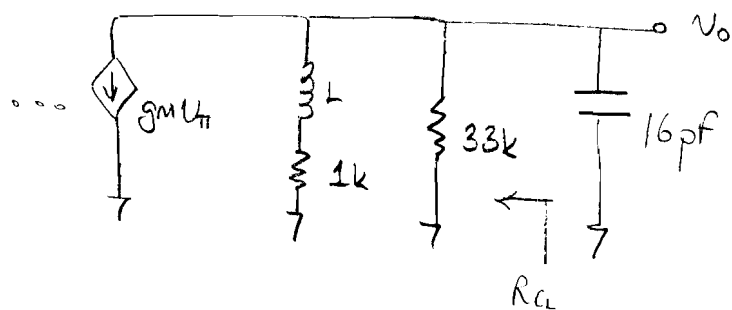1) a) The transistor is an ideal NPN $\Rightarrow C_{be}=0, C_{bc}=0$

Since C_1, C_2 and C_3 are very large they do not affect the upper cutoff frequency and will be short circuited as mentioned in Open-Circuit time constants method.



$$L=0 \Rightarrow R_{CL} = 1k\Omega // 33k\Omega \approx 1k\Omega$$

$$\tau_{CL} = R_{CL} \cdot C_L = 16ns$$

$$\omega_{h,est} = \frac{1}{\tau_{CL}} \Rightarrow \omega_{h,est} = \frac{1}{16 \times 10^{-9}} = 62,5 \times 10^6 \text{ rad/sec}$$

$$f_{h,est} \approx 9,95 \text{ MHz}$$

b) In order to extend the upper cutoff frequency shunt peaking technique is utilized for this amplifier.

The impedance of the RLC network can be written as :

$$Z(s) = (sL + 1k) // \frac{1}{sC} // 33k \approx (sL + 1k) // \frac{1}{sC}$$

↑
assuming that 33k is large compared to $(sL + 1k)$

Now, as explained in section 8.2.1 of the course book, an expression for $\frac{\omega_{h,new}}{\omega_{h,old}}$ can be derived from this impedance $Z(s)$:


$$\frac{\omega_{h,new}}{\omega_{h,old}} = \sqrt{\left(-\frac{m^2}{2} + m + 1\right)} + \sqrt{\left(-\frac{m^2}{2} + m + 1\right)^2 + m^2}, \text{ where } m = \frac{RC}{L/R}, R = 1k\Omega$$

Then, maximum -3dB frequency ($\omega_{h,new}$) is found as 1,85 times $\omega_{h,old}$, when $m = \sqrt{2}$.

$$\Rightarrow m = \frac{RC}{L/R} = 1,41 = \frac{10^3 \cdot 16 \times 10^{-12}}{L/10^3} \Rightarrow L = 11,3 \mu H$$

(2)

2) a)

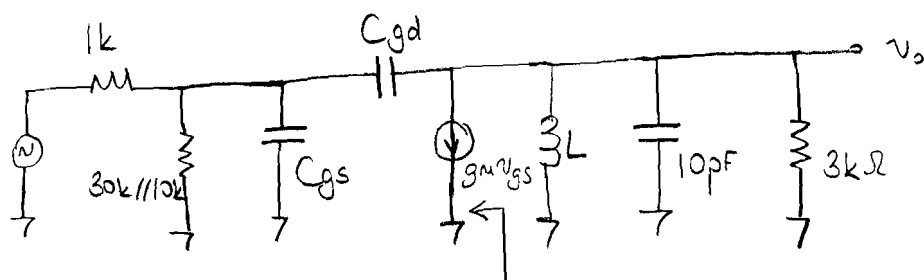

$$2\pi f_0 = \frac{1}{\sqrt{LC_{TOTAL}}}$$

$$\Rightarrow L = \frac{1}{C_{TOTAL} \times (2\pi f_0)^2}$$

$$= \frac{1}{11,86 \times 10^{-12} \times (2\pi 50 \times 10^6)^2}$$

$$\Rightarrow L = \boxed{0,854 \mu H}$$

If we use a test voltage source to find the admittance seen by the tank circuit, we end up with an equivalent resistance in parallel with an equivalent capacitance:

$$C_{eq} = C_{gd} [1 + g_m (\overbrace{1k // 10k // 30k}^{882\Omega})]$$

$$= 0,1 \times 10^{-12} [1 + 20 \times 10^{-3} \times 882]$$

$$= 1,86 \text{ pF}$$

$$\Rightarrow C_{TOTAL} = 11,86 \text{ pF}$$

b)

$$C_{input} = C_{gs} + C_{gd} (1 + g_m R_L) \quad * \text{ See lecture notes (Tuned Amplifiers)}$$

$$= 0,2 \times 10^{-12} + 0,1 \times 10^{-12} (1 + 20 \times 10^{-3} \times 3 \times 10^3) \quad * \text{ Assuming } C_{in} \text{ is large compared to transistor capacitances. (not included)}$$

$$= \boxed{6,3 \text{ pF}}$$

c)

$$R_{cin} = 1k // 10k // 30k = 882\Omega$$

Using Open Circuit time constants estimation:

$$\omega_{h,est} = \frac{1}{\tau_{cin}} = \frac{1}{R_{cin} C_{in}} = \frac{1}{882 \times 6,3 \times 10^{-12}} = 1,8 \times 10^8 \text{ rad/sec}$$

$$\Rightarrow f_{h,est} = \boxed{28,6 \text{ MHz}}$$