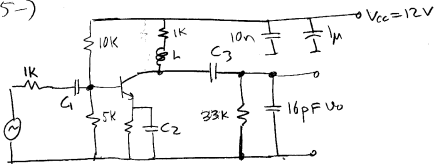


EEE 411/511 - HW#3 due November 7, 2008
assigned Nov 02, 2008

5-)



C_1, C_2 & C_3 are very large $I_c = 10\text{mA}$ $V_T = 26\text{mV}$


The transistor is an ideal NPN transistor

a-) Find upper cutoff frequency of the amplifier with $L = 0$.

b-) Extend the upper cutoff frequency for maximum BW by choosing an appropriate value for L .

Hint = Please make the necessary simplifying assumptions.

6-)

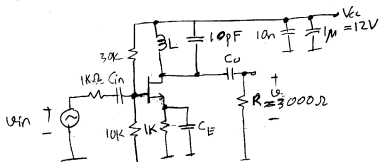

$$g_m = 20\text{mS}$$

$$C_{gs} = 0.2\text{pF} \quad C_{gd} = 0.1\text{pF}$$

a-) Find L to make $f_{\text{resonance}} = 50\text{MHz}$

b-) Find the i/p capacitance of the circuit

c-) Estimate upper cutoff frequency from the result in (b)