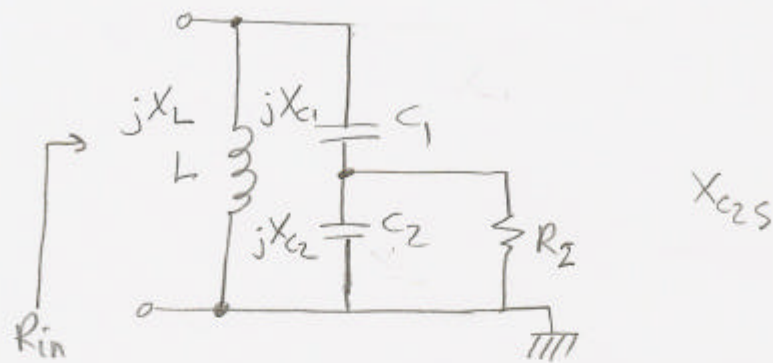



note on resonant impedance transformer



In this circuit we would like to find the impedance seen in parallel with the inductor, namely R_{in} . The problem is similar to Π -match, with the differences:

- a-) The ground is at a different position
- b-) We are trying to find the equivalent resistance seen in parallel with L instead of in parallel with C_1

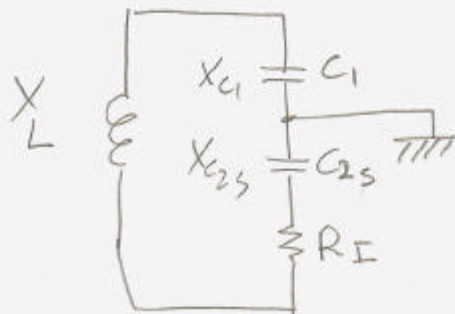The above circuit is equivalent to grounding changed



$$R_I = R_L / (Q_R^2 + 1)$$

$$X_{C2S} = \frac{Q_R^2}{Q_R^2 + 1} X_{C2}$$

The circuit resonates at the frequency ω_0 defined by

(2)

Our aim is to transform the resistance R_L to R_{in} at resonance. If we let

$$K = \frac{R_{PL}}{R_2} = \frac{R_{in}}{R_2} \quad \text{where } R_{PL} \text{ is the equivalent resistance in parallel with } L$$

$$R_{in} = R_{PL} = \frac{R_I}{(Q^2 + 1)} \quad \text{where } Q = Q_L + Q_R$$

$$(Q^2 + 1) R_I = R_{in} \quad Q$$

$$(Q^2 + 1) R_I = R_2$$

dividing the 2 equations

$$\frac{Q^2 + 1}{Q^2 + 1} = \frac{R_{in}}{R_2} = K \Rightarrow$$

$$Q^2 + 1 = K Q^2 + K \Rightarrow K Q^2 = Q^2 + 1 - K \Rightarrow$$

$$Q_R = \sqrt{\frac{Q^2 + 1 - K}{K}}$$

$$Q_L = Q - Q_R = Q - \sqrt{\frac{Q^2 + 1 - K}{K}}$$

After finding Q_L & Q_R for the required Q & K R_I can be found by

$$R_I = \frac{R_2}{Q^2 + 1} \quad \text{and} \quad Q_L = Q - Q_R = \frac{X_{C1}}{R_F} \quad \text{and} \quad Q = \frac{R_{in}}{X_L}$$

$$(Q^2 + 1) R_E = R_{in} \Rightarrow R_E = \frac{R_{in}}{Q^2 + 1}$$


$$(Q_R^2 + 1) R_E = R_2 \Rightarrow Q_R^2 = \frac{R_2}{R_E} - 1$$

$$Q - Q_R = Q_L = \frac{X_{C1}}{R_E} \text{ and finally}$$

$$Q = \frac{R_{in}}{X_L} \text{ all unknowns being found.}$$

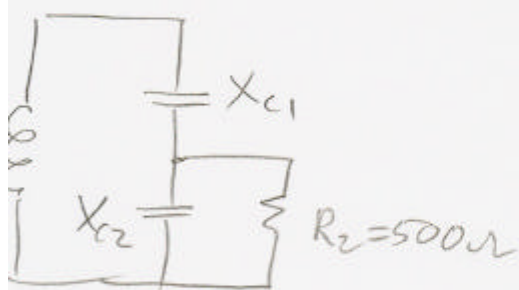Example:

Find the reactances of the upward transformer which converts 500Ω into 1000Ω employing a $Q = 3$.



$$(Q^2 + 1) R_E = R_{in}$$

$$(3^2 + 1) R_E = 1000$$

$$\Rightarrow R_E = \frac{1000}{10} = 100\Omega$$

$$(Q_R^2 + 1) R_E = 500\Omega \Rightarrow$$

$$+1 = \frac{500}{100} = 5 \Rightarrow Q_R = 2$$

$$- = 3 - 2 = Q_L = 1 \Rightarrow X_{C1} = -100j$$

$$2 = \frac{500}{X_{C1}} \Rightarrow X_{C1} = \frac{-500}{2} = -250j$$

$$- = \frac{R_{in}}{Q} = \frac{1000}{3} = +333.33j$$