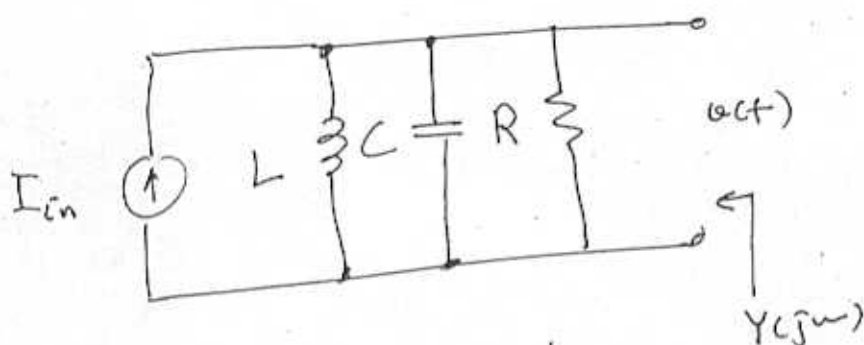


1.10.2003

RLC Circuits and their applications

(1)

Bandwidth and Q



$$Y(jw) = G + jwC + \frac{1}{jwL}$$

$$= G + j\left(wC - \frac{1}{wL}\right)$$

Conductance at the lowest or the impedance is at the highest and it is real at

$$wC - \frac{1}{wL} = 0 \quad \text{or} \quad w = \frac{1}{\sqrt{LC}}$$

Different definitions of Q around

$$Q = w \frac{\text{Energy stored}}{\text{average power dissipated}} \quad \text{dimensionless}$$

Q factor or Quality factor of the tank inductor or capacitor

$$= \frac{2\pi}{T} \frac{\text{Energy stored}}{P_{av}} = 2\pi \frac{\text{energy stored}}{T \times P_{av}}$$

$$= 2\pi \frac{\text{energy stored}}{\text{Energy dissipated in a cycle}}$$

1-10-2003

(2)

peak voltage = $I_{pk} R$ at resonance

$$\text{energy stored} = \frac{1}{2} C V_{pk}^2 = \frac{1}{2} C (I_{pk} R)^2$$

$$\text{average diss. pow} = \frac{1}{2} I_{pk}^2 R$$

$$Q = \omega_0 \frac{E_{\text{stored}}}{P_{\text{av}}} = \omega_0 \frac{\frac{1}{2} C I_{pk}^2 R}{\frac{1}{2} I_{pk}^2 R} = \omega_0 C R$$

since $\omega_0 C = \frac{1}{\omega_0 L}$ at resonance

$$Q = \frac{1}{\omega_0 L} R = \frac{\sqrt{LC}}{1} \times \frac{R}{L} = R \sqrt{\frac{C}{L}} = \frac{R}{\sqrt{L/C}}$$

also the reactive currents peak at resonance along with the voltage

$$|I_{\text{ind}}| = |I_{\text{cap}}| = \frac{|V|}{|Z|} = \frac{|I_R| R}{\omega L} = Q |I_R|$$

$\underbrace{\quad}_{=Q}$

Therefore branch currents are multiplied by Q at resonance, means that if $Q=1000$ and you drive 1mA input to the tank, the capacitor and the inductor must be rated at 1 Amps

1.10.2003
(3)

approximate
The 3 dB BW of high Q
resonators

$$\text{let } \omega = \omega_0 + \Delta\omega \quad |\Delta\omega| \ll \omega_0$$

$$Y = G + \frac{-j}{\omega L} + j\omega C = G + j\left(\omega C - \frac{1}{\omega L}\right)$$
$$= G + j\frac{C}{\omega} \left[\omega^2 - \frac{1}{LC} \right]$$

$$\text{letting } \omega = \omega_0 + \Delta\omega$$

$$Y = G + j\frac{C}{\omega} \left[\cancel{\omega_0^2} + 2\omega_0\Delta\omega + \cancel{\Delta\omega^2} - \frac{1}{LC} \right]$$

but $\omega_0^2 = \frac{1}{LC}$ and letting $|\Delta\omega| \ll \omega$

$$Y = G + j\frac{C}{\omega} 2\omega_0\Delta\omega = G + j2C\Delta\omega$$

just like a parallel RC circuit
with $2C \rightarrow C$ & $\Delta\omega \rightarrow \omega$

The 3 dB BW of the system is defined by

$$G = \pm 2C\Delta\omega \Rightarrow$$

$$\Delta\omega = \pm \frac{G}{2C} \Rightarrow BW = 2\Delta\omega = \frac{G}{C}$$


The normalized BW is given by

$$\frac{BW}{\omega_0} = \frac{2\Delta\omega}{\omega} = \frac{G}{C} \cdot \frac{\sqrt{LC}}{1} = G\sqrt{\frac{L}{C}} = \frac{1}{R}\sqrt{\frac{L}{C}} = \frac{1}{Q}$$

$$\boxed{\frac{\omega_0}{BW} = Q}$$

1.10.2003

(4)

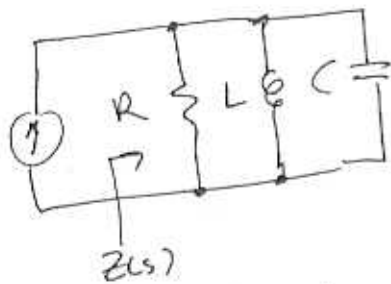

The natural response is determined by the zeroes of the admittance or the poles of the impedance $Z(s)$

$$G(s) = \frac{1}{Z(s)} = G + sC + \frac{1}{sL} = \frac{GLs + s^2LC + 1}{sL}$$

$$GLs + LCs^2 + 1 = \underbrace{LC}_{a}s^2 + \underbrace{GL}_{b}s + \underbrace{1}_{c} = 0$$

$$s_{1,2} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} = \frac{-GL \pm \sqrt{G^2L^2 - 4LC}}{2LC}$$

$$= \frac{-G}{2C} \pm \sqrt{\frac{G^2L^2}{4L^2C^2} - \frac{1}{LC}}$$

$$= -\frac{1}{2RC} \pm \sqrt{\frac{1}{4R^2C^2} - \frac{1}{LC}}$$

The damping factor

$$v_n(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} =$$

$$= B_1 e^{-\frac{t}{2RC}} \sin(\omega t + \theta)$$

where

$$\frac{1}{4R^2C^2} - \frac{1}{LC} < 0$$

or

$$\frac{1}{LC} > \left(\frac{1}{2RC}\right)^2$$

$\Rightarrow$ high Q

1.10.2003

(5)

The time response can also be written as

$$Q = \frac{\omega_0}{BW} = RC \omega_0$$

$$\Rightarrow RC = \frac{Q}{\omega_0} \Rightarrow \frac{1}{2RC} = \frac{\omega_0}{2Q} = \frac{\frac{2\pi}{T}}{2Q} = \frac{1}{TQ}$$

$$\Rightarrow \frac{1}{2RC} = \frac{\pi}{TQ}$$

$$a_n(t) = B_1 e^{-\frac{\pi}{TQ} t} \sin(\omega t + \theta)$$

letting

$$e^{-\frac{\pi}{TQ} t} = e^{-1}$$

$$\frac{\pi}{TQ} t = 1 \Rightarrow t = \frac{TQ}{\pi} \text{ or } \frac{Q}{\pi} \text{ cycles is the}$$


time constant of decay

If we say that 4% is the vanishing point


$0.04 \approx e^{-\pi} \Rightarrow Q$ gives us the no. of cycles of ringing - A useful tool in estimating Q from the impulse response

1-10-2003

⑥

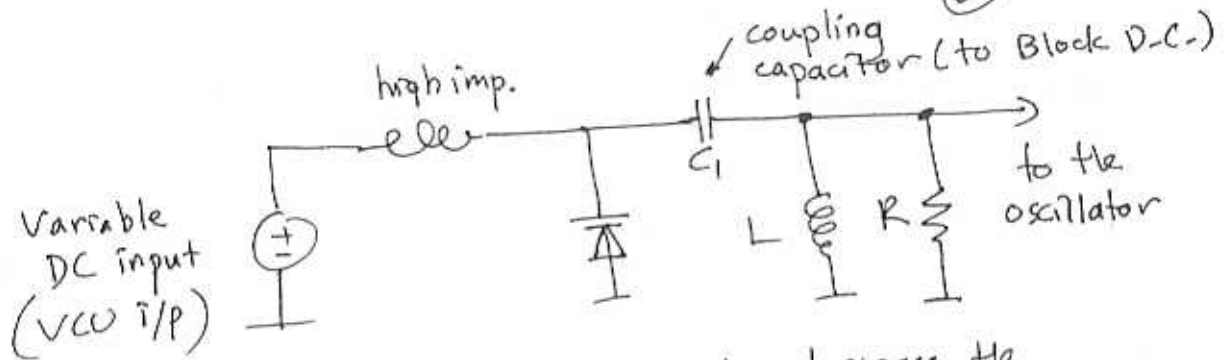

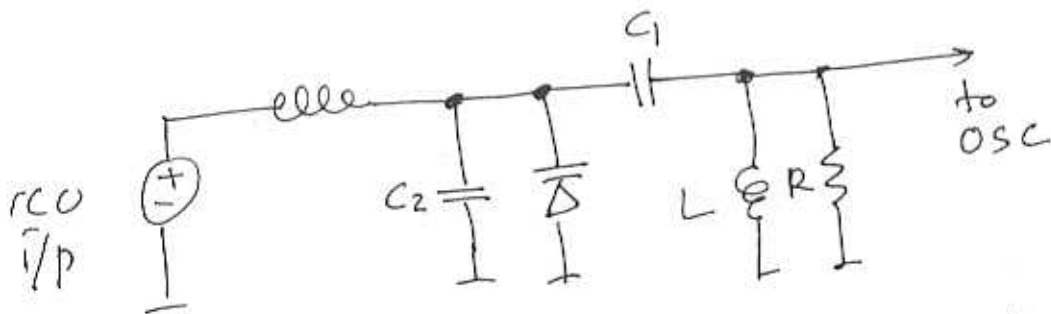Sometimes C_1 is used to decrease the capacitor range to a suitable value and also to absorb some of the voltage on the varactor to limit the AC voltage on the varactor. A more practical circuit is



Suitable values of C_1 & C_2 maps the varactor range to the required capacitor range whilst manipulating the A-C swing on the varactor to minimize the effects of the nonlinearity of the varactor.

L10, 2003

(6A)

Example:

Design a VCO (voltage controlled oscillator) tank circuit centered at 100 MHz using a 3-20 pF varactor diode (Centered means the geometric mean of the lowest & highest frequencies). The Q of the circuit must at least be 100. Find L & the minimum parallel resistance of the tank and draw the circuit.

$$\omega_{\text{low}} = \frac{1}{\sqrt{C_{\text{high}} L}} \quad , \quad \omega_{\text{high}} = \frac{1}{\sqrt{C_{\text{low}} L}}$$

$$\omega_{\text{low}} \times \omega_{\text{high}} = \omega_{\text{midrange}}^2 = (2\pi \times 100 \times 10^6)^2 = (6.28 \times 10^8)^2$$

$$\frac{1}{\sqrt{20 \times 10^{-12} \times 3 \times 10^{-12}}} \cdot \frac{1}{L} = 3.94 \times 10^{17}$$

$$\frac{1}{160 \times 10^{-12} \times 3.94 \times 10^{17}} = L$$

$$L = \frac{1}{7.75 \times 3.94 \times 10^5} = 3.27 \times 10^{-7} = 0.327 \mu\text{H} = 327 \text{ nH}$$

$$Q = \frac{R}{\omega_0 L} = R \omega_0 C$$


$$80 = R \times 2\pi \times 10^8 C = \frac{R}{2\pi \times 10^8 L}$$

$$\Rightarrow R = Q \omega_0 L = 80 \times 6.28 \times 10^8 \times 0.327 \times 10^{-6} = 16,453 \Omega$$

$$\boxed{R = 16.5 \text{ k}\Omega \text{ min}}$$

1-10-2003
(7)

Series RLC networks

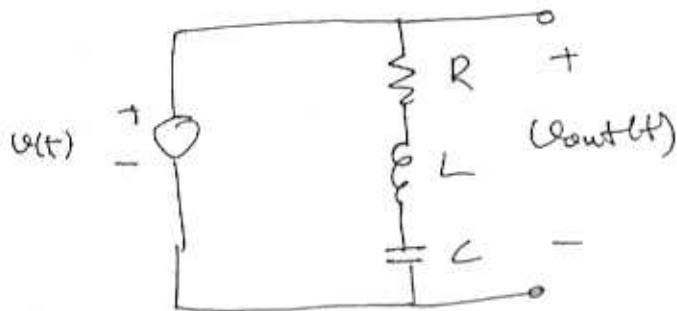

Almost the same kind of equations are used except Q is given in a different form as the dual of the parallel RLC circuit

$$Q = \frac{\sqrt{L/C}}{R} = \frac{\sqrt{L}}{R\sqrt{C}} = \frac{\sqrt{L}}{R\sqrt{C}} \times \frac{\sqrt{L}}{\sqrt{L}} = \frac{L\omega_0}{R} \leftarrow$$

$$= \frac{\sqrt{L}}{R\sqrt{C}} \cdot \frac{\sqrt{C}}{\sqrt{C}} = \frac{\sqrt{LC}}{RC} = \frac{1}{\omega_0 RC} \leftarrow$$


reciprocal of the parallel tank formulas

You can work them out if you wish to.

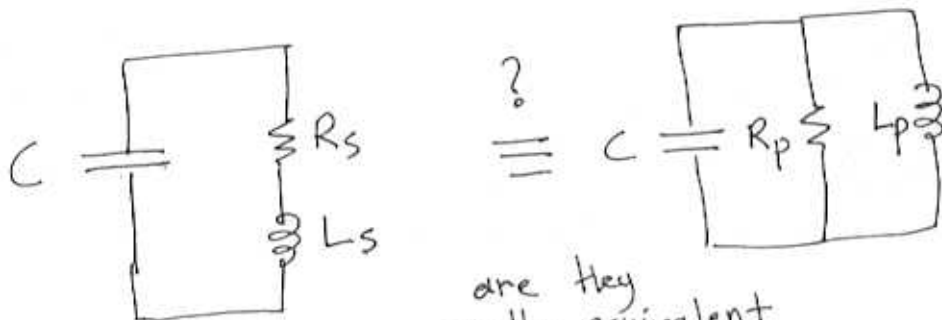1.10.2003
(8)

Other RLC circuits

How do we account for series losses of the energy storing elements.



are they
really equivalent
or
equivalent under
what condition

$$R_s + j\omega L_s = R_p // j\omega L_p = \frac{R_p j\omega L_p}{R_p + j\omega L_p}$$

$$= \frac{R_p j\omega L_p [R_p - j\omega L_p]}{R_p^2 + \omega^2 L_p^2}$$

$$R_s + j\omega L_s = \frac{\omega^2 R_p L_p^2 + j\omega L_p R_p^2}{R_p^2 + \omega^2 L_p^2}$$

equating real and imaginary parts

$$R_s = \frac{\omega^2 R_p L_p^2}{R_p^2 + \omega^2 L_p^2} \quad \text{and} \quad \omega L_s = \frac{\omega L_p R_p^2}{R_p^2 + \omega^2 L_p^2}$$

1-10-2003

(9)

$$\text{But } \frac{R_p}{\omega_0 L_p} = Q \text{ or } R_p^2 = \omega_0^2 L_p^2 Q^2$$

notice ω becomes ω_0
so at resonance when $\omega = \omega_0$

$$L_p = \frac{R_p}{\omega_0 Q}$$
$$\omega_0^2 L_p^2 = \frac{R_p^2}{Q^2}$$

$$R_s = R_p \cdot \frac{R_p^2/Q^2}{R_p^2 + R_p^2/Q^2}$$

$$R_s = R_p \cdot \frac{1}{Q^2} \cdot \frac{1}{1 + \frac{1}{Q^2}} = R_p \frac{1}{Q^2 + 1}$$

$$R_s (Q^2 + 1) = R_p$$

and

$$\omega L_s = \frac{\omega L_p R_p^2}{R_p^2 + \omega^2 L_p^2} = \omega L_p \frac{R_p^2}{R_p^2 + \frac{R_p^2}{Q^2}}$$

$$L_s = L_p \frac{1}{1 + \frac{1}{Q^2}} = L_p \frac{Q^2}{Q^2 + 1}$$


$$L_s \frac{Q^2 + 1}{Q^2} = L_p$$

inductance changes slightly and
series resistance is multiplied by $Q^2 + 1$
to be transformed to parallel
... to same Q

Example 1

let $\omega = 10^9$ $Q = 40$

$\frac{1-10.2003}{(10)}$

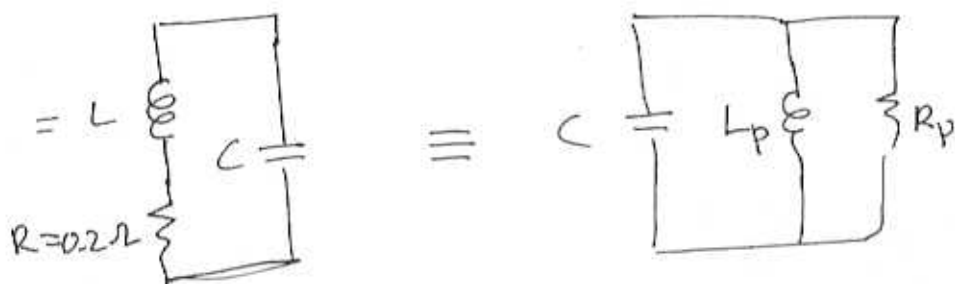

$$R_p = R_s (Q^2 + 1) = 0.2 \times (40^2 + 1) = 0.2 \times 1601 \\ \approx 320 \Omega$$

$$L_s = 10 \text{ nH} \quad \omega^2 = \frac{1}{LC} \quad C = \frac{1}{\omega^2 L} = 100 \text{ pF}$$

$$L_p = L_s \frac{Q^2 + 1}{Q} = 10.00625$$

Talk about the effective series resistance of a capacitor


Example 2

Impedance transformation

$$R_p = 50 \Omega, \quad R_s = 10 \Omega, \quad f_0 = 10 \text{ MHz}$$

Find L & C such that R_s is transformed to parallel load R_p
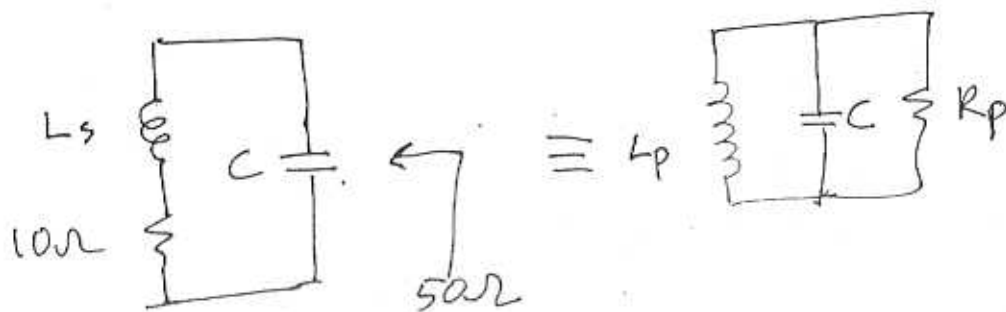
$$Q^2 + 1 = \frac{R_p}{R_s} = 5 \Rightarrow Q^2 = 4, \quad Q = 2$$



1.10.2003
(11)

$$Q = \frac{\omega_0 L}{R_s} \quad \text{series circuit}$$

$$2 = \frac{2\pi \times 10^7}{10 \Omega} L \Rightarrow L = \frac{2 \times 10}{2 \times \pi \times 10^7}$$

$$L = \frac{1}{\pi \times 10^6} = \frac{10^{-6}}{\pi} \approx 3.18 \times 10^{-7} = 318 \text{ nH}$$

$$Q = \omega_0 R_p C = 2\pi \times 10^7 \times 50 \times C \Rightarrow$$

$$C = \frac{Q}{2\pi \times 10^7 \times 50} = \frac{2}{2\pi \times 10^7 \times 50} = 6.36 \times 10^{-10} \text{ F}$$

$$C = 636 \text{ pF}$$


1.10.2003

(12)

Maximum power transfer

The correct question is

$$Z_s = R_s + jX_s$$

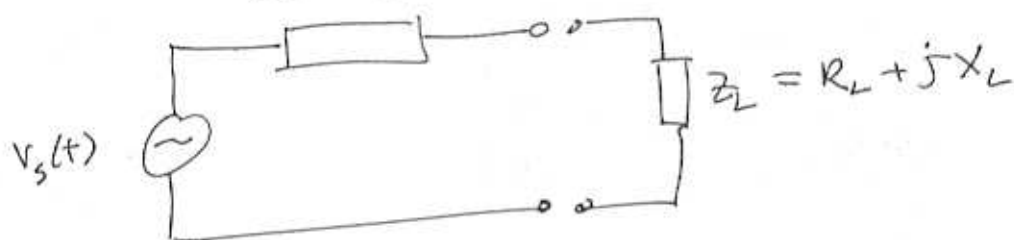

Find Z_L such that maximum power is transferred to the load for a given Z_s .
The opposite is not true.

$$P_{R_L} = \frac{|V_{R_L}|^2}{R_L} = \frac{R_L |V_s|^2}{(R_L + R_s)^2 + (X_L + X_s)^2}$$

obviously $X_L + X_s = 0$ is the optimum
find the maximum by finding the derivative
of the dissipated power by R_L
 $\Rightarrow R_L = R_s$ $X_s + X_L = 0$ is the
optimum solution.

~~24~~
1-10-2007
(12 A)

$$P_{R_L} = |V_s|^2 \cdot \frac{R_L}{(R_L + R_s)^2}$$

$$\frac{d P_{R_L}}{d R_L} = |V_s|^2 \left[1 \times \frac{1}{(R_L + R_s)^2} - \frac{2 R_L}{(R_L + R_s)^3} \right]$$

$$\frac{(R_L + R_s) - 2 R_L}{(R_L + R_s)^3} = 0$$

$$R_L + R_s = 2 R_L$$


$$\boxed{R_s = R_L}$$

1-10-2003

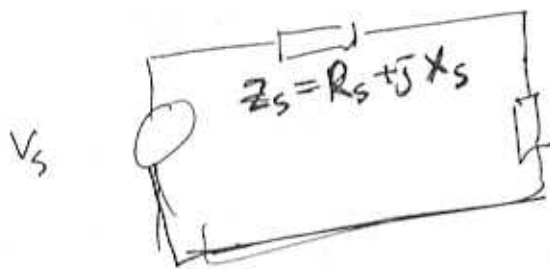(13)

The wrong question 13

Find the optimum source resistance R_s for a given R_L for maximum power transfer



The optimum solution is naturally!

$$X_L + X_s = 0 \text{ and } R_s = 0!$$

The reason we use $R_s = R_L$ is that we use





$$R_s = R_L = R_{\text{characteristic}}$$

to prevent reflections and mismatch when a transmission line is involved.

The Π Match

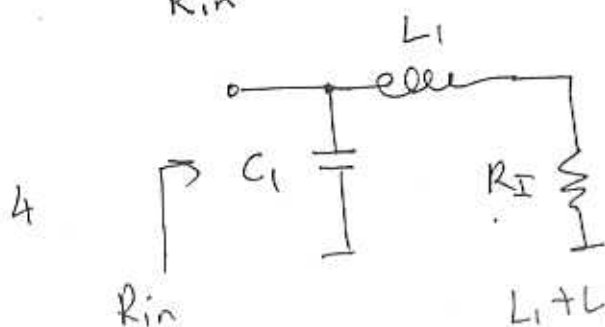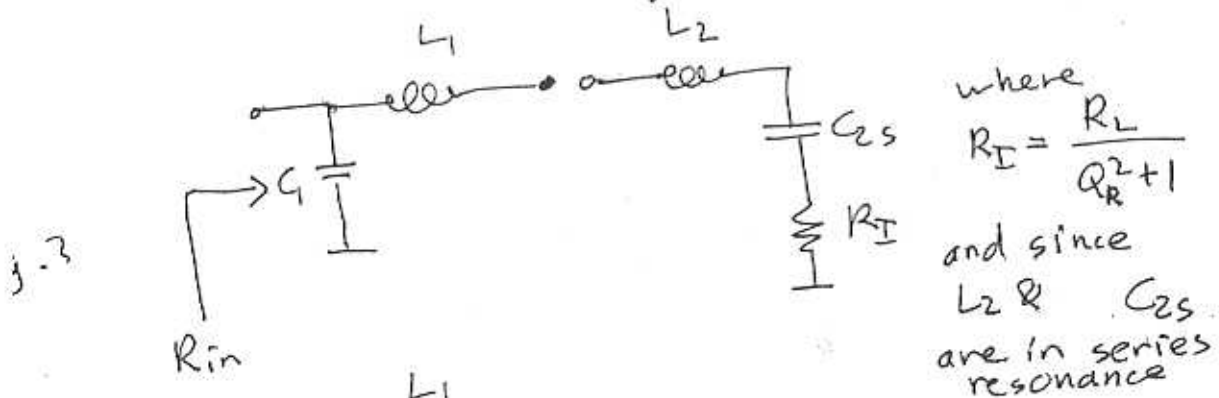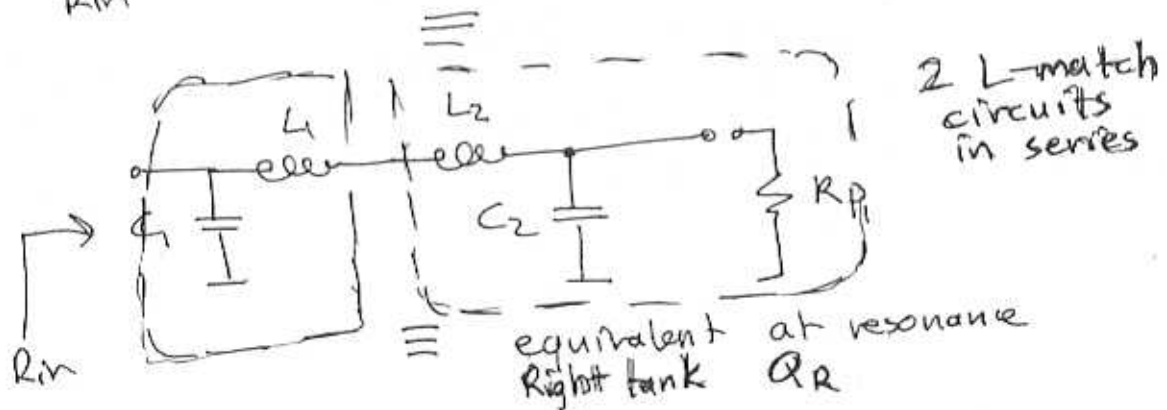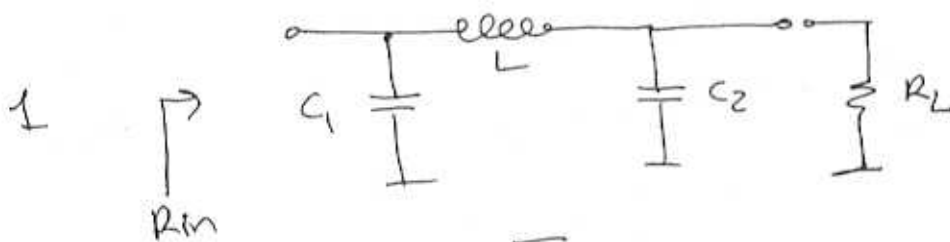8.10.03
①

In order to be able to choose the transformation ratio and the Q of the Π -Match independently, we can combine 2 L-Match circuits to arrive at an Π -match circuit



$$R_{in} = R_I (Q_L^2 + 1)$$

back to parallel again

Please note that here the only lossy element is R_L !!!

$L_1 + L_2 = L_T$

8.10.03
(02)

Q_L is given by

$$Q_L = \omega_0 C_1 R_{in} = \frac{\omega_0 L_1}{R_I}$$

$$Q_R = \omega_0 C_2 R_L = \frac{\omega_0 L_2}{R_I}$$

$$Q_{Total} = \frac{\omega_0 (L_1 + L_2)}{R_I} \quad \text{from Figure 3}$$

Here it must be emphasized that R_{in} is the impedance from the terminals of R_{in} , i.e.

Q_{Total} is the Q of the circuit driven by an ideal current source. When talking about the Q of a circuit driven by a ~~source~~ like source must also be taken into account. If the loss of the inductor L_I is represented by R_{Loss} (series loss) and letting

$$R_I' = R_I + R_{Loss}$$

R_{in} becomes

$$R_{in} = (R_I + R_{Loss}) (Q_L^2 + 1)$$

$$\text{where } Q_L = \frac{\omega_0 L_1}{R_I + R_{Loss}}$$

8-10.03
(3)

$$Q_T = Q_L + Q_R = \frac{\omega(L_1 + L_2)}{R_I}$$
$$= \sqrt{\frac{R_{in}}{R_I} - 1} + \sqrt{\frac{R_L}{R_I} - 1}$$

To attack a design problem where typically R_{in} , R_L is known and Q is calculated from the BW of the match, find R_I first. Finding R_I from the equation R_I first requires either iteration or high Q assumption.
or look,

But actually the problem has an analytical solution. $\rightarrow$ look at the note on π -Match calculation.

8-10-2003

A-(1)

Π match design example

$$R_{in} = 50\Omega \quad R_s = 10\Omega \quad f_0 = 10\text{MHz}$$

$$Q = 30$$

$$Q = \frac{X_L}{R_E} \Rightarrow R_E = \frac{X_L}{Q} \quad \text{if you find } R_E \text{ then } Q_E \text{ \& } Q_L$$

problem is solved.


$$Q_R = \frac{[Q^2 K + 2K - K^2 - 1]^{\frac{1}{2}} - Q}{K - 1} \quad \text{where } K = \frac{R_{in}}{R_L} = \frac{50}{10} = 5$$

$$Q_R = \frac{[30^2 \times 5 + 10 - 25 - 1]^{\frac{1}{2}} - 30}{4} = \frac{66.96 - 30}{4} = 9.24$$

$$Q_L = 30 - 9.24 = 20.76$$

$$R_E (Q_R^2 + 1) = R_L$$
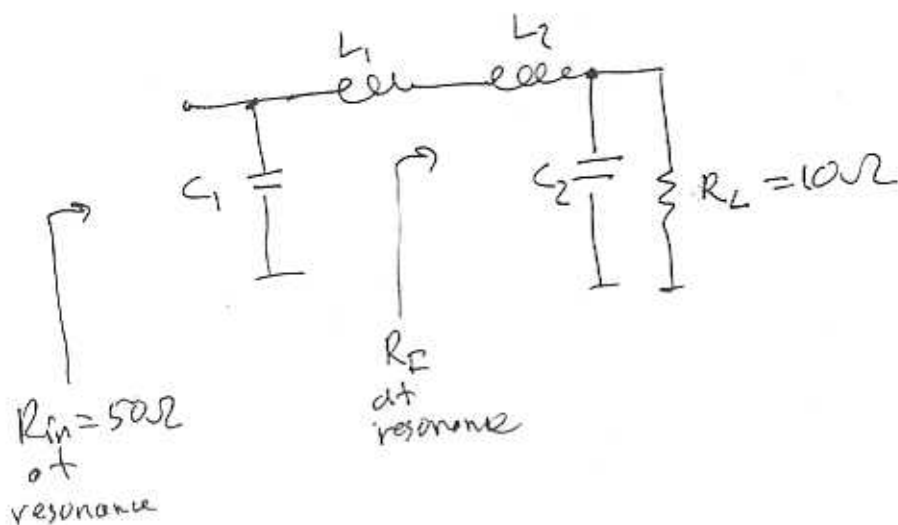
$$\frac{R_L}{(Q_R^2 + 1)} = R_E = \frac{10}{9.24^2 + 1} = 0.1157\Omega$$



8-10-2003
A-2

$$X_L = R_{\text{all}} \times Q = 3.473 \Omega$$

$$Q_L = \omega C_1 R_1 = \frac{R_{\text{in}}}{-X_{C1}}$$

$$X_{C1} = \frac{R_{\text{in}}}{-Q_L} = \frac{50}{-20.76} = -2.41$$

$$X_{C2} = \frac{R_L}{-Q_R} = \frac{10}{-9.24} = -1.082$$

I have not used the frequency yet. I just found the reactances for a π -match. I now calculate component values by

$$\omega L_{\text{Total}} = 3.473 \Omega \quad \text{by letting } \omega = 2\pi f = 62.8 \times 10^6 \text{ rad/sec}$$


$$L = 5.53 \times 10^{-9} \text{ H} = 5.53 \text{ nH}$$

$$\frac{1}{C_1 \omega} = -X_{C1} \quad C_1 = \frac{-1}{X_{C1} \omega} = 6.61 \times 10^{-9} \text{ F} = 6.61 \text{ nF}$$

$$C_2 = \frac{-1}{X_{C2} \omega} = 1.47 \times 10^{-9} \text{ F} = 1.47 \text{ nF}$$

8-10-2003
A-3

Assume we need a high pass π -match

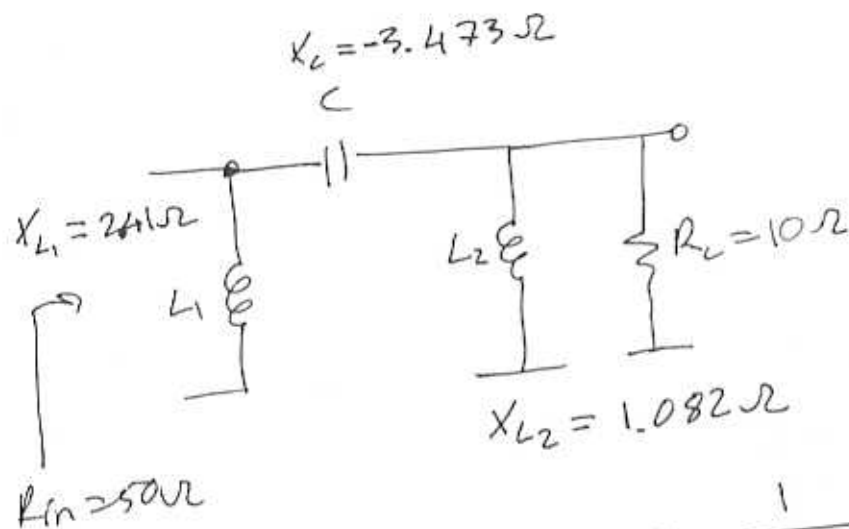


$$\frac{1}{\omega C} = -3.473 \Omega \Rightarrow C = \frac{1}{3.473 \times \omega} = 4.58 \times 10^{-9} \text{ F}$$

$$C = 4.58 \text{ nF}$$

$$\omega L_1 = 2.41 \Omega \Rightarrow L_1 = \frac{2.41}{\omega} = 3.84 \times 10^{-8} \text{ H} = 38.4 \text{ nH}$$

$$\omega L_2 = 1.082 \Omega \Rightarrow L_2 = \frac{1.082}{\omega} = 1.72 \times 10^{-8} \text{ H} = 17.2 \text{ nH}$$

Therefore the matching circuit is

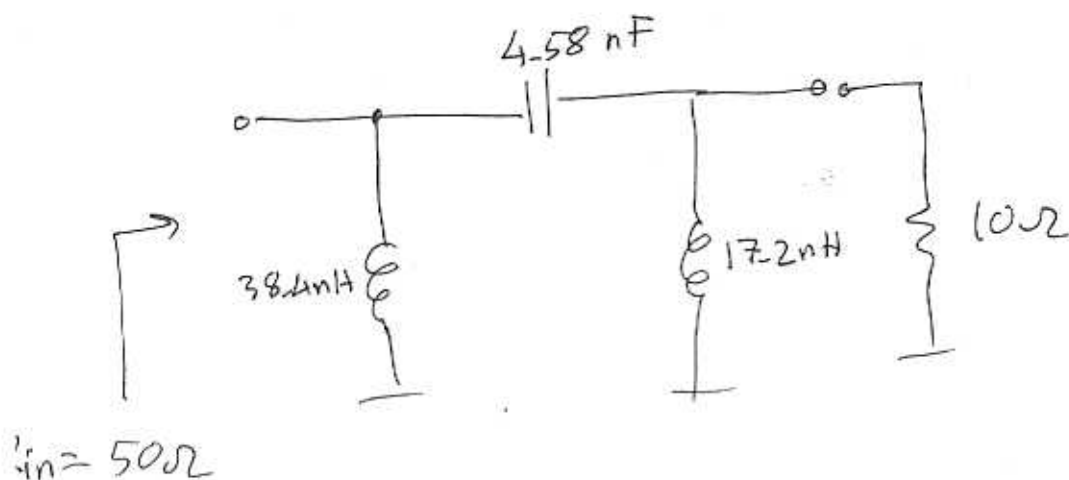

8.10.2003

A-4

Here we must note that:

(1.) C_1 & L_1 are in resonance at ω_0

$$\frac{1}{(C_1 L_1)^{1/2}} =$$

$$\frac{\omega_0 L_1}{R_1} = Q_L \rightarrow L = \frac{Q_L R_1}{\omega_0} = \frac{20.76 \times 0.1157}{62.8 \times 10^6}$$

$$L_1 = 3.825 \times 10^{-8} \text{ H} = 38.25 \text{ nH}$$

$$\omega_0 = \frac{1}{(C_1 L_1)^{1/2}} = 62.9 \text{ Mrad/sec} \checkmark$$

$$L_2 = L_T - L_1 = 55.3 - 38.25 = 17.05 \text{ nH}$$

(2.) L_2 and C_2 series is in resonance

$$C_{\text{series}} = C_p \frac{Q^2 + 1}{Q}$$

$$C_{2\text{series}} = 14.7 \times \frac{Q_R^2 + 1}{Q_R^2} = 14.7 \times \frac{9.25^2 + 1}{9.25^2}$$

$$= 14.87 \text{ nF}$$

$$\omega_0 = 62.8 \text{ Mrad/sec}$$

30 Note that C_1 series $C_{2\text{series}}$ and L_T is in resonance:

$$C_{\text{eq}} = \frac{C_1 \times C_{2\text{ser}}}{C_1 + C_{2\text{ser}}} = 4.576 \text{ nF}$$

8.10.2003
A-5

$$\omega_0 = \frac{1}{C_{eq} \times L_T} = \frac{1}{(4.576 \times 10^{-9} \times 55.3 \times 10^{-9})^{1/2}}$$
$$= 62.86 \text{ M rad/sec}$$


26.9.2005

L-match - 1

L-Match

Match a load into the source (both resistive) using a tank circuit.

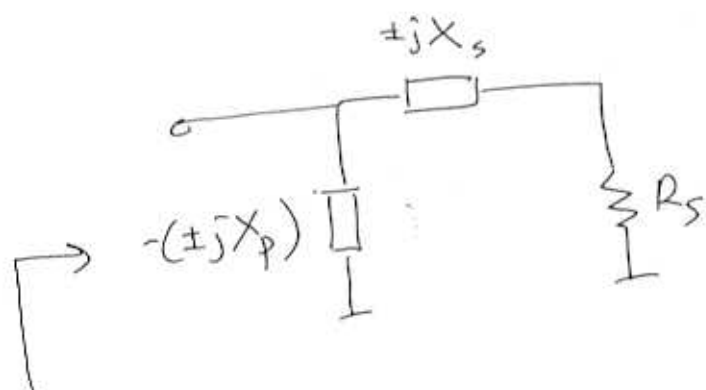Using the parallel-to-series transformation



R_p always higher than R_s for $Q > 1$

$$Q_s = \frac{X_s}{R_s} = \frac{R_p}{X_p} = Q_p = Q$$

$$R_p = (Q^2 + 1)R_s \Rightarrow \frac{R_p}{R_s} - 1 = Q^2$$

$\Rightarrow Q$ is determined by the transformation ratio.

26.9.2005

L-match -2

$$\left. \begin{aligned} \frac{X_s}{R_s} = Q &\Rightarrow X_s = Q \cdot R_s \\ \frac{R_p}{X_p} = Q &\Rightarrow X_p = \frac{R_p}{Q} \end{aligned} \right\} \Rightarrow X_s \cdot X_p = \cancel{Q} \cdot \frac{R_s \cdot R_p}{\cancel{Q}} \quad \text{or}$$

$$\Rightarrow \frac{X_s}{R_s} = Q = Q = \frac{R_p}{X_p} \Rightarrow \text{all is determined}$$

only one ^{series} reactance & one parallel reactance
for a given set of R_p , R_s & Q

Example: a) Match

75 Ω into a 15 Ω driven

b-) Find component values for a highpass circuit
with $f = 1 \text{ MHz}$

c-) Find component values for a lowpass
circuit with $f = 20 \text{ GHz}$

d-) Find the loaded Q when driven by a 75 Ω source
and a 15 Ω load.

Solution


$$a-) Q^2 + 1 = \frac{75}{15} = 5 \Rightarrow Q = 2$$

$$X_s = 2 \times R_s = 2 \times 15 = 30 \Omega$$

$$X_p = \frac{R_p}{Q} = \frac{75}{2} = 37.5 \Omega$$

26.9.2006
L-match - 3

b-) High pass

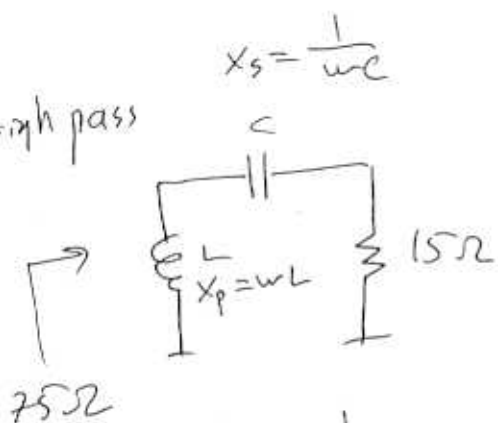


$$\omega = 6.28 \times 10^6$$

$$X_s = 30 = \frac{1}{\omega C} \Rightarrow C = \frac{1}{X_s \omega} = 5.307 \times 10^{-9} \text{ F}$$

$$X_p = 37.5 = \omega L \Rightarrow L = \frac{X_p}{\omega} = \frac{37.5}{\omega} = 5.97 \times 10^{-6} \text{ H}$$


c-) Low pass

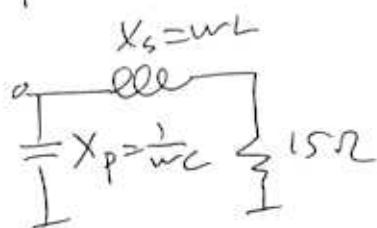

$$X_s = 30 = \omega L \Rightarrow L = \frac{30}{\omega} = 2.388 \times 10^{-10} \text{ H}$$

$$X_p = \frac{1}{\omega C} \Rightarrow C = \frac{1}{X_p \omega} = \frac{1}{37.5 \omega} = 2.12 \times 10^{-13} \text{ F}$$

d-)

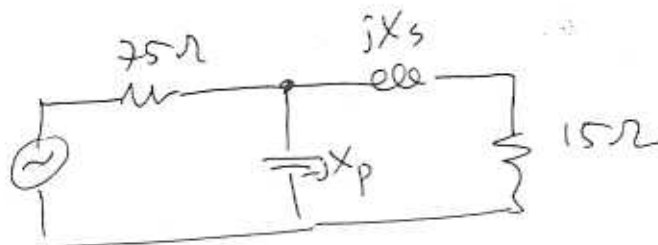

$$Q_{\text{loaded}} = \frac{Q_{\text{match}}}{2} = \frac{2}{1} = 1 = \frac{75 // 75}{37.5} = \frac{R_p}{X_p}$$