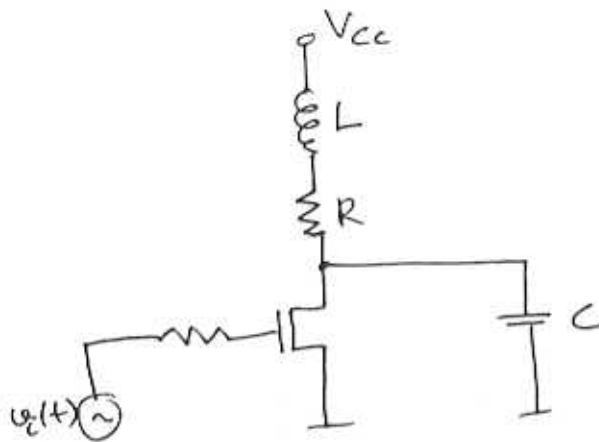


Shunt-peaked amplifier


22.10.2003
①



The o/p time constant is RC which creates a 3dB cut-off frequency $= \omega_1 = \frac{1}{2\pi RC} = \frac{1}{2\pi \tau_1}$

for $L = 0$. The question is:

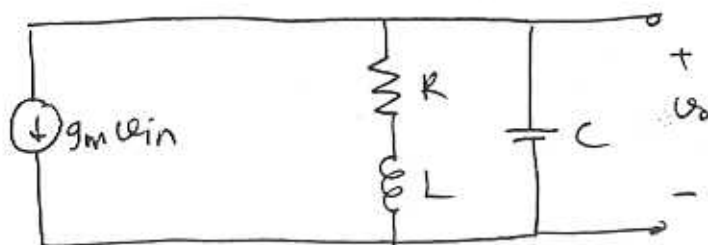
Can we extend the BW of an amplifier (ω_1) by adding an inductor L with a suitable value in series with the drain resistor R . In this proposed solution, we are creating a parallel resonant circuit with a lossy inductor driven by a current source.



22.10.2003

2

The circuit is equivalent to


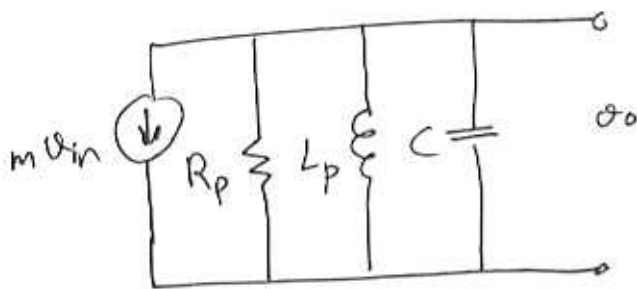


where $R_p = (Q^2 + 1)R$

$L_p = \frac{Q^2 + 1}{Q^2} L_s$ & $Q = \frac{\omega L}{R}$

which is an exact expression at any ω and only at that ω .

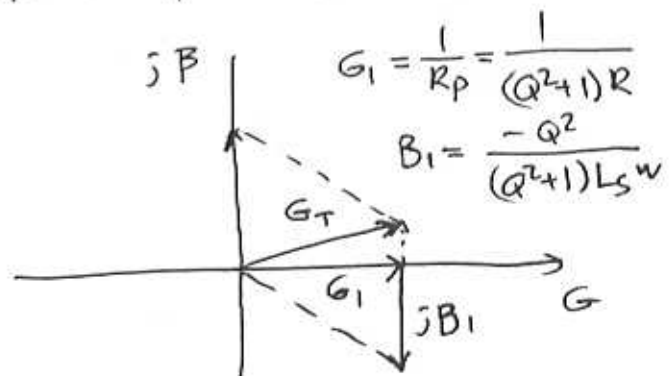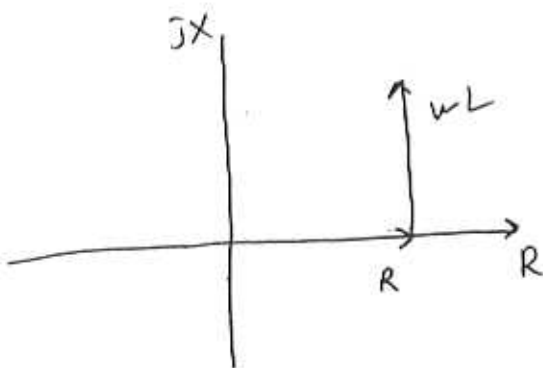If we now draw the phasor diagrams for frequencies at which R , $\frac{1}{\omega C}$ & ωL are not very much different from each other:



at frequencies approaching ω_1 or going beyond it (i.e. the value of $\frac{1}{\omega C}$ being not very much different from R) a value of L can be chosen such that jB_1 compensates $j\omega C$ to some extent, which results at a value of $G_1 < \frac{1}{R}$ (because $Q > 0$) and therefore creating an overall impedance greater than the impedance of the output load without L (maybe perhaps greater than R). Therefore the response in the vicinity of ω_1 is increased.

22-10-2003

(3)

This is a low Q circuit, therefore exact derivation is required.

$$Z(j\omega) = (R + j\omega L) \parallel \frac{1}{j\omega C} = \frac{(R + j\omega L) \frac{1}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}}$$

$$= \frac{R + j\omega L}{1 + j\omega RC - \omega^2 LC} = R \left(\frac{1 + j\omega L/R}{1 - \omega^2 LC + j\omega RC} \right)$$

$$\frac{Z(j\omega)}{R} = \frac{1 + j\omega \left(\frac{L}{R} \right)}{(1 - \omega^2 LC) + j\omega RC}$$

Let $\tau = \frac{L}{R}$, $\tau_c = RC = \frac{1}{\omega_1}$

$$m = \frac{\tau_c}{\tau} = \frac{RC}{L/R} = \frac{1}{\omega_1 \tau} = \frac{R^2 C}{L} = \frac{R^2 C}{L}$$

$$\Rightarrow L = \tau R, C = \frac{m\tau}{R} \Rightarrow LC = \tau R \frac{m\tau}{R} = m\tau^2 = m \frac{1}{\omega_1^2 \tau^2}$$

and $\tau = \frac{1}{m\omega_1} = \frac{L}{R}$

$$LC = \frac{1}{m\omega_1^2}$$

$$\Rightarrow \left| \frac{Z(j\omega)}{R} \right| \text{ becomes}$$

$$\frac{|Z(j\omega)|}{R} = \left[\frac{1 + (\omega\tau)^2}{(1 - \omega^2 \tau^2 m)^2 + (\omega\tau m)^2} \right]^{1/2}$$

or by defining $\omega_n = \frac{\omega}{\omega_1}$

$$|G_n(j\omega)| = \frac{|Z(j\omega)|}{R} = \left[\frac{1 + \frac{\omega^2}{\omega_1^2 m^2}}{\left(1 - \frac{\omega^2}{m\omega_1^2}\right)^2 + \frac{\omega^2}{\omega_1^2}} \right]^{1/2} = \left[\frac{1 + \frac{\omega_n^2}{m^2}}{\left(1 - \frac{\omega_n^2}{m}\right)^2 + \omega_n^2} \right]^{1/2}$$

by defining this ratio as $G_n(j\omega)$

22.10.2003

(4)

We are now trying to find the new 3dB point with the introduced L. Therefore we can find the bandwidth extension ratio w_n by equating

$$|G_n(jw_n)| \text{ to } \frac{1}{\sqrt{2}} \text{ or } |G_n(jw_n)|^2 = \frac{1}{2} \text{ and}$$

solving for w_n taking m as the parameter defining the ratio of time constants

$$m = \frac{\tau_c}{\tau} = \frac{w_L}{w_i} \text{ where } w_i = \frac{1}{RC} \text{ \& } w_L = \tau = \frac{L}{R}$$

or the ratio of the cut-off frequencies.

$$\frac{1}{2} = \frac{1 + \frac{w_{n3}^2}{m^2}}{\left(1 - \frac{w_{n3}^2}{m}\right)^2 + w_{n3}^2}$$

where w_{n3} is the 3dB point of the normalized frequency or the bandwidth extension ratio

letting $d = w_{n3}^2$

$$\frac{1}{2} = \frac{1 + \frac{d}{m^2}}{\left(1 - \frac{d}{m}\right)^2 + d} \Rightarrow 1 - 2\frac{d}{m} + \frac{d^2}{m^2} + d = 2 + \frac{2d}{m^2}$$

$$\underbrace{\frac{d^2}{m^2}}_a + d \underbrace{\left[1 - \frac{2}{m} - \frac{2}{m^2}\right]}_b \underbrace{- 1}_c = 0$$

$$w_{n3}^2 = d_{1,2} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} = -\frac{m^2 - 2m - 2}{2} \pm \sqrt{\frac{(m^2 - 2m - 2)^2}{4} + \frac{4m^2}{4}}$$


22.10.2003

(5)

$$\frac{\omega_{3db}}{\omega_1} = \omega_{n3} = \left[-\frac{m^2}{2} + m + 1 + \sqrt{\left(-\frac{m^2}{2} + m + 1\right)^2 + m^2} \right]^{1/2}$$


where ω_{3db} is the 3dB radial frequency.
we take only the positive quadratic since the negative one results at a negative frequency.

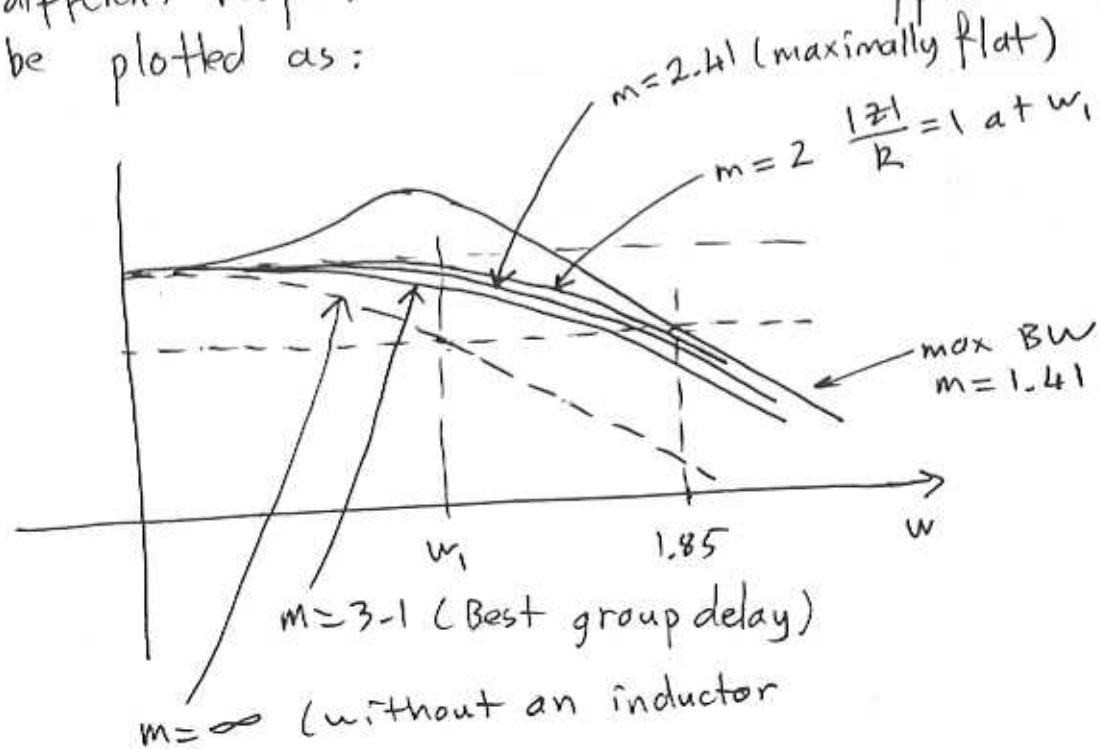For different values of the index m , we get different response curves which can approximately be plotted as:



22.10.2003

(6)

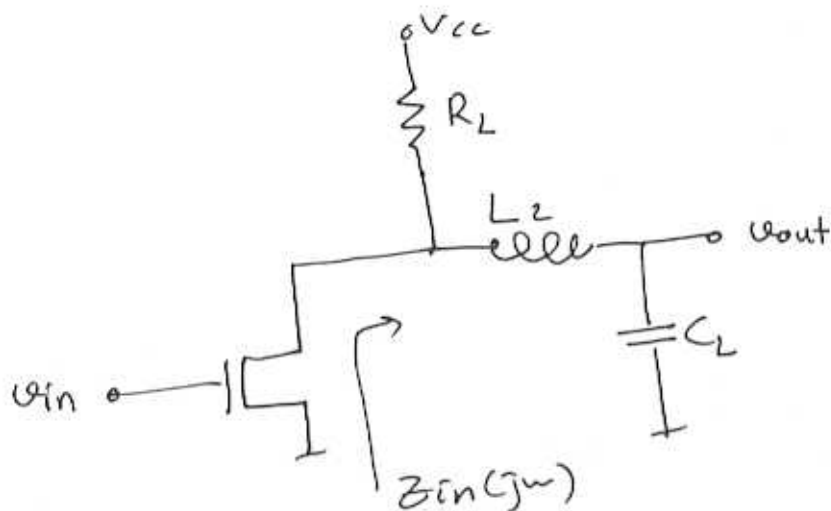Series Peaking

$$\text{Gain}(j\omega) = Z_{in}(j\omega) \cdot \frac{Z_L}{Z_C + Z_L} = G(j\omega)$$

$$= \left[\left(j\omega L_2 + \frac{1}{j\omega C_L} \right) \parallel R_L \right] \times \frac{Z_C}{Z_C + Z_L}$$

$$= \frac{R_L \left[j\omega L_2 + \frac{1}{j\omega C_L} \right]}{R_L + j\omega L_2 + \frac{1}{j\omega C_L}} \cdot \frac{\frac{1}{j\omega C_L}}{\left[j\omega L_2 + \frac{1}{j\omega C_L} \right]}$$

$$\frac{G(j\omega)}{R_L} = \frac{1}{(1 - \omega^2 L_2 C_L) + j\omega R_L C_L}$$

$$\text{Letting } \omega_1 = \frac{1}{R_L C_L}, \quad m = \frac{\tau_C}{\tau} = \frac{R_C}{L/R}$$

$$\gamma = \frac{L_2}{R_L} \quad \tau_C = R_L C_L = \frac{1}{\omega_1} \quad \text{again}$$

$$L_2 C_L = \frac{1}{m \omega_1^2} \quad \text{and} \quad R_L C_L = \frac{1}{\omega_1} \quad \text{are obtained}$$

22-10-2003

(7)

defining $G_n(j\omega) = \frac{G(j\omega)}{R_L}$, it becomes

$$G_n(j\omega) = \frac{1}{\left(1 - \frac{\omega^2}{\omega_1^2 m}\right) + j\frac{\omega}{\omega_1}} = \frac{1}{\left(1 - \frac{\omega_n^2}{m}\right) + j\omega_n}$$

where $\omega_n = \frac{\omega}{\omega_1}$

$$|G_n(j\omega)|^2 = \frac{1}{\left(1 - \frac{\omega_n^2}{m}\right)^2 + \omega_n^2} = \frac{1}{1 - 2\frac{\omega_n^2}{m} + \frac{\omega_n^4}{m^2} + \omega_n^2}$$

at the 3dB point $|G_n(j\omega)|^2 = \frac{1}{2} \Rightarrow$

$$\frac{1}{2} = 1 - \omega_n^2 \left(1 - \frac{2}{m}\right) + \frac{\omega_n^4}{m^2} \quad \text{letting } \omega_n^2 = d$$

$$\frac{1}{m^2} d^2 + \left(1 - \frac{2}{m}\right) d - 1 = 0 \Rightarrow \underbrace{d^2 + d(m^2 - 2m) - m^2}_{a=1 \quad b=m^2-2m \quad c=-m^2} = 0$$

$$d_{1,2} = -\frac{b}{2a} \pm \sqrt{\frac{b^2}{4a^2} - \frac{c}{a}} = \frac{2m - m^2}{2} \pm \sqrt{\frac{(2m - m^2)^2}{4} + m^2}$$

taking only the positive quadratic again as ω_n should be a real number (negative quadratic results in imaginary ω_n)

$$\begin{aligned} \omega_n^2 = d &= m - \frac{m^2}{2} + \sqrt{\frac{m^2(2-m)^2}{4} + \frac{4m^2}{4}} \\ &= m - \frac{m^2}{2} + \left(\frac{4m^2 - 4m^3 + m^4 + 4m^2}{4} \right)^{1/2} \\ \omega_{n3} &= d^{1/2} = \left[m - \frac{m^2}{2} + \left[\frac{8m^2 - 4m^3 + m^4}{4} \right]^{1/2} \right]^{1/2} \end{aligned}$$

22.10.2003

(8)

$$w_{n3} = \left[m - \frac{m^2}{2} + \left[2m^2 - m^3 + \frac{m^4}{4} \right]^{1/2} \right]^{1/2}$$


$$\text{for } m=2 \Rightarrow w_{n3} = \sqrt{2}$$

$$\text{for } m=3 \Rightarrow w_{n3} = 1.36165$$


18.10.2005

①

There are other peaking arrangements

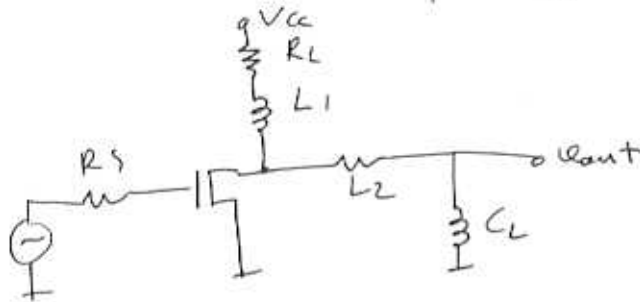

Amplifier with shunt & series peaking

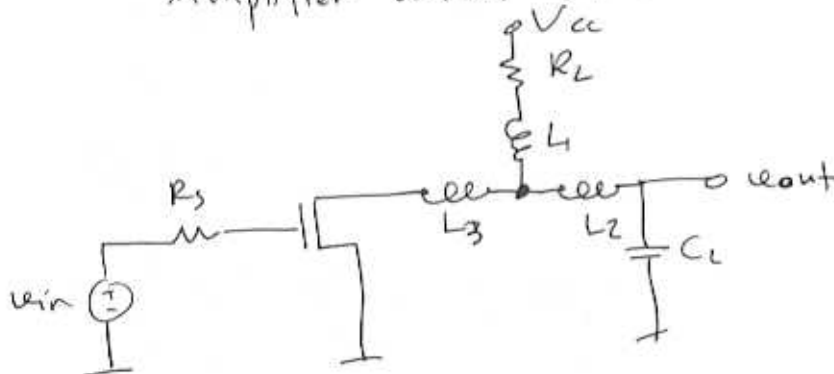


Shunt and double-series peaking

exchanges increased delay with bandwidth

$$L = \frac{R^2 C_L}{2(1+k)}$$

$$\tau_c = \frac{C_L}{4} \left[\frac{1-k}{1+k} \right]$$

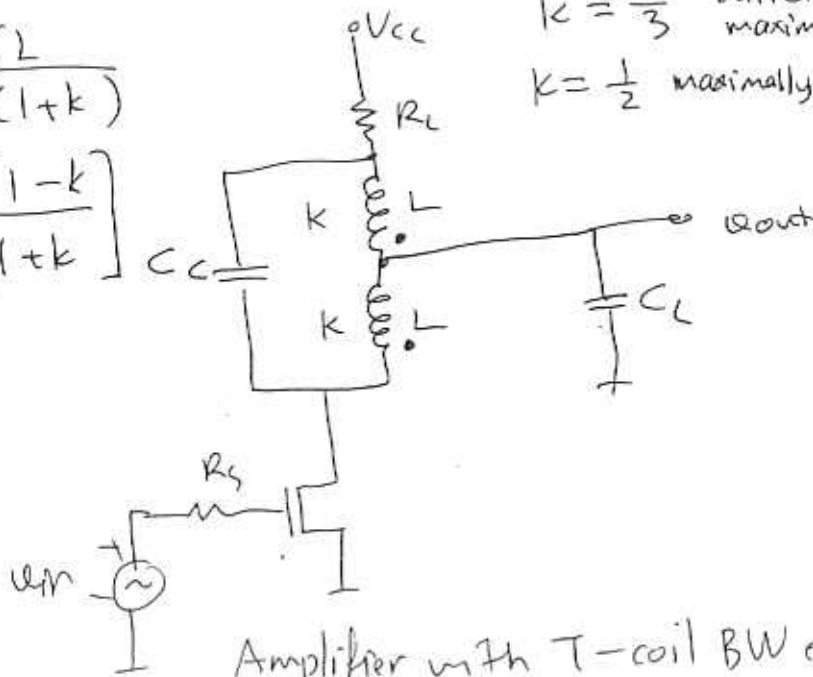$k = \frac{1}{3}$ Butterworth-type
maximally flat response
 $k = \frac{1}{2}$ maximally flat group delay



Amplifier with T-coil BW enhancement