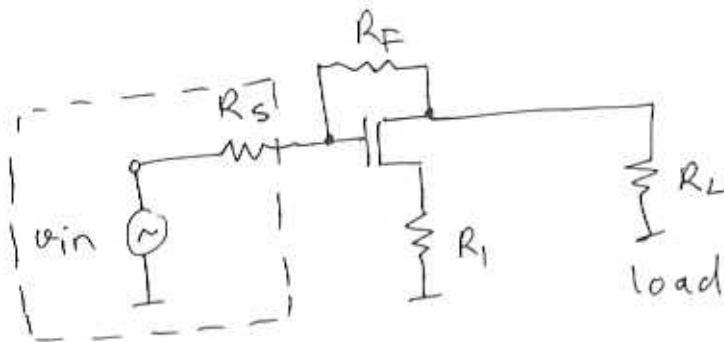


24.10.03

①

The Shunt-Series Amplifier




Source

This is an amplifier which has controlled gain and input and output impedances. At low enough frequencies and if the effect of R_F is neglected, then

$$A_v \approx -\frac{R_L}{R_1} \quad (\text{open-loop gain})$$

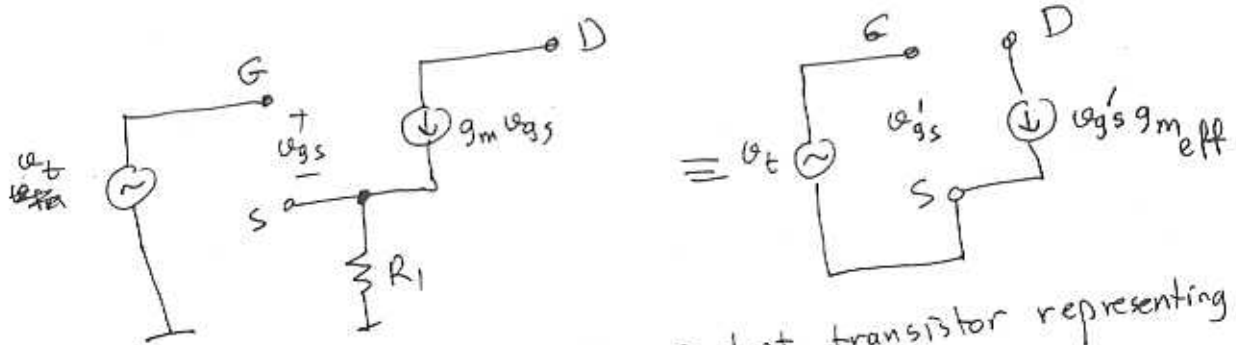But for a more precise calculation of the gain, let us first find the equivalent circuit for the source degeneration.



Can we define an equivalent transistor representing the R_1 and transistor combination.

24-10-2003

(2)



$$v_{gs} = v_t - v_s = v_t - g_m v_{gs} R_1$$

$$\Rightarrow v_{gs}(1 + g_m R_1) = v_t \Rightarrow i_o = g_m v_{gs} = v_t \frac{g_m}{1 + g_m R_1}$$

Therefore we can replace the transistor with an source degeneration resistor R_1 by another transistor with transconductance equal to

$$\boxed{\frac{g_m}{g_m R_1 + 1} = g_{m_{eff}}}$$

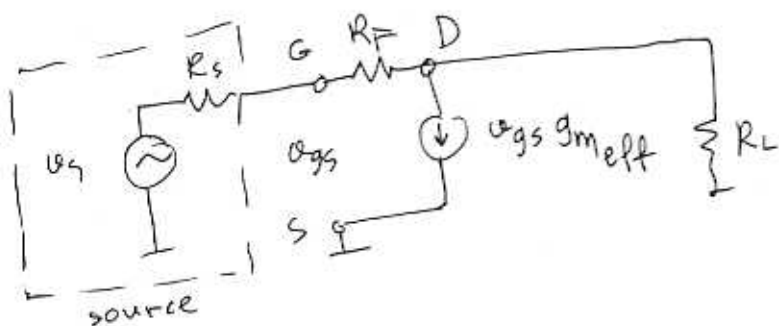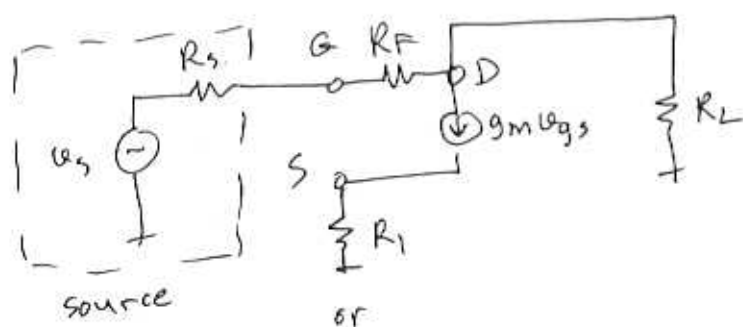The small signal equivalent circuit of the shunt-series amplifier is:




where $g_{m_{eff}} = \frac{g_m}{1 + g_m R_1}$

24-10-2003

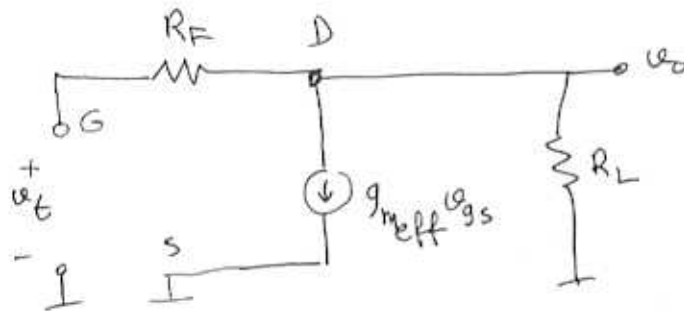(3)

If we define the gain of the amplifier as $\frac{v_o}{v_G}$, then we can draw the equivalent circuit as:



By superposition

$$v_o = v_G \frac{R_L}{R_F + R_L} - v_G \underbrace{g_{m,eff} \cdot \frac{R_F}{R_F + R_L} \cdot R_L}_{\text{load current contribution from the current source}}$$

$$A_v = \frac{v_o}{v_G} = \frac{R_L}{R_F + R_L} \left[1 - \underbrace{\frac{g_m}{1 + g_m R_1}}_{g_{m,eff}} \cdot R_F \right]$$

If we continue rearranging A_v as below:
to express A_v in terms of $-\frac{R_L}{R_1}$ times
modifying factors

24.10.2003
 (4) (20.10.2005)


$$\begin{aligned}
 A_v &= \frac{R_L}{R_F + R_L} \left[1 - \frac{g_m R_F}{1 + g_m R_1} \right] \\
 &= - \frac{R_L}{R_F + R_L} \left[\frac{g_m R_F - 1 - g_m R_1}{1 + g_m R_1} \right] \\
 &= - \frac{R_L}{R_1} \cdot \left[\frac{g_m R_F - 1 - g_m R_1}{g_m + \frac{1}{R_1}} \right] \cdot \frac{1}{R_F + R_L} \\
 &= - \frac{R_L}{R_1} \left[\frac{R_F - \frac{1}{g_m} - R_1}{1 + \frac{1}{g_m R_1}} \right] \frac{1}{R_F \left(1 + \frac{R_L}{R_F} \right)} \\
 &= - \frac{R_L}{R_1} \cdot \frac{1}{1 + \frac{1}{g_m R_1}} \cdot \frac{1}{1 + \frac{R_L}{R_F}} \left[1 - \frac{1}{g_m R_F} - \frac{R_1}{R_F} \right] \\
 &= - \frac{R_L}{R_1} \cdot \frac{1}{1 + \frac{1}{g_m R_1}} \cdot \frac{1}{1 + \frac{R_L}{R_F}} \left[1 - \frac{1 + R_1 g_m}{g_m R_F} \right] \\
 &= - \frac{R_L}{R_1} \left[\frac{1}{1 + \frac{1}{g_m R_1}} \right] \cdot \left[\frac{1}{1 + \frac{R_L}{R_F}} \right] \cdot \left[1 - \frac{1}{g_{\text{meff}} R_F} \right]
 \end{aligned}$$

all of the expressions inside the parentheses are less than one. If $\frac{1}{g_m R}$, $\frac{R_L}{R_F}$ and $\frac{1}{g_{\text{meff}} R_L}$ are much less than one, then the gain approaches $-\frac{R_L}{R_1}$

24-10-2003

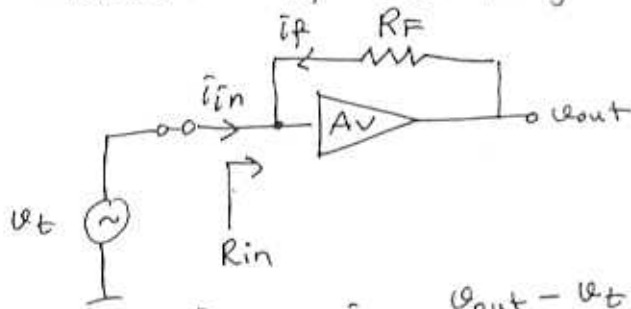(5)

In order to calculate the i/p impedance of the shunt-series amplifier, we can make use of the formula giving the input impedance of the h_{∞} input impedance amplifier with the feedback resistance R_F and the gain A_v .



$$i_{in} = -i_f = -\frac{v_{out} - v_t}{R_F} = -\frac{v_t A_v - v_t}{R_F} = v_t \frac{(1 - A_v)}{R_F}$$

$$\Rightarrow R_{in} = \frac{v_t}{i_{in}} = \frac{R_F}{1 - A_v}$$

Substituting the expression for A_v into the equ. above:

$$R_{in} = \frac{R_F}{1 - \frac{R_L}{R_F + R_L} [1 - R_F g_{m_{eff}}]} \quad \text{letting } R_E = \frac{1}{g_{m_{eff}}}$$

$$R_{in} = \frac{R_F}{1 + \frac{R_L}{R_F + R_L} \left[\frac{R_F}{R_E} - 1 \right]} = \frac{R_F}{1 + \frac{R_L [R_F - R_E]}{R_E [R_F + R_L]}}$$


$$= \frac{R_F R_E [R_F + R_L]}{R_E [R_F + R_L] + R_L [R_F - R_E]} = \frac{R_F \cdot R_E [R_F + R_L]}{R_E R_F + R_E R_L + R_L R_F - R_L R_E}$$

$$R_{in} = \frac{R_F \cdot R_E [R_F + R_L]}{R_F [R_E + R_L]} = R_E \frac{[R_F + R_L]}{[R_E + R_L]}$$

24-10-2003

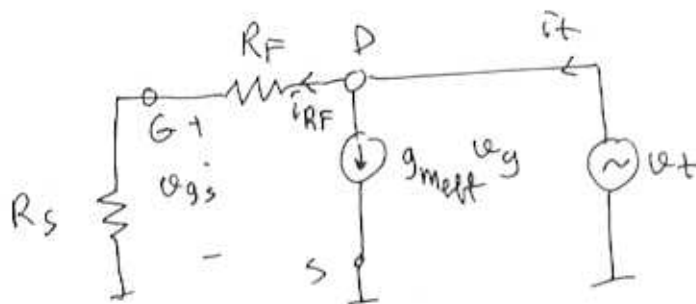(6)

In order to find the o/p impedance of the shunt-series amplifier, we connect a test source to the output



By adding i_{RF} and the current source

$$i_t = \frac{v_t}{R_F + R_S} + g_{meff} v_t \frac{R_S}{R_S + R_F} = v_t \cdot \frac{1}{R_S + R_F} [1 + R_S g_{meff}]$$

$$= v_t \frac{1 + g_{meff} R_S}{R_S + R_F} \Rightarrow$$

$$\frac{v_t}{i_t} = \frac{R_S + R_F}{1 + \frac{R_S}{R_E}} \quad \text{by } R_E = \frac{1}{g_{meff}}$$

$$= R_E \frac{R_S + R_F}{R_E + R_S}$$

24.10.2003

(7)

$$R_{in} = R_E \frac{R_F + R_L}{R_E + R_L} \text{ and } R_{out} = R_E \frac{R_F + R_S}{R_E + R_S}$$

if R_S is chosen as equal to R_L , then R_{in} becomes equal to R_D and

$$R_{in} = R_{out} = R_E \frac{R_F + R}{R_E + R} \text{ where } R_S = R_L = R$$

For designing a shunt-series amplifier the following equations are useful:

If we would like to have $R = R_S = R_L$, then:

$$R = R_E \frac{R_F + R}{R_E + R} \Rightarrow R R_E + R^2 = R_E (R_F + R)$$

$$\Rightarrow R_E (R_F + \cancel{R} - \cancel{R}) = R^2 \Rightarrow R_E = \frac{R^2}{R_F}$$

$$R_E = \frac{R^2}{R(1-A_v)} = \frac{R}{1-A_v} \text{ and } R = \frac{R_F}{1-A_v}$$

and

$$R_E = \frac{g_m R_i + 1}{g_m} \Rightarrow R_E g_m = g_m R_i + 1$$

$$\Rightarrow R_i = \frac{g_m R_E - 1}{g_m} = R_E - \frac{1}{g_m}$$

24-10-2003

7-A

Explanation of equal input & output impedances
at a shunt-series amplifier:

$$R_{in} = R_E \frac{R_F + R_L}{R_E + R_L} = R_o = R_E \frac{R_F + R_s}{R_E + R_s} = R = R_L = R_s$$

Is there a such solution?

$$R = R_E \frac{R_F + R}{R_E + R} = R_E \frac{R_F + R}{R_E + R}$$

Obviously the quotients are equal. The only requirement is to find pairs of R_E & R_F to satisfy the condition on the left.

$$\cancel{R} R_E + R^2 = R_E R_F + \cancel{R} R \Rightarrow \boxed{R_E R_F = R^2}$$

is the condition defining the pairs of R_E & R_F

24-10-2003

Design example: (shunt-series amp)

(8)

Design an amplifier with input & output impedances equal to 600Ω . The gain of the amplifier when driven by a 600Ω source and being loaded by 600Ω ohms must be 10 dB. The transconductance of the transistor to be used is 12 mS .

$$10\text{ dB} \rightarrow A_v = -10^{1/2} = -3.1622$$

$$R_i = R_E - \frac{1}{g_m} = \frac{600}{1 - A_v} - \frac{1}{g_m} = \frac{600}{4.1622} - \frac{1}{12 \times 10^{-3}}$$

$$= 144.1518 - 83.33 = 60.818\Omega$$

$$R_i = R_E - \frac{1}{g_m} = 60.818\Omega$$

Here R_i must be a positive reasonable resistor. Therefore from this equation, it can be seen if the values of R , A_v and g_m are compatible or not.

As the last step R_F can be found from

$$R_F = R(1 - A_v) = 2497.32\Omega$$


as a check R_i can be calculated from

$$R_E = \frac{R}{1 - A_v} = 144.1545 \text{ (a slight calculation error)}$$

24-10-2003

(9)

The amplifier becomes:

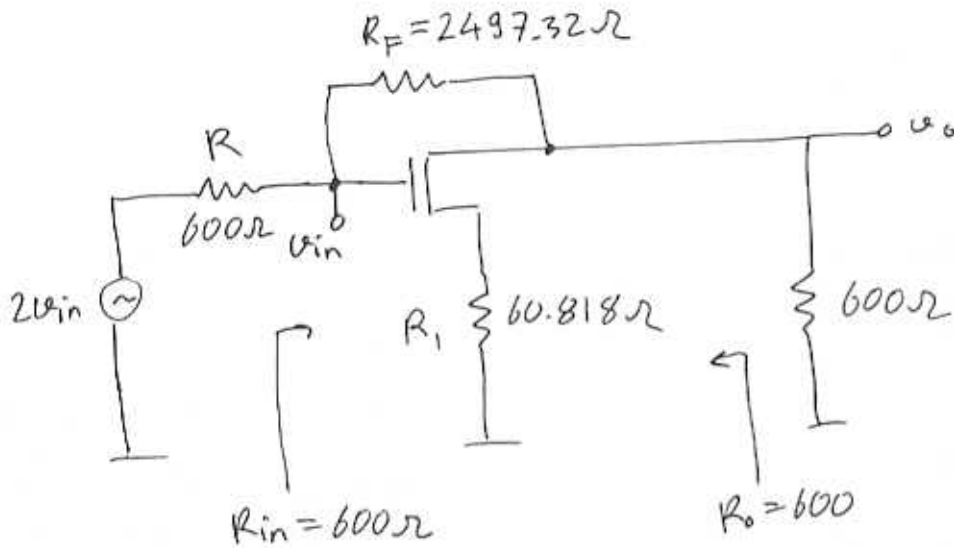

$$\frac{v_o}{v_{in}} = -3.1622 \Rightarrow 10 \text{ dB}$$

$$R_E = \frac{g_m R_i + 1}{g_m} = 144.1518 \Omega$$

$$R_{in} = R_E \frac{R_F + R}{R_E + R} = 144.1518 \frac{2497.32 + 600}{144.1518 + 600} = 600 \Omega$$

$$R_{out} = R_{in}$$


$$A_v = + \frac{R}{R_F + R} \left[1 - \frac{R_F}{R_E} \right] = -3.1622$$

$$g_m R_i = 0.72 \quad A_v = 3.16$$

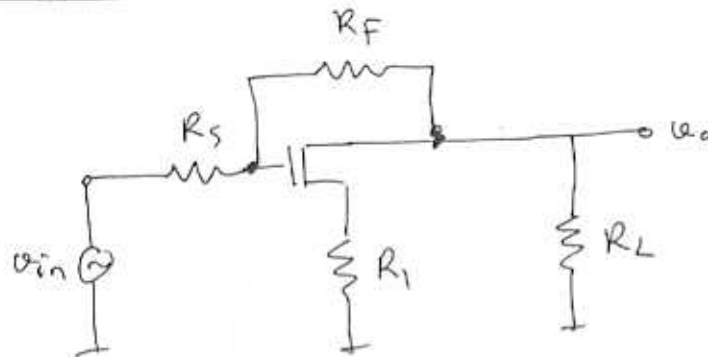
31.10.2003

①

Bandwidth, input-output impedances as a function of frequency



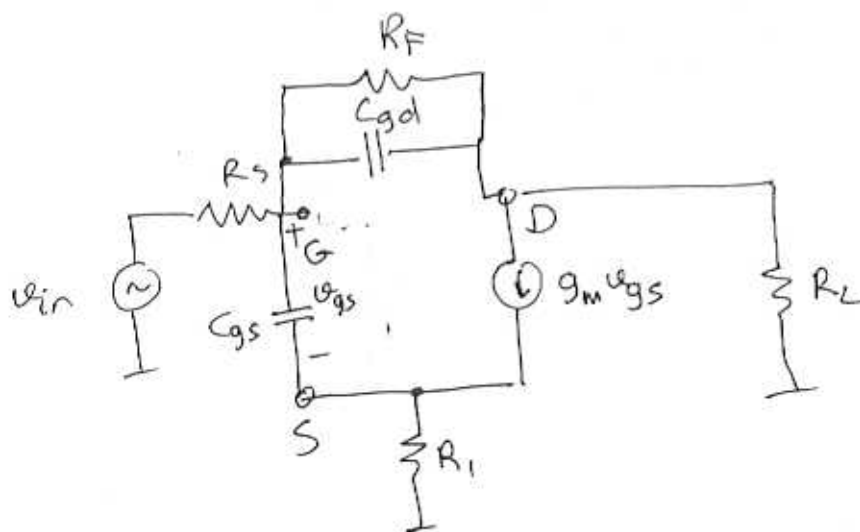The high frequency equivalent circuit of the shunt-series amplifier, if C_{gs} , C_{gd} and g_m only are taken into the model, becomes:



Since this is a low order system, $\Rightarrow$ open circuit time constants is a good estimate of the BW.
Assume $R_s = R_L = R$ as it is the usual application.

31.10.2003

(2)

The resistance facing C_{gd} is

$$R_{gd} = R_F // R_{eq} \quad \text{where}$$

$$R_{eq} = r_{left} + r_{right} + g_{m_{eff}} r_{left} r_{right} \quad \text{where } g_{m_{eff}} = \frac{g_m}{1 + g_m R_i}$$

$$R_{eq} = R + R + g_{m_{eff}} R^2 \Rightarrow$$

$$R_{gd} = R_F // R [2 + g_{m_{eff}} R]$$

$$\text{but } R_F = R_i (1 - A_v) = R (1 - A_v)$$

$$\Rightarrow R_{gd} = R (1 - A_v) // R [2 + R g_{m_{eff}}]$$

$$= R [(1 - A_v) // [2 + R \frac{g_m}{1 + g_m R_i}]]$$

$$\text{let } g_m R_i \gg 1$$

$$R_{gd} = R \left[(1 - A_v) // \left(2 + \frac{R}{R_i} \right) \right] = R [(1 - A_v) // (2 - A_v)]$$

$$\text{let } |A_v| \gg 1 \text{ and } |A_v| \gg 2$$

$$R_{gd} = -R [+A_v // A_v] = -R \frac{+A_v \times A_v}{A_v + A_v} = -R \frac{A_v^2}{2A_v}$$

$$R_{gd} \approx -R \frac{A_v}{2}$$


31.10.2003

(3)

$$R_{gd} \approx R \frac{|A_v|}{2}$$

$$\Rightarrow \tau_{gd} = C_{gd} \times R \frac{|A_v|}{2}$$

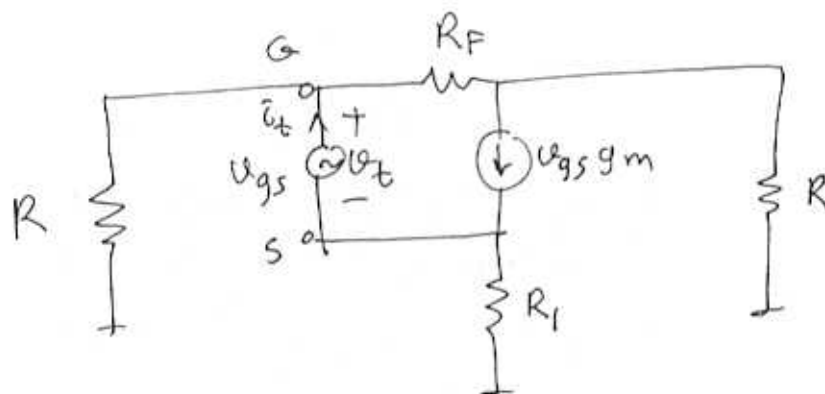In order to find R_{gs} , the circuit becomes:



We can connect a test source u_t and calculate i_t , the current passing through the source and then calculate R_{in} by

$$R_{in} = \frac{u_t}{i_t}$$

In order to find it we can use superposition to find the effects of u_t and $u_{gs}g_m = u_t g_m$


The contribution by u_t is given by

$$\begin{aligned} i_{g,t} &= u_t \times \frac{1}{L[(R_F + R) \parallel R] + R_1} = u_t \frac{1}{\frac{(R_F + R)R}{R_F + R + R} + R_1} \\ &= u_t \frac{R_F + 2R}{R_F R + R^2 + R_1 R_F + 2R R_1} \end{aligned}$$

31.10.2003

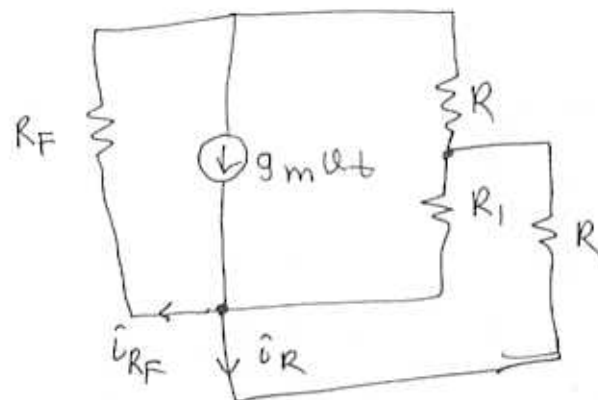(4)

The contribution by $g_m v_t$ can be calculated from the redrawn circuit:



$$i_{g_c} = i_{R_F} + i_R$$

$$i_{R_F} = g_m v_t \cdot \frac{(R_1 // R) + R}{(R_1 // R) + R + R_F}$$

$$i_R = g_m v_t \cdot \frac{R_F}{(R_1 // R) + R + R_F} \cdot \frac{R_1}{R_1 + R}$$

$$i_{g_c} = i_{R_F} + i_R = g_m v_t \cdot \frac{(R_1 // R) + R + \frac{R_F R_1}{R_1 + R}}{(R_1 // R) + R + R_F}$$

$$= \frac{\frac{R_1 R}{R_1 + R} + \frac{R_F R_1}{R_1 + R} + \frac{R(R_1 + R)}{R_1 + R}}{\frac{R_1 R}{R_1 + R} + \frac{R(R_1 + R)}{R_1 + R} + \frac{R_F(R_1 + R)}{R_1 + R}} \cdot g_m v_t$$

$$i_{g_c} = g_m v_t \cdot \frac{R R_1 + R_1 R_F + R R_1 + R^2}{R R_1 + R R_1 + R^2 + R_F R_1 + R_F R}$$

31-10-2003

(5)

$$\begin{aligned} \bar{i}_t = \bar{i}_{gt} + \bar{i}_{ct} &= v_t \frac{R_F + 2R}{2R_F + R^2 + R_1 R_F + 2R R_1} \\ &+ v_t g_m \frac{R R_1 + R_1 R_F + R R_1 + R^2}{2R R_1 + R^2 + R_F R_1 + R_F R} \end{aligned}$$

$$\bar{i}_t = v_t \frac{R_F + 2R + g_m (2R R_1 + R_1 R_F + R^2)}{R (2R_1 + R + R_F) + R_F R_1}$$

$$R_{eq} = \frac{v_t}{\bar{i}_t} = \frac{R (2R_1 + R + R_F) + R_F R_1}{(R_F + 2R)(g_m R_1 + 1) + g_m R^2}$$

If component values are given R_{eq} can easily be calculated. But to get a general feeling about the BW of the amplifier R_{eq} can be simplified at large A_v to:

31.10.2003

(5A)

$$R_{eq} = \frac{R \left(2R_1 \frac{R_F}{R_F} + \frac{R_F}{1-A_v} + R_F \right) + R_F R_1}{\left(R_F + \frac{2R_F}{1-A_v} \right) g_m R_E + g_m R^2}$$

because $R = \frac{R_F}{1-A_v}$ and $g_m R_E = 1 + g_m R_1$

$$R_{eq} = \frac{\cancel{R_F} \left[R \left(\frac{2\cancel{R_1}}{\cancel{R_F}} + \frac{1}{1-A_v} + 1 \right) + R_1 \right]}{\cancel{R_F} g_m \left[\left(1 + \frac{2}{1-A_v} \right) R_E + \frac{R^2}{R_F} \right]}$$

but $R_F = \frac{R^2}{R_E}$

or $R_E = \frac{R^2}{R_F}$

for large A_v $\frac{1}{1-A_v} \ll 1$ $R_1 < R_E \ll R \ll R_F$

$$R_{eq} = \frac{R + \cancel{R_1}}{g_m (R_E + R_E)} \approx \frac{R}{2g_m R_E}$$

$$R_{eq} = \frac{\cancel{R} (1-A_v)}{2g_m \cancel{R}} \approx \frac{|A_v|}{2g_m}$$

31-10-2003
⑥

$$\tau_{gs} = C_{gs} \times R_{gs} = C_{gs} \cdot \frac{R}{2R_E} \frac{1}{g_m} \approx C_{gs} \frac{-A_v}{2g_m}$$

Therefore the BW becomes

$$BW \equiv \frac{1}{\tau_{gs} + \tau_{gd}} = \frac{1}{C_{gd} R \frac{|A_v|}{2} + C_{gs} \frac{|A_v|}{2g_m}}$$

$$BW \approx \left[|A_v| \left(\frac{C_{gs}}{2g_m} + \frac{RC_{gd}}{2} \right) \right]^{-1}$$

$$BW = \frac{1}{|A_v|} \frac{1}{\frac{C_{gs}}{2g_m} + \frac{RC_{gd}}{2}} \Rightarrow$$

$$BW \times |A_v| = \frac{1}{\frac{C_{gs}}{2g_m} + \frac{C_{gd} R}{2}}$$

different from the book $\Rightarrow$ The gain-bandwidth product of the amplifier is constant. And in practical cases C_{gd} dominates the bandwidth.

For a typical small signal transistor which we are using at the examples,

$$\frac{C_{gs}}{2g_m} = 9.16 \times 10^{-12}$$

$$\frac{C_{gd} R}{2} = 13.5 \times 10^{-12}$$

$\Rightarrow C_{gs}$ is not negligible and

$$BW \times |A_v| = 4.41 \times 10^{10}$$

31.10.2003

(7)

Assuming that the BW is mainly limited by one dominant pole at the input (remember the case at experiment II), i.e.

$$\omega_0 = \frac{1}{\tau} \approx \frac{1}{R C_{in}} = \frac{1}{|A_v| \frac{C_{gs}}{2g_m} + |A_v| \frac{RC_{gd}}{2}}$$

$$\overset{=R_s}{R} C_{in} = \frac{R}{R_1} \frac{C_{gs}}{2g_m} + \frac{R C_{gd}}{2} |A_v|$$


$$C_{in} \approx \frac{C_{gs}}{2R_1 g_m} + C_{gd} \frac{|A_v|}{2}$$

in practical cases $C_{gd} \frac{|A_v|}{2}$ dominates the input impedance


Formulation to find out the exact expression of R_o of the shunt-series amplifier

24-10-2003

(1)

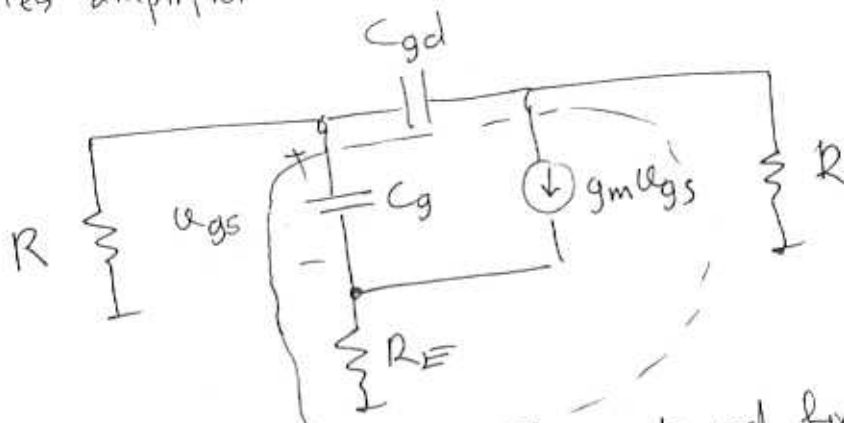

isolate this part and find an equivalent

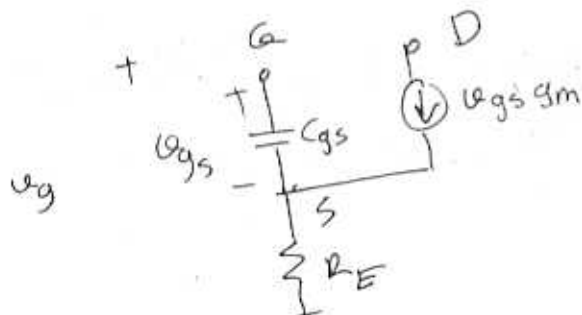

writing the node equation at the

source

$$v_s G_E = (v_g - v_s) s C_{gs} + (v_g - v_s) g_m$$

$$v_s G_E = v_g (s C_{gs} + g_m) - v_s (s C_{gs} + g_m)$$

$$v_s [G_E + g_m + s C_{gs}] = v_g [s C_{gs} + g_m]$$

$$\Rightarrow v_s = v_g \frac{[s C_{gs} + g_m]}{G_E + g_m + s C_{gs}}$$

$$i_g = s C_{gs} [v_g - v_s] \Rightarrow$$

$$Z_{in} = \frac{v_g}{i_g} = \frac{v_g}{s C_{gs} \left[v_g - \frac{v_g [s C_{gs} + g_m]}{G_E + g_m + s C_{gs}} \right]}$$

$$\parallel s C_{gs} [v_g - v_s]$$

24-10-2003

(2)

$$Z_{in} = \frac{1}{sC_{gs} \left[1 - \frac{g_m + sC_{gs}}{G_E + sC_{gs} + g_m} \right]}$$

$$= \frac{1}{sC_{gs} \left[\frac{G_E + sC_{gs} + g_m - g_m - sC_{gs}}{G_E + sC_{gs} + g_m} \right]}$$

$$= \frac{G_E + g_m + sC_{gs}}{sC_{gs}G_E} = \frac{G_E + g_m}{sC_{gs}G_E} + \frac{1}{G_E}$$

$$Z_{in} = \frac{1 + \frac{g_m}{G_E}}{sC_{gs}} + R_E = \underbrace{\frac{1 + g_m R_E}{C_{gs}} \cdot \frac{1}{s}}_{C_{eq.}} + \underbrace{R_E}_{R_E}$$

$$Z_{in} = \frac{1}{sC_{eq}} + R_E \quad \text{where } C_{eq} = \frac{C_{gs}}{1 + g_m R_E}$$

$$i_d = v_{gs} g_m = g_m (v_g - v_s) = g_m v_g \left[1 - \frac{sC_{gs} + g_m}{G_E + g_m + sC_{gs}} \right]$$


$$\bar{i}_d = v_g g_m \frac{G_E + g_m + sC_{gs} - sC_{gs} - g_m}{G_E + g_m + sC_{gs}}$$

$$\bar{i}_g = v_g \frac{g_m G_E}{G_E + g_m + sC_{gs}} = v_g g_m \frac{1}{1 + g_m R_E + sC_{gs} R_E}$$


$$\bar{i}_g = v_g \frac{g_m}{1 + g_m R_E + sC_{gs} R_E}$$

24-10-2003


3

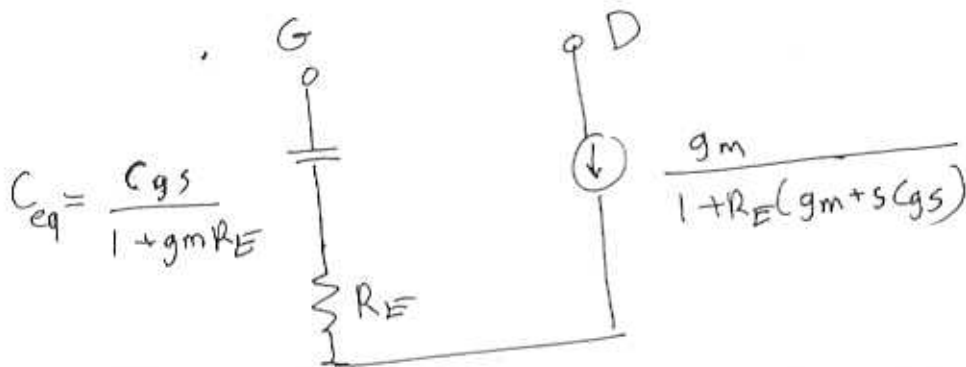

Substituting into the original diagram

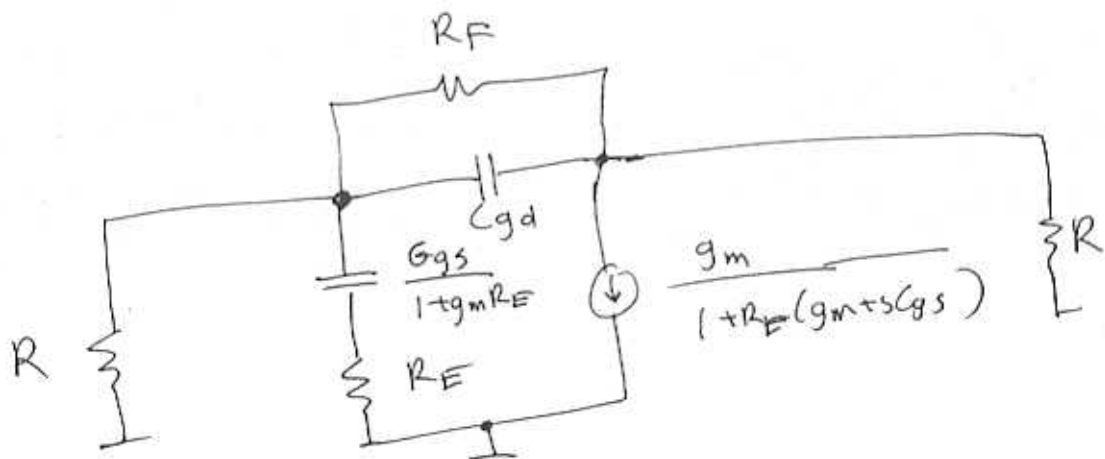

24

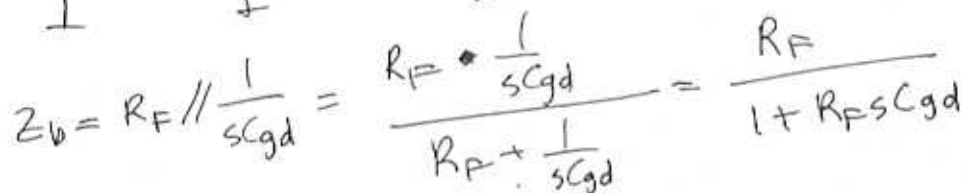

$$Z_a = R \parallel \left(R_E + \frac{1}{s C_{eq}} \right) = \frac{R \left(R_E + \frac{1}{s C_{eq}} \right)}{R + R_E + \frac{1}{s C_{eq}}} = R \frac{[s C_{eq} R_E + 1]}{(R + R_E) s C_{eq} + 1}$$

$$Z_a = \mathbb{R}$$

$$i = i_0 - v_g g_{m \text{ eff}}$$

$$\bar{z}_a = \vartheta_g = z_a (i - \vartheta_g g_{\text{eff}})$$

$$U_g = z_o \dot{I}_o - z_a U_g g_{\text{meff}}$$

$$V_g (1 + Z_a g_{mef}) = Z_a i_o$$

$$U_g = Z_o i_o - Z_a U_g g_{mefl}$$

$$U_g (1 + Z_a g_{mefl}) = Z_o i_o \Rightarrow U_g = i_o \frac{Z_o}{1 + Z_a g_{mefl}}$$

24-10-2003
(5)

$$\bar{v} [Z_a + Z_b] = v_o$$

$$v_o = [Z_a + Z_b] [\bar{v}_o - v_g g_{m\text{eff}}]$$

$$v_o = [Z_a + Z_b] \left[\bar{v}_o - \bar{v}_o g_{m\text{eff}} \cdot \frac{Z_a}{1 + Z_a g_{m\text{eff}}} \right]$$

$$R_o = \frac{v_o}{\bar{v}_o} = [Z_a + Z_b] \left[1 - g_{m\text{eff}} \frac{Z_a}{1 + Z_a g_{m\text{eff}}} \right]$$

$$= [Z_a + Z_b] \left[\frac{1 + \cancel{Z_a g_{m\text{eff}}} - \cancel{Z_a g_{m\text{eff}}}}{1 + Z_a g_{m\text{eff}}} \right]$$

$$= [Z_a + Z_b] \frac{1}{1 + Z_a g_{m\text{eff}}}$$

$$R_o = \frac{Z_a + Z_b}{1 + Z_a g_{m\text{eff}}}$$

$$= \frac{Z_a + Z_b}{1 + Z_a \frac{g_m}{1 + R_E(g_m + sC_{gs})}}$$

$$Z_a = R \frac{\frac{sC_{gs} R_E}{1 + g_m R_E} + 1}{(R + R_E) \frac{sC_{gs}}{1 + g_m R_E} + 1}$$

$$= R \frac{R_E sC_{gs} + 1 + g_m R_E}{(R + R_E) sC_{gs} + 1 + g_m R_E}$$

$$= R \frac{R_E sC_{gs} + 1 + g_m R_E}{(R + R_E) sC_{gs} + 1 + g_m R_E} = R R_E \frac{sC_{gs} + G_E + g_m}{\frac{R + R_E}{R_E} sC_{gs} + G_E + g_m}$$

$$Z_a = R \frac{sC_{gs} + G_E + g_m}{\left(1 + \frac{R}{R_E}\right) sC_{gs} + G_E + g_m}$$

$$R_o = (Z_o + Z_b) \frac{1}{1 + R_E(g_m + sC_{gs}) + Z_o g_m}$$

$$1 + R_E(g_m + sC_{gs})$$

$$R_o = \frac{(Z_o + Z_b)(1 + R_E(g_m + sC_{gs}))}{1 + R_E(g_m + sC_{gs}) + Z_o g_m}$$

$$R_o = \frac{\left[R \frac{sC_{eq} R_E + 1}{(R + R_E)sC_{eq} + 1} + \frac{R_F}{1 + R_F sC_{gd}} \right]}{1 + R_E(g_m + sC_{gs}) + g_m R \frac{sC_{eq} R_E + 1}{(R + R_E)sC_{eq} + 1}}$$

$$R \left[\frac{s \frac{C_{gs} R_E}{1 + g_m R_E} + 1}{(R + R_E)s \frac{C_{gs}}{1 + g_m R_E} + 1} + \frac{R_F}{1 + R_F sC_{gd}} \right]$$



$$Z_o = \frac{1 + R_E(g_m + sC_{gs}) + g_m R \left[\frac{s \frac{C_{gs} R_E}{1 + g_m R_E}}{(R + R_E)s \frac{C_{gs}}{1 + g_m R_E} + 1} \right]}{1 + R_E(g_m + sC_{gs}) + g_m R \left[\frac{s \frac{C_{gs} R_E}{1 + g_m R_E}}{(R + R_E)s \frac{C_{gs}}{1 + g_m R_E} + 1} \right]}$$

$$R_o = \frac{R \frac{sC_{gs} + G_E + g_m}{\left(1 + \frac{R}{R_E}\right)sC_{gs} + G_E + g_m} + R_F \frac{1}{G_F + sC_{gd}}}{1 + R_E(g_m + sC_{gs}) + g_m R \frac{sC_{gs} + G_E + g_m}{\left(1 + \frac{R}{R_E}\right)sC_{gs} + G_E + g_m}}$$

18.10.2005

(2)

Talk about scope probe

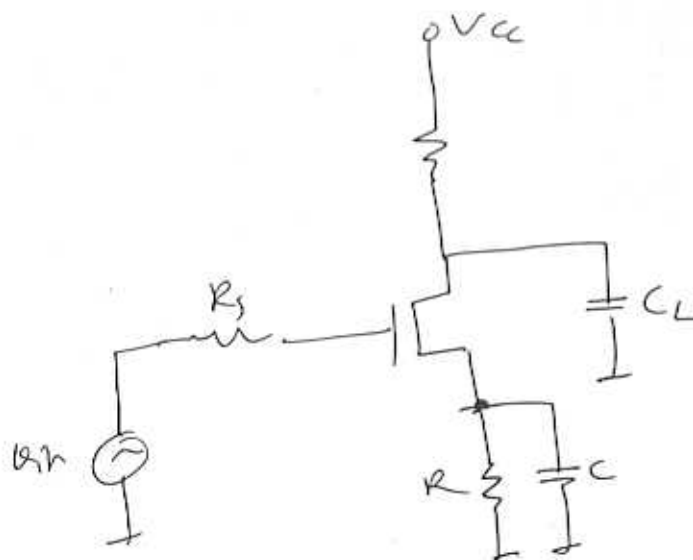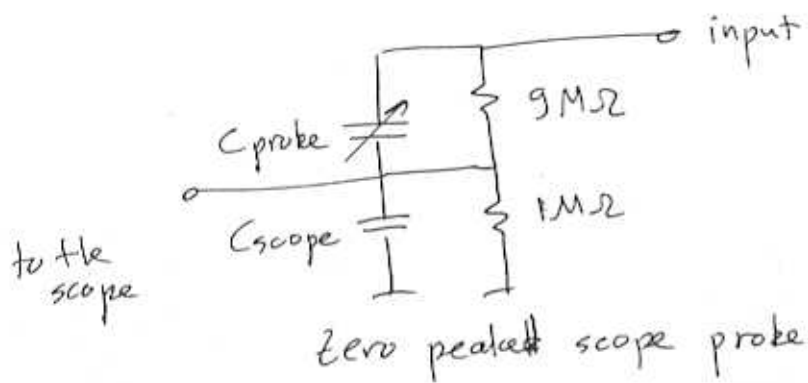

zero-peaked common source amplifier.