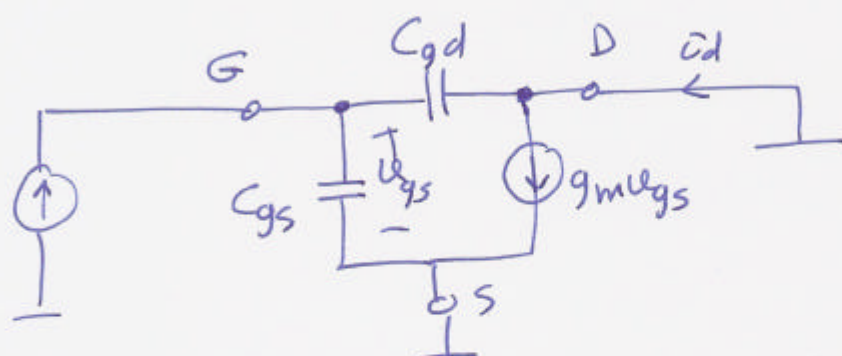


f_T (the unity gain bandwidth)

The definition

The most common definition of $\omega_T = 2\pi f_T$:



Neglecting the effect of C_{gd} on i_d and shorting the drain to A.C.-ground:

ω_T is the radian frequency at which the current gain of the amplifier is equal to unity (or more precisely at the frequency at which the extrapolated gain curve meets unity gain line).


$$\left| \frac{i_d}{v_{in}} \right| = \frac{g_m}{\omega (C_{gs} + C_{gd})}$$

$$1 = \frac{g_m}{\omega_T (C_{gs} + C_{gd})} \Rightarrow$$

$$\omega_T = \frac{g_m}{C_{gs} + C_{gd}}$$

5-11-2003
(2)

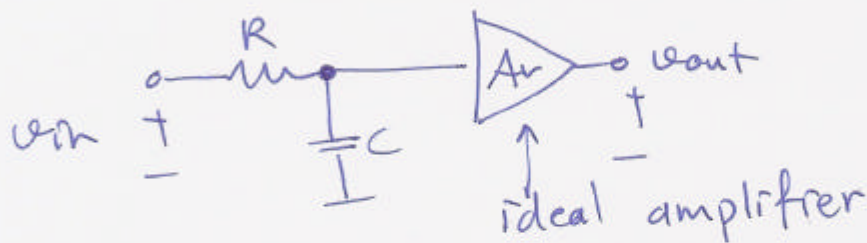The other name for ω_T is the gain-bandwidth product. Take the following example of an amplifier with single dominant pole.



$$G(\omega) = \frac{v_{out}(j\omega)}{v_{in}(j\omega)} = \frac{A_v}{1 + j\omega RC}$$


$$G(\omega_T) = 1 = \left(\frac{A_v^2}{1 + \omega_T^2 R^2 C^2} \right)^{1/2}$$

$$\Rightarrow \omega_T = \frac{(A_v^2 - 1)^{1/2}}{RC} \approx \frac{A_v}{RC} \quad \text{for } A_v \gg 3$$

The 3dB bandwidth of the amplifier is $\omega_{3dB} = \frac{1}{RC} \Rightarrow$

$$\text{gain-bandwidth product} = \frac{A_v}{RC} = \omega_T$$

f_t doubler

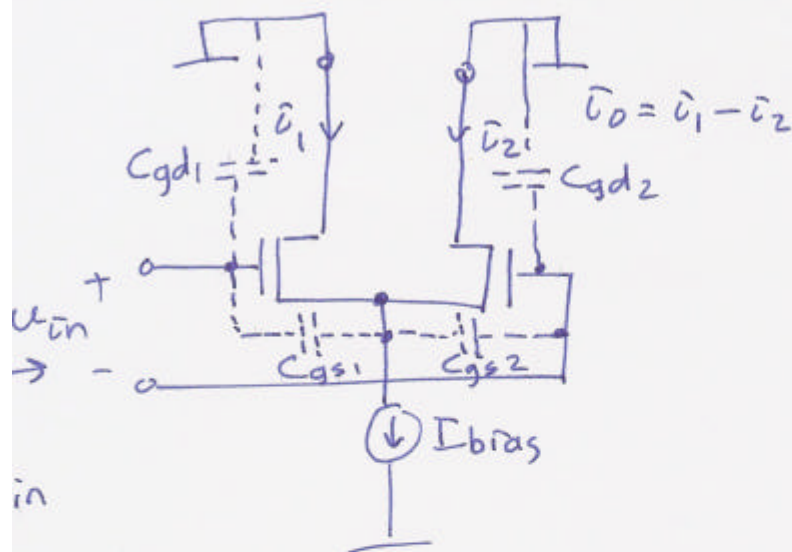

differential pair as f_t doubler

The gain g_m of the differential pair is the same as of the single transistor if i_o is taken as $i_1 - i_2$ since v_{gs} of each transistor is the half of v_{in} , but i_o is twice of i_1 and i_2 . At the same time, C_{in} is half of the gate-to-source capacitance, therefore doubling f_t . Remember

$$w_f = \frac{g_m}{C_{in}} = \frac{2 \times g_m / 2}{\frac{C_{gs}}{2} + \frac{C_{gd}}{2}} = \frac{2g_m}{C_{gs} + C_{gd}}$$