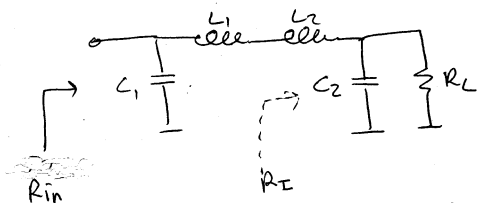


(i)

A note on π -match Q calculation



$$1st \quad Z_{C1} = +jX_{C1} = -j \frac{1}{\omega_0 C_1}$$

$$Z_{C2} = jX_{C2} = -j \frac{1}{\omega_0 C_2}$$

$$Z_{L1} = jX_{L1} = j\omega_0 L_1$$

$$Z_{L2} = jX_{L2} = j\omega_0 L_2$$

$$Z_L = jX_L = j\omega_0 L$$

$$Q = Q_L + Q_R = \frac{\omega_0(L_1 + L_2)}{R_I} = \frac{X_L}{R_I}$$

$$Q_L = \omega_0 C_1 R_{in} = \frac{R_{in}}{-X_{C1}}$$

$$Q_R = \omega_0 C_2 R_L = \frac{R_L}{-X_{C2}}$$

$$(Q_L^2 + 1) R_I = R_{in} \quad \text{equ. (1)}$$

$$(Q_R^2 + 1) R_I = R_L \quad \text{equ. (2)}$$

The equation for overall Q was

$$Q = \frac{\omega_0(L_1 + L_2)}{R_I} = Q_L + Q_R = \sqrt{\frac{R_{in}}{R_I} - 1} + \sqrt{\frac{R_L}{R_I} - 1}$$

This equation requires iteration to solve for R_I especially if the Q is low. But this system of

equations actually has an analytical solution. (2)
 Dividing equ. 1 by equ. 2, we get:

$$\frac{R_{in}}{R_L} = \frac{Q_L^2 + 1}{Q_R^2 + 1}, \quad \text{letting } K = \frac{R_{in}}{R_L}$$

$$K = \frac{Q_L^2 + 1}{Q_R^2 + 1} \quad \text{equ. (3)}$$

$$K Q_R^2 + K = Q_L^2 + 1$$

$$K Q_R^2 + K - 1 = Q_L^2 = (Q - Q_R)^2 = Q^2 - 2Q Q_R + Q_R^2$$

$$K Q_R^2 - Q_R^2 + \underbrace{2Q Q_R}_b - \underbrace{Q^2 + K - 1}_c = 0$$

$$K - 1 = a$$

This is a quadratic equation, the solution of which is given by:

$$Q_{R,1,2} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$= \frac{-2Q \pm \sqrt{4Q^2 - 4(K-1)(K-1-Q^2)}}{2(K-1)}$$

$$= \frac{-2\sqrt{Q^2 - (K^2 - K - KQ^2 - K + 1 + Q^2)}}{2(K-1)} - Q$$

$$Q_{R,1,2} = \frac{\sqrt{Q^2 - K^2 + K + KQ^2 + K - 1 - Q^2} - Q}{K-1}$$

(3)

Rearranging the terms and taking only the positive signed $\sqrt{\quad}$ term, we get

$$Q_R = \frac{[Q^2 K + 2K - K^2 - 1]^{1/2} - Q}{K - 1} \quad \text{Equ. (4)}$$

which lets us directly calculate Q_R hence Q_L . The other root of the equation is obviously negative. Note that the numerator of the equation changes sign along with the denominator at $K=1$, so Q_R turns out to be positive even for $1 > K > 0$. For $K \leq 0$ we are talking about lossless loads and negative resistance which are beyond the scope of this note.

④

Extension to T-match

In T-match the dual equations are

$$Q = \omega_0 R_I (C_1 + C_2) = \sqrt{\frac{R_I}{R_{in}} - 1} + \sqrt{\frac{R_I}{R_L} - 1} = Q_L + Q_R$$

$$(Q_L^2 + 1) R_{in} = R_I \quad \text{equ- (5)}$$

$$(Q_R^2 + 1) R_L = R_I \quad \text{equ- (6)}$$

dividing equ 5 by equ-6, we obtain

$$\frac{Q_L^2 + 1}{Q_R^2 + 1} = \frac{R_L}{R_{in}} = K \quad \text{equ- (7)}$$

This time letting $K = \frac{R_L}{R_{in}}$ instead of $\frac{R_{in}}{R_L}$


The rest of the derivation is the same $\Rightarrow$

$$Q_R = \frac{[Q^2 K + 2K - K^2 - 1]^{1/2} - Q}{K - 1}$$

$$Q_R = \frac{X_{L2}}{R_L}$$

$$Q_L = \frac{X_{L1}}{R_{in}}$$

$$Q = \frac{R_I}{X_C}$$

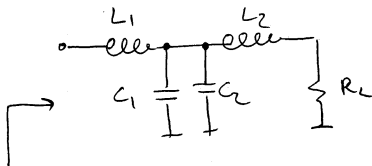

R_{in}
Of course, one must be careful in substituting the appropriate variables in dual Q expressions.