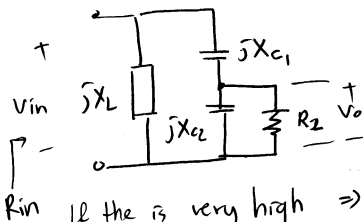


Tapped Impedance match

①



If the is very high $\Rightarrow R_2 \gg (X_{C2}) \Rightarrow$

this is a simple voltage divider and as the result +

$$V_o = n V_{in} = \frac{X_{C2}}{X_{C1} + X_{C2}} V_{in} \Rightarrow n = \frac{X_{C2}}{X_{C1} + X_{C2}} = \frac{\frac{1}{j\omega C_2}}{\frac{1}{j\omega C_1} + \frac{1}{j\omega C_2}}$$

$$\Rightarrow n = \frac{\frac{1}{C_2} C_1 C_2}{\left(\frac{1}{C_1} + \frac{1}{C_2}\right) C_1 C_2} = \frac{C_1}{C_1 + C_2}$$

Since dissipation must be the same the equivalent resistance R_{in} is related R_2 as

$$\frac{\frac{V_{in}^2}{R_{in}}}{\frac{V_o^2}{R_2}} = 1 \Rightarrow \frac{V_{in}^2}{V_o^2} = \frac{R_{in}}{R_2} = n^2$$

$\Rightarrow R_{in} = n^2 R_2$ as in a transformer

Note that the loss is always transformed, but to observe it purely you need to tune out the capacitive part.

5-10-2006
(2)


The capacitive part to be tuned out is given by approximately again

$$X_{C1} + X_{C2} \text{ as } R_2 \ll X_{C2} \Rightarrow$$

$$C_{eq} = C_1 \text{ in series with } C_2 = \frac{C_1 C_2}{C_1 + C_2}$$


To solve the problem exactly at resonance please refer to "a note on impedance transformer".

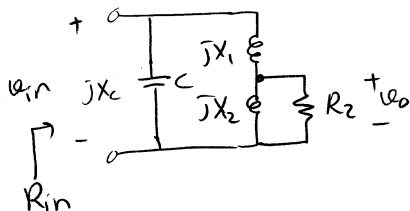The inductive divider acts similarly with only the capacitive and inductive impedances interchanged.



A note on resonant impedance transformer


①

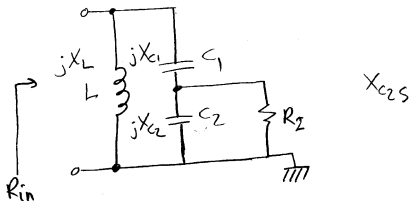

In this circuit we would like to find the impedance seen in parallel with the inductor, namely R_{in} . The problem is similar to Π -match, with the differences:

- a-) The ground is at a different position
- b-) we are trying to find the equivalent resistance seen in parallel with L instead of in parallel with C_1

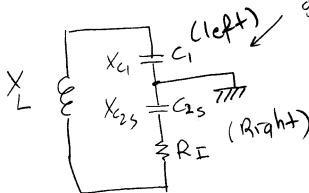The above circuit is equivalent to grounding changed



$$Q_R = \frac{R_2}{X_{C2}} \Rightarrow X_{C2} = \frac{R_2}{Q_R}$$

$$R_E = R_L / (Q_R^2 + 1)$$

$$X_{C2s} = \frac{Q_R^2}{Q_R^2 + 1} X_{C2}$$

The circuit resonates at the frequency ω defined by X_L & $X_{C1} + X_{C2s}$

(2)

Our aim is to transform the resistance R_L to R_{in} at resonance. If we let

$$K = \frac{R_{PL}}{R_2} = \frac{R_{in}}{R_2} \quad \text{where } R_{PL} \text{ is the equivalent resistance in parallel with } L$$

$$R_{in} = R_{PL} = R_I (Q^2 + 1) \quad \text{where } Q = Q_L + Q_R$$

$$(Q^2 + 1) R_I = R_{in} \quad \text{①}$$

$$(Q_R^2 + 1) R_I = R_2$$

dividing the 2 equations

$$\frac{Q^2 + 1}{Q_R^2 + 1} = \frac{R_{in}}{R_2} = K \Rightarrow$$

$$Q^2 + 1 = K Q_R^2 + K \Rightarrow K Q_R^2 = Q^2 + 1 - K \Rightarrow$$

$$Q_R = \sqrt{\frac{Q^2 + 1 - K}{K}}$$

$$Q_L = Q - Q_R = Q - \sqrt{\frac{Q^2 + 1 - K}{K}}$$

After finding Q_L & Q_R for the required Q & K
 R_I can be found by

$$R_I = \frac{R_2}{Q_R^2 + 1} \quad \text{and} \quad Q_L = Q - Q_R = \frac{X_{C1}}{R_I} \quad \text{and} \quad Q = \frac{R_{in}}{X_L}$$

$$\Rightarrow X_{C1} = Q_L R_I \quad \text{and} \quad X_L = \frac{R_{in}}{Q}$$

(3)

or alternatively use the following steps in solving the problem:


$$1-) (Q^2 + 1) R_E = R_{in} \Rightarrow R_E = \frac{R_{in}}{Q^2 + 1} \text{ \& } X_L = \frac{R_{in}}{Q}$$

$$2-) (Q_R^2 + 1) R_E = R_2 \Rightarrow Q_R^2 = \frac{R_2}{R_E} - 1 \Rightarrow |X_{C1}| = \frac{R_2}{Q_R}$$

$$3-) Q - Q_R = Q_L = \frac{|X_{C1}|}{R_E}$$

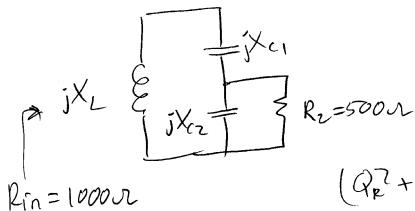Example:

Find the reactances of the upward transformer which converts 500Ω into 1000Ω employing a $Q = 3$.



$$(Q^2 + 1) R_E = R_{in}$$

$$(3^2 + 1) R_E = 1000$$

$$\Rightarrow R_E = \frac{1000}{10} = 100\Omega$$

$$(Q_R^2 + 1) R_E = 500\Omega \Rightarrow$$

$$Q_R^2 + 1 = \frac{500}{100} = 5 \Rightarrow Q_R = 2$$

$$\frac{|X_{C1}|}{100} = 3 - 2 = Q_L = 1 \Rightarrow X_{C1} = -100$$

$$Q_R = 2 = \frac{500}{|X_{C1}|} \Rightarrow X_{C1} = \frac{-500}{2} = -250j$$

$$X_L = \frac{R_{in}}{Q} = \frac{1000}{3} = 333.33$$