

Solutions

Q. 1

$$a-) F_{1,2} = F_1 + \frac{F_2 - 1}{G_1}$$

$$F_{1,2} \text{ 8 dBFS } \Rightarrow F_{1,2} = 6.31$$

$$F_1 = 6 \text{ dB} \rightarrow F_1 = 4$$

$$F_2 = 6 \text{ dB} \rightarrow F_2 = 4$$

$$6.31 = 4 + \frac{3}{G_1} \Rightarrow 2.31 = \frac{3}{G_1}$$

$$G_1 = \frac{3}{2.31} = 1.3 \text{ times} \Rightarrow 1.135 \text{ dB}$$

But there are 4 dB cable losses and 6 dB divider loss. Therefore gain of the antenna amplifier must be
 $4 + 6 + 1.135 = 11.135 \text{ dB}$

b-)

$$F_{1,2} = 6.31 = \frac{S_i/N_i}{S_o/N_o} = \frac{S_i/kT_oB}{\frac{20/10}{10}}$$


$$6.31 = \frac{S_i}{100kT_oB} \Rightarrow S_i = 6.31 \times 100 \times 1.38 \times 10^{-23} \times 290 \times 5.5 \times 10^6$$

$$S_i = 1.3889 \times 10^{-11} \text{ W} = 1.389 \times 10^{-8} \text{ mW}$$

$$S_i = 10 \times \log 1.389 \times 10^{-8} = -78.6 \text{ dBm}$$

Solutions

Q. 2

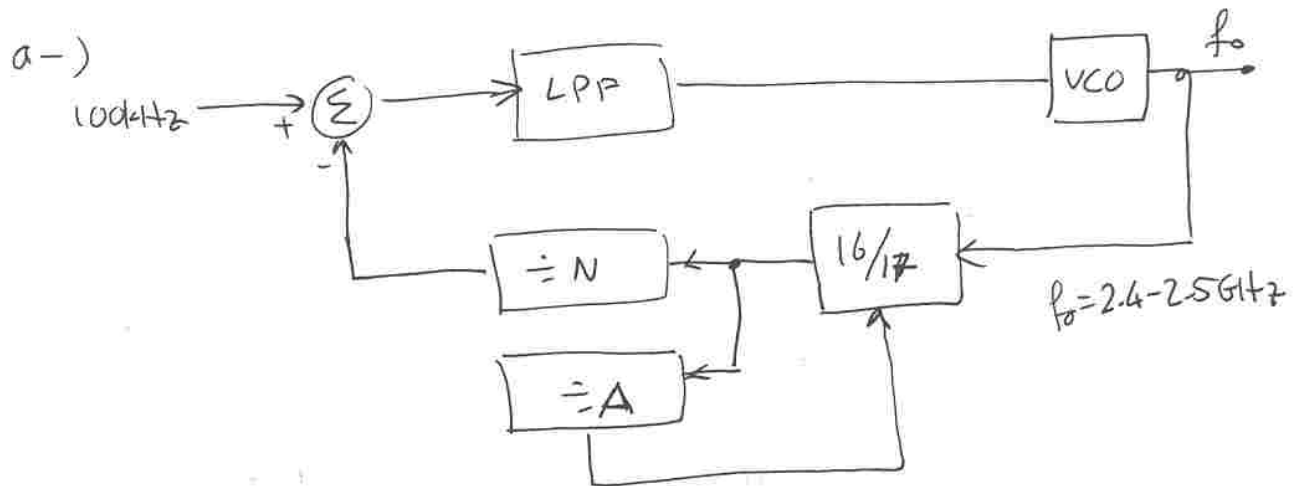


b-)

$$M = NP + A = \frac{2.455 \text{ GHz}}{0.0001 \text{ GHz}} = 24550$$

$$N = \frac{24550}{16} = 1534.375 \Rightarrow N = 1534$$

$$A = M - NP = 24550 - 1534 \times 16 = 6$$

c-)

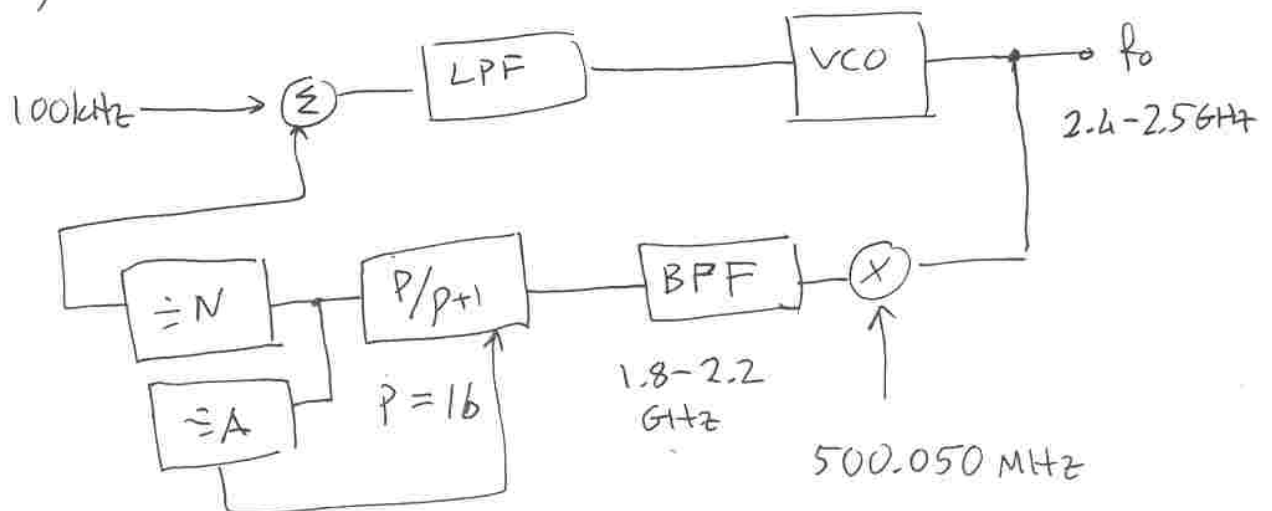

$$d-) f_0 = 2455.05 \text{ MHz}$$

$$f_{\text{divider}} = 2455.05 - 500.05 \\ = 1955 \text{ MHz}$$

$$M = \frac{f_{\text{divider}}}{0.1 \text{ MHz}} = \frac{1955}{0.1} = 19550$$

$$N = \frac{M}{P} = 1221.875 \Rightarrow N = 1221$$

$$A = M - NP = 19550 - 1221 \times 16 = 14$$

Q.3

Solutions

$$a \rightarrow g_m > \frac{1}{R(1-n^2)}$$

$$IV \quad R_p = (Q^2 + 1)R_I = 1501 \Omega$$

$$III \quad Q = \frac{\omega L_s}{R} = 38.73$$

$$II \quad \omega_0 = \frac{1}{\sqrt{LC_1}} = 387.3 \text{ Mrad/sec}$$

$$I \quad C_{eq} = \frac{C_1 C_2}{C_1 + C_2} = \frac{100 \times 200}{300} = 66.66 \text{ pF}$$

$$f_0 = 61.64 \text{ MHz}$$

$$VI \quad R_{eq} = 1500 // 10K = \frac{1500 \times 10}{11.5} = 1305 \Omega$$

$$n = \frac{100}{100+200} = \frac{C_1}{C_1+C_2} = \frac{1}{3}$$

$$g_m > \frac{1}{1305 \left(\frac{1}{3} - \frac{1}{9} \right)} = 3.45 \text{ millisiemens}$$

$$b \rightarrow V_{tan\omega} = 2I_{BIAS} R(1-n)$$

$$1V_{rms} \Rightarrow \sqrt{2} V_{peak}$$

$$\sqrt{2} = 2I_{BIAS} \times 1305(1-0.33)$$

$$I_{BIAS} = \frac{\sqrt{2}}{2 \times 1305 \times 0.66} = 8.1 \times 10^{-4} = 0.81 \text{ mA}$$

Solutions

Q. 4

a-) This is a class-D amplifier. At (class-D) amplifiers the output^{peak} voltage is

$$V_{p_{\text{output}}} = \frac{4 V_{DD}}{\pi} n \quad \text{here } V_{pp} = 5V - 1V = 4V$$

because of the saturation voltage

The output peak voltage required is

$$\frac{V_p^2}{2 \times 50 \Omega} = 10W \Rightarrow$$

$$V_p^2 = 1000 \Rightarrow V_p = \sqrt{10} \times 10 = 31.6 V_{\text{peak}}$$

Equation both identities

$$\frac{4 V_{DD}}{\pi} n = 31.6 V$$

$$\Rightarrow \frac{4 \times 4}{\pi} n = 31.6 V \Rightarrow \boxed{n = \frac{\pi \times 31.6}{16} = 6.21}$$

b-) Since Class-D amplifier has the efficiency of 100% for the V_{DD} achievable, the amplifier must have $\frac{4}{5} = 80\%$ efficiency because of the transistor saturation voltage

$$\Rightarrow V_{DD} I_D = \frac{10W}{0.8} = 12.5W$$

$$\boxed{I_D = \frac{12.5W}{5V} = 2.5A}$$

Solution

Q.5

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2} = \frac{300 \times 600}{900} = 200 \text{ pF} \quad n = \frac{C_1}{C_1 + C_2} = \frac{300}{900} = 0.33$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 438.5 \text{ Mrad/sec}$$

$$f_0 = 69.795 \text{ MHz}$$

The output tank is tuned to the third harmonic of the input signal.

$$Q = \frac{R_{eq}}{\omega L} = \frac{450 \Omega}{\omega \times 26 \text{ nH}} = 39.46$$

$$R_{eq} = 50 \times \frac{1}{n^2} = 50 \times 9 = 450 \Omega$$

Since Q is high other harmonics including the fundamental are rejected.

$$V_{out} = I_{\text{drain}} \times 450 \Omega \times \frac{1}{3}$$

$$I_{\text{drain}} = g_{m_{\text{eff}}} \times \frac{V_{\text{gen}}}{2} = \frac{g_m}{1 + g_m \times 500} \times \frac{6.28 \times 4}{3 \pi} \times \frac{1}{2}$$

$$= \frac{1}{2} \times \frac{2 \times 10^{-3}}{1+3} \times \frac{8}{3} = \frac{4}{2} \times 10^{-3} \text{ A} = 2 \times 10^{-3} \text{ A}$$

$$\Rightarrow V_{out} = 2 \times 10^{-3} \times 450 \times \frac{1}{3} = 0.3 \text{ V}_{\text{peak}}$$

$$P_{out} = \frac{(0.3)^2}{2 \times 50} = 0.9 \text{ mW} = -0.46 \text{ dBm}$$