

EE411/EEE511 Midterm II


25th December 2002 18.00

Question 1: (16 points)

There is a mathing contest. The winner will be the person who used the minimum number of components to match a 1 Ohm-resistor into 10 Ohms at the frequency of 15.91 MHz. The allowed component types are inductors and capacitors. Do the match, state the component values and draw the circuit.
Note: The matching circuit must reject low frequency components.

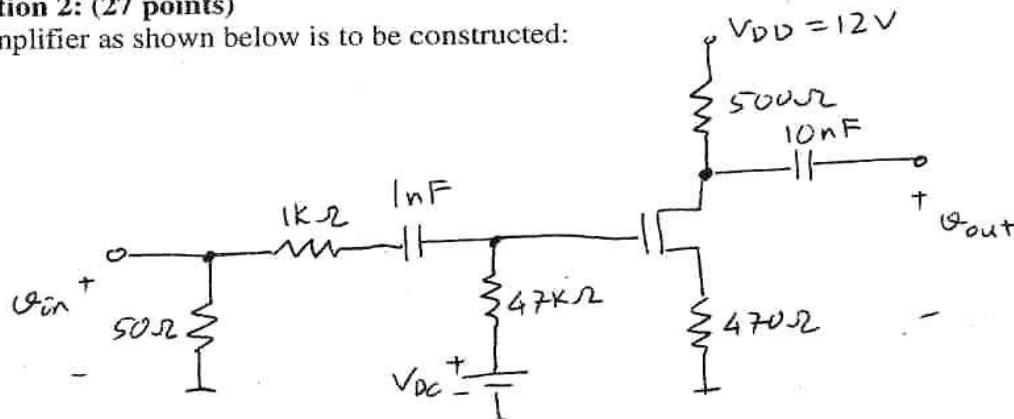Question 2: (27 points)


An amplifier as shown below is to be constructed:



$$G_m = 8 \times 10^{-3} \text{ millisiemens} \quad C_{gs} = 1 \text{ pF} \quad C_{gd} = 0.5 \text{ pF}$$

The 3dB-bandwidth of the amplifier is not known. The engineer responsible from the design tries to measure the bandwidth of the the amplifier by driving it using a 50 Ohm source and by measuring the output using a FET probe connected to an oscilloscope (The equivalent circuit of the FET probe is given below).

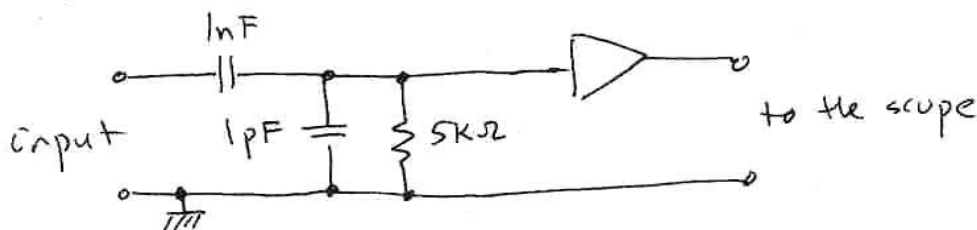- (11 points) Estimate the midband gain and the bandwidth of the amplifier without the FET probe.
- (11 points) Estimate the midband gain and the bandwidth of the amplifier with the FET probe connected.
- (5 points) Comment on the results.




The equivalent circuit of a typical FET probe.

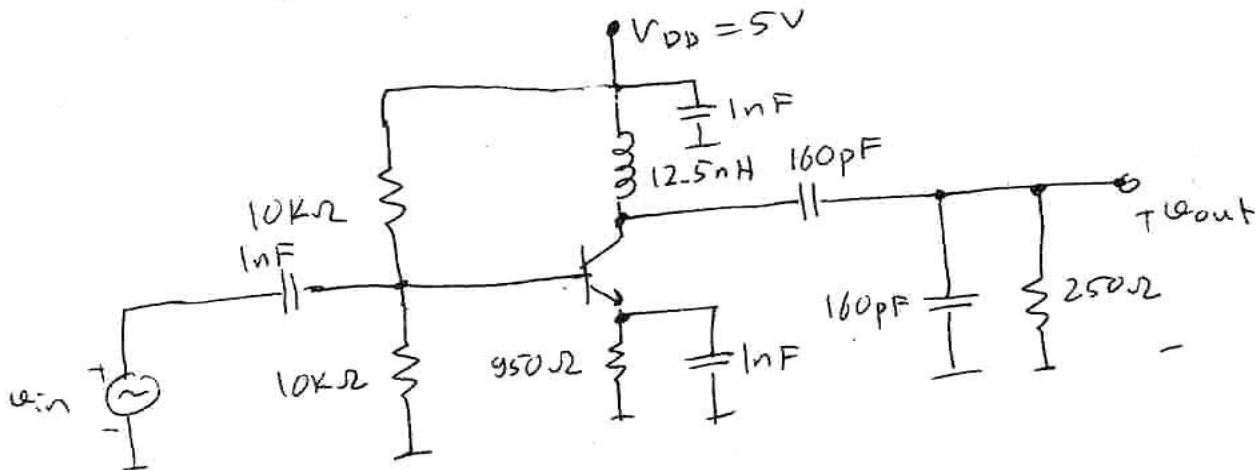Question 3: (30 points)


Given the circuit below:

- (10 points) Calculate the resonance frequency of the output tank
- (10 points) Calculate the Q of the output tank
- (10 points) If $v_{in} = 10^{-3} \cos 10^9 t$, what is the rms voltage at the output?



The transistor is an ideal BJT with $V_{BE} = 0.6$ Volts.

Question 4: (27 points)

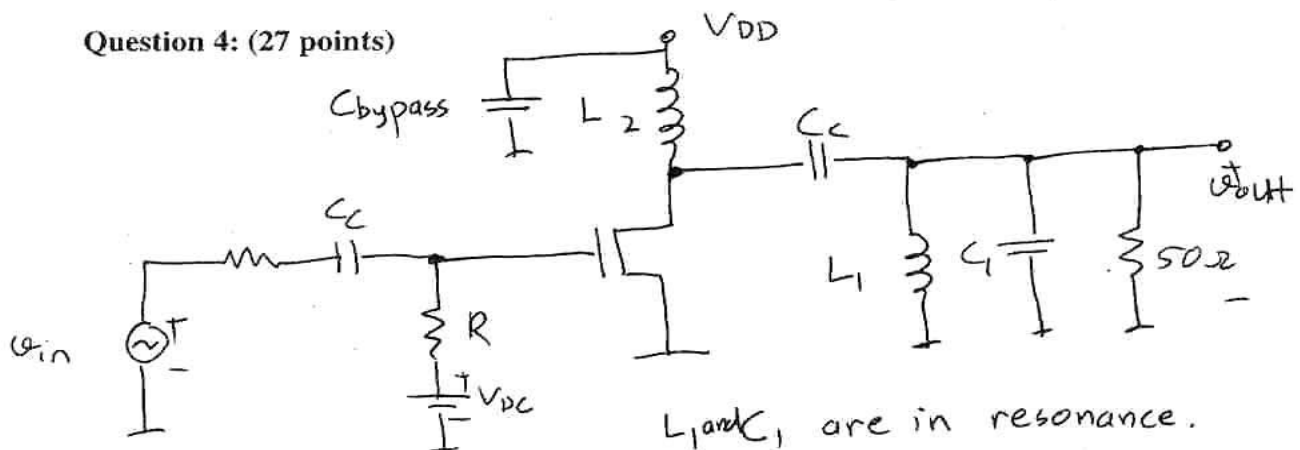

L_1 and C_1 are in resonance.

L_2 is large. C_c 's are coupling capacitors.

There is an RF power amplifier which was designed to operate either in class-A or class-B modes depending on the application. The delivered power is 1 Watts.

- (9 points) What must be the power supply voltage V_{DD} so that the amplifier operates at maximum efficiency at both class-A and class-B modes?
- (9 points) In class-A operation, find the power supply current, transistor dissipation and the peak transistor current.
- (9 points) In class-B operation, find the power supply current, transistor dissipation and the peak transistor current.