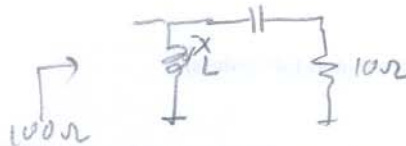



a-)



$$Q^2 + 1 = \frac{100}{10} = 10 \Rightarrow Q = 3$$

$$X_L = 3 \times 10 = 30 \Omega$$

$$X_L = \frac{100}{Q} = \frac{100}{3} = 33.3 \Omega$$

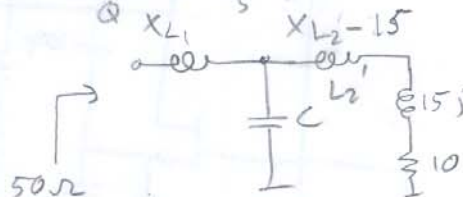b-)  
i-) T-Match

$$\frac{R_L}{R_{in}} = K = \frac{10}{50} = 0.2 \quad Q = 5$$

$$Q_R = \frac{[Q^2 K + 2K - K^2 - 1]^{1/2} - Q}{K - 1} = \frac{[25 \times 0.2 + 0.2 \times 2 - 0.04 - 1]^{1/2} - 5}{0.2 - 1}$$

$$= 3.6399 \approx 3.64$$

$$Q_L = 1.36$$

$$X_{L2} = Q_R \times 10 \Omega = 36.4 \Rightarrow X_{L2} - 15 = 21.4 \Omega \Rightarrow X_{L2}' = 21.4 j$$

$$X_{L1} = 50 \times Q_L = 50 \times 1.36 \Omega = 68 \Omega$$

$$R_I = 10 \Omega \times (Q_R^2 + 1) = 10 \times 14.25 = 142.5 \Omega$$

$$X_C = \frac{142.5}{Q} = 28.5 \Omega$$

ii-)  $\pi$ -match: Convert the load into parallel:

$$Q = \frac{15}{10} = 1.5 \quad R_p = (Q^2 + 1)10 \Omega = 32.5 \Omega \quad X_{LP} = X_{LS} \frac{Q^2 + 1}{Q^2} = 15 \times \frac{3.25}{2.25} = 21.6 \Omega$$

$$K = \frac{R_{in}}{R_L} = \frac{50}{32.5} \Rightarrow Q_R = 2.19, \quad Q_L = 2.81$$

$$\Rightarrow \frac{R_{LP}}{X_{L2}} = Q_R \Rightarrow X_{L2} = \frac{R_{LP}}{Q_R} = \frac{32.5}{2.19} = 14.85 \Omega$$

$$\frac{R_{in}}{X_{L1}} = Q_L \Rightarrow X_{L1} = \frac{R_{in}}{Q_L} = \frac{50}{2.81} = 17.79 \Omega$$


$$R_I = \frac{R_{LP}}{Q_R^2 + 1} = \frac{32.5}{2.19^2 + 1} = 5.61 \Omega \Rightarrow X_C = Q_R R_I = 5 \times 5.61 = 28 \Omega$$

06/01/2007

(2)

Q-1 continued

$$X_c = 28\Omega$$

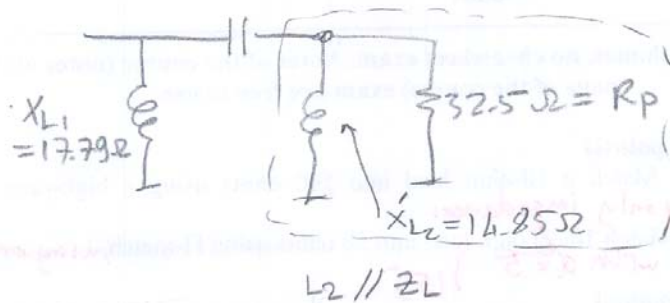


$$X_{Lp} = 21.6\Omega$$

$$X_{L2} // X_{Lp} = X'_{L2} = 14.85\Omega \Rightarrow$$

$$X_{L2} = \frac{14.85 \times 21.6}{21.6 - 14.85} = 47.52 \Rightarrow$$

The matching circuit become

$$Z_c = -j28\Omega$$

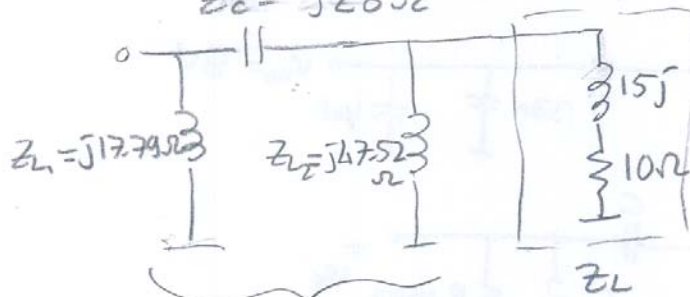

$\Pi$ -match circuit

06/01/2007

(3)

Q-2

$$a-) FKT_{dB} = 9.6 \times 10^{-13} \text{ Watts} = -120.2 \text{ dBW} = -90.2 \text{ dBm}$$

$$S/N \text{ required} = 8 \text{ dB} \Rightarrow S_{\text{req}} = -90.2 + 8 = -82.2 \text{ dBm}$$

$$b-) IP3_{i/p} = -2 \times IP3 + 3 \times S_{in} \quad \begin{aligned} &= 6 \times 10^{-12} \text{ W} \\ &= 6 \times 10^{-9} \text{ mW} \end{aligned}$$

The interfering signal is  $IP3_{i/p}$

$$IP3_{i/p} = -2 \times 25 + (3 \times 3) = -59 \text{ dBm}$$

$$\Rightarrow \text{The required signal level is } -59 \text{ dBm} + 8 \text{ dB} \\ = -51 \text{ dBm}$$

Q-3)

$$a-) I_{\text{max}} = 1 \text{ A} \Rightarrow I_{\text{peak}} = \frac{1 \text{ A}}{2} = 0.5 \text{ A}$$

$$V_p = 8 - V_{\text{sat}} = 7 \text{ V}$$

$$R_{\text{opt}} = \frac{7 \text{ V}}{0.5 \text{ A}} = 14 \Omega$$

$$R_L = 50 \Omega \quad R_{in} = 14 \Omega \quad K = \frac{R_{in}}{R_L} = \frac{14}{50} = 0.28$$

$$Q_L = \frac{[Q^2 K + 2K - K^2 - 1]^{1/2} - Q}{K - 1} = 6.61$$

$$Q_L = 3.39$$

$$R_E = \frac{R_L}{Q_L^2 + 1} = \frac{50}{6.61^2 + 1} = 1.1188 \Omega$$

$$X_C = Q \times R_E = 10 \times 1.1188 = 11.188 \Omega \quad C = 142 \text{ pF}$$

$$X_{L2} = \frac{50}{Q_L} = 7.504 \Omega \quad L_2 = 12.18 \text{ nH}$$

$$X_{L1} = \frac{14}{Q_L} = 4.13 \Omega \quad L_1 = 6.57 \text{ nH}$$

$$b-) \eta = \frac{7 \text{ V} \times 0.5 \text{ A} / 2}{8 \text{ V} \times 0.5 \text{ A}} = \frac{7}{16} = 0.4375$$

# Solutions

06/01/2007

(4)

Q4

$$a-) q_m > \frac{1}{R(n-1)n}$$

$$R_L' = 50 \times 4^2 = 800 \Omega \Rightarrow R = 800 // 800 = 400 \Omega$$

$$n = \frac{1}{4}$$

$$q_m > \frac{1}{400 \times 0.25 \times 0.75} = 0.013 \text{ s}$$

$$b-) 8 \text{ dBm} = 6.3 \text{ mW} = \frac{V_p^2}{2 \times 50} \Rightarrow V_p^2 = 6.3 \times 10^{-3} \times 10^{-2} = 0.63$$

$$V_p = 0.795 \text{ V} \text{ since here } n = 0.25$$

$$V_{\text{tank}} = \frac{0.795}{0.25} = 3.177 \text{ V}_p$$

$$V_{\text{tank}} = 3.177 = 2 I_{\text{BIAS}} R(1-n)$$

$$3.177 = 2 \times I_{\text{BIAS}} 400 \times 0.75$$

$$I_{\text{BIAS}} = \frac{3.177}{2 \times 400 \times 0.75} = 0.00529 \text{ A} = 5.3 \text{ mA}$$

$$Q-5-) \frac{8 \text{ GHz}}{6} = 1.33 \text{ GHz} > 500 \text{ MHz}$$

$$\frac{8 \text{ GHz}}{16} = 500 \text{ MHz} = 500 \text{ MHz}$$

16 barely divides  $\Rightarrow$  choose 16/17

$$f_{\text{ref}} = 2 \text{ MHz} \Rightarrow M = NP + A = \frac{6500}{2} = 3250$$

$$3250 = NP + A \quad P = 16$$

$$\frac{3250}{16} = 203.125 \Rightarrow N = 203$$

$$A = 3250 - NP = 3250 - 203 \times 16 = 2$$

# EEE411/511 Final Exam, 06 January 2007, 09.00, 150 Minutes

Student no:

Name:

This is a no cellphones, no cheatsheet closed-book exam. Notes of the course (notes at the web page of the course) exam are free to use.

## Question 1) (20 points)


- (10 points) Match a 10-ohm load into 100 ohms using a high-pass L-match circuit using only impedances.
- (10 points) Match  $10 + 15j$  ohm load into 50 ohms using  $\Pi$ -match with  $Q=5$  using only impedances.

## Question 2) (22 points)

An amplifier with the following parameters is given. The parameters are; BW=30 MHz, Noise Figure = 9 dB, IIP3 = 25 dB (Input referred third order intercept point), please answer the following questions:

- (10 points) What should be the input signal level in order that the S/N at the output of the amplifier is 8 dB,
- (12 points) A signal along with two unwanted high level signals is applied to the input of the amplifier. The unwanted signals are  $\Delta f$  and  $2\Delta f$  Hertz away from the signal and their amplitudes are -3dBm's. What should be level of the input signal in order to have the signal-to-interference level equal to 8 dB again (Please note that the intermodulation product of the unwanted signals act as interference on the signal). Note that Boltzmann's constant  $K=1.38 \times 10^{-23}$ .


## Question 3) (22 points)

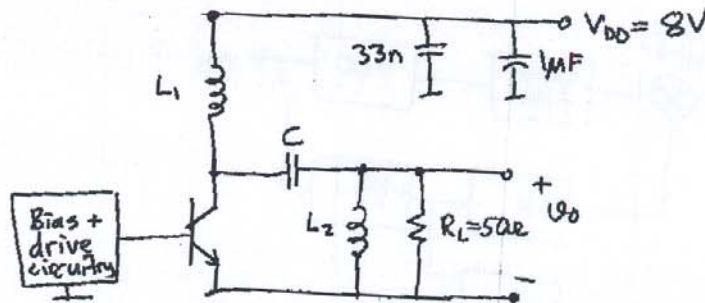

The circuit given above is operated as a class A amplifier at 100 MHz. In this circuit,  $V_{CESAT} = 1$  Volts and  $I_{max} = 1$  amps. Please carry out the following:

- (12 points) Match the load resistor  $R_L$  to obtain maximum power transfer to it by calculating the values of  $L_1$ ,  $L_2$  and  $C$ . The  $Q$  of the match must be 10,
- (10 points) Find the efficiency of the amplifier when delivering maximum power output to the load.


Question 4) ( 20 points)

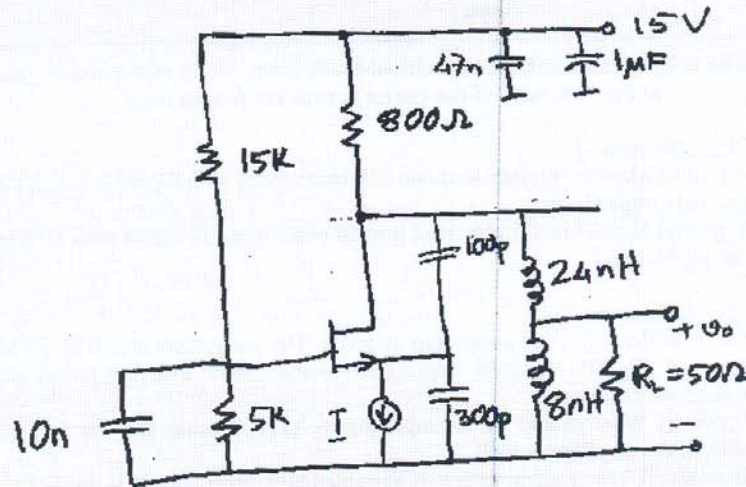

For the oscillator circuit given above (assume that DC bias is designed correctly):

- (10 points) Find the minimum value of  $g_m$  to start oscillation,
- (10 points) Set the source bias current  $I$  to make the power output to the load ( $R_L$ ) 8 dBm.

Question 5) (16 points)

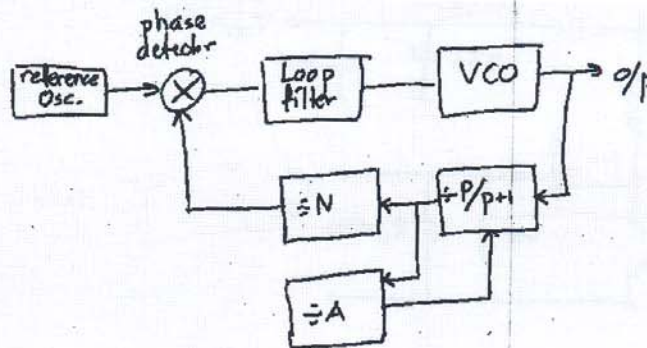

At the frequency synthesizer shown above  $f_{ref} = 2$  MHz. The  $N$  and  $A$  dividers are guaranteed to operate up to 500 MHz. The output frequency band of the synthesizer is 6-8 GHz. There are two prescalers available for design. They are divide by 6/7 and 16/17 prescalers. Choose the right prescaler and find a pair of  $N$  and  $A$  values to operate the frequency synthesizer at 6.5 GHz.