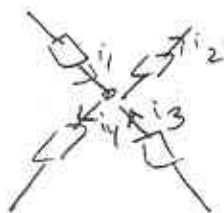


1 Let  $i_1(t), \dots, i_b(t), v_1(t), \dots, v_b(t)$  branch currents/voltages

$$I_j(s) = \mathcal{L}\{i_j(t)\}, \quad V_j(s) = \mathcal{L}\{v_j(t)\} \quad j=1, \dots, b.$$

Likewise for node voltages.

KCL:




$$-i_1(t) + i_2(t) - i_3(t) + i_4(t) = 0 \quad \text{take Laplace}$$

$$\Rightarrow \boxed{-I_1(s) + I_2(s) - I_3(s) + I_4(s) = 0}$$

$\Rightarrow$  KCL retains its form

KVL:

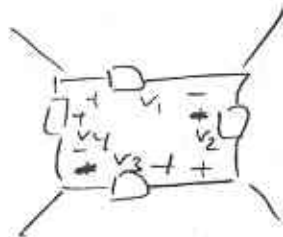

$$v_1(t) - v_2(t) + v_3(t) - v_4(t) = 0$$

$$\Rightarrow \boxed{V_1(s) - V_2(s) + V_3(s) - V_4(s) = 0}$$

$\Rightarrow$  KVL retains its form

BRANCH RELATIONS:

Resistor:




$$v(t) = Ri(t)$$

$$\Rightarrow \boxed{V(s) = RI(s)}$$


$\Rightarrow$  Resistor retains its form

Sources:

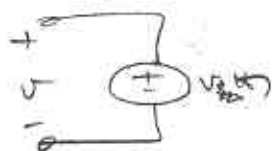

$$v(t) = v_E(t)$$

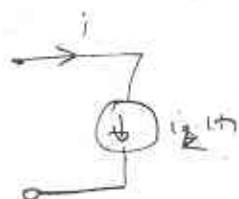
$$\Rightarrow V(s) = V_E(s) \quad \leftarrow \text{known}$$



$$i(t) = i_K(t)$$

$$\Rightarrow I(s) = I_K(s) \quad \leftarrow \text{known}$$

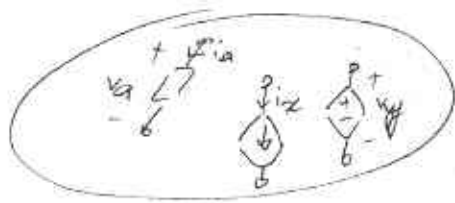
In general: any algebraic relation retains its form:



$$v_a(t) = k i_a(t) \\ i_x(t) = \alpha v_a(t)$$

$$\Rightarrow V_y(s) = k I_a(s)$$

$$\Rightarrow I_x(s) = \alpha V_a(s)$$

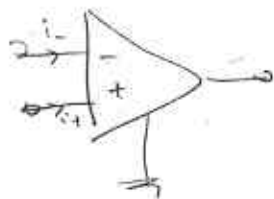


$$i_+ = i_- \\ v_+ = v_-$$

$$\Rightarrow$$

$$I_+ = I_- \\ V_+ = V_-$$

CAPACITOR:

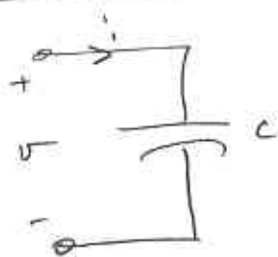

$$i = C \frac{dv}{dt}$$

$$\Rightarrow$$


$$I(s) = sC V(s) - C v(0)$$

(for node eqn's)

$$V(s) = \frac{1}{sC} I(s) + \frac{1}{s} v(0)$$

(for mesh eqn's)

example:

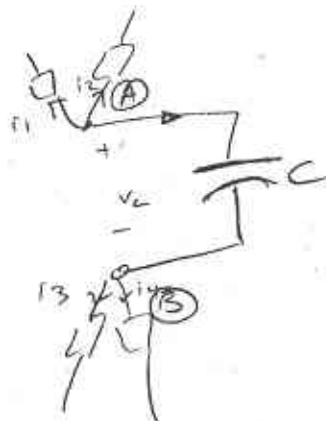



$$\textcircled{A} \quad I_1 + I_2 + sC (V_A(s) - V_B(s)) - C v_c(0) = 0$$

$$\textcircled{B} \quad I_3(s) + I_4(s) \Rightarrow [sC (V_A(s) - V_B(s)) - C v_c(0)] = 0$$

$$\text{mesh A: } \dots + \frac{1}{sC} [I_A(s) - I_B(s)] + \frac{1}{s} v_c(0) + \dots = 0$$
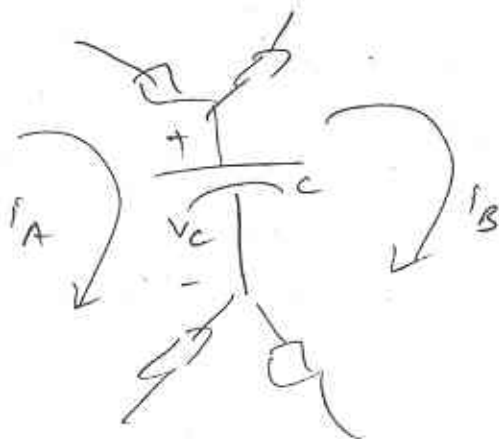
$$\text{mesh B: } \dots - \left[ \frac{1}{sC} (I_A(s) - I_B(s)) + \frac{1}{s} v_c(0) \right] + \dots = 0$$



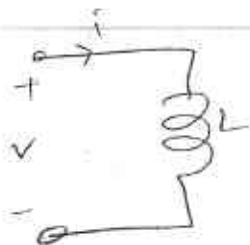


$$v = L \frac{di}{dt}$$



$$V(s) = sL I(s) - L i(0)$$
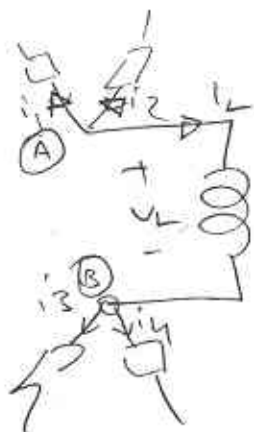
$$I(s) = \frac{1}{sL} V(s) + \frac{1}{s} i(0)$$



$$\textcircled{A} \quad I_1 + I_2 + \left\{ \frac{1}{sL} [V_A(s) - V_B(s)] + \frac{1}{s} i_L(0) \right\} \dots = 0$$

$$\textcircled{B} \quad I_3 + I_4 - \left\{ \frac{1}{sL} [V_A(s) - V_B(s)] + \frac{1}{s} i_L(0) \right\} \dots = 0$$




10-4

$$\text{mesh A} \Rightarrow \dots + [sL(I_A(s) - I_B(s)) - L i_L(0)] \dots = 0$$

$$\text{mesh B} \Rightarrow \dots - [sL(I_A(s) - I_B(s)) - L i_L(0)] \dots = 0$$
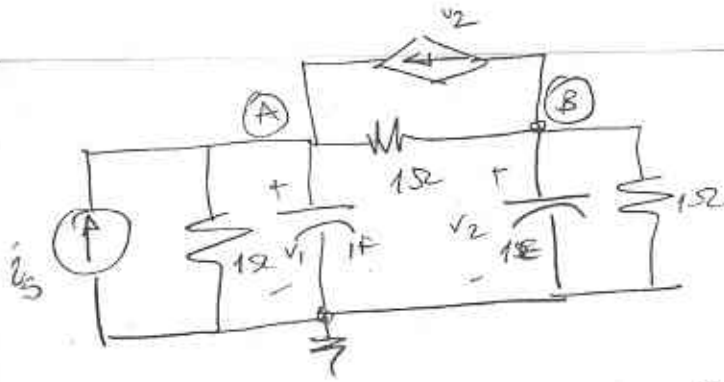
### LODE ANALYSIS:

- \* Write KCL at nodes
- \* Express each current in terms of voltages if you can. If for a certain branch, current cannot be expressed in terms of voltages, leave it as an unknown.
- \* Add the branch relations for such branches in the list of equations.



$$v_1(0) = 2V$$

$$v_2(0) = 1V$$

$$i_s(t) = u(t) \quad (\text{unit step})$$

$$\textcircled{A} \Rightarrow I_s = \frac{V_A}{1} + [sV_A - 2] + \frac{V_A - V_B}{1} - V_B$$

$$\left[ \frac{1}{s} = (s+2)V_A - 2V_B - 2 \right] \Rightarrow \boxed{(s+2)V_A - 2V_B = \frac{2s+1}{s}}$$

$$\textcircled{B} \Rightarrow -V_B + \frac{V_B}{1} + [sV_B - 1] + \frac{V_B - V_A}{1} = 0 \Rightarrow \boxed{-V_A + (s+3)V_B = 1}$$

$$-V_A = (s+3)V_B - 1 \Rightarrow (s+2)(s+3)V_B - (s+2) - 2V_B = \frac{2s+1}{s}$$

$$\Rightarrow (s^2 + 5s + 4)V_B = \frac{2s+1}{s} + (s+2) = \frac{s^2 + 4s + 1}{s}$$

$$V_B = \frac{s^2 + 4s + 1}{s(s^2 + 5s + 4)} = \frac{s^2 + 4s + 1}{s(s+1)(s+4)} = \frac{k_1}{s} + \frac{k_2}{s+1} + \frac{k_3}{s+4}$$


$$k_1 = sV_B \Big|_{s=0} = 1/4$$

$$k_2 = (s+1)V_B \Big|_{s=-1} = \frac{1-4+1}{(-1)(3)} = \frac{-2}{-3} = 2/3$$

$$k_3 = (s+4)V_B \Big|_{s=-4} = \frac{16-16+1}{(-4)(-3)} = \frac{1}{12}$$

$$\boxed{v_B(t) = v_{C2}(t) = \left( \frac{1}{4} + \frac{2}{3}e^{-t} + \frac{1}{12}e^{-4t} \right) u(t)}$$

Exercise (p. 510)

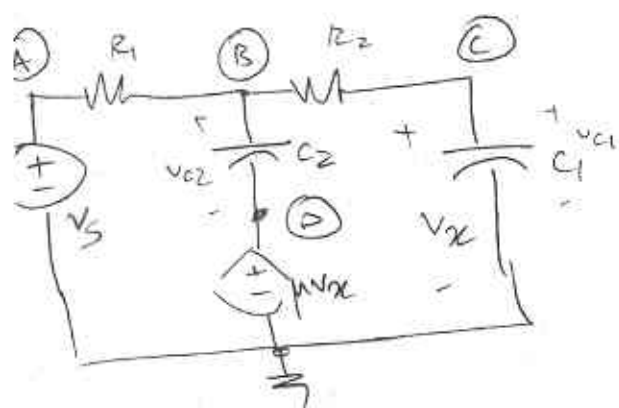

$$\underline{V_A = V_S}$$

$$\boxed{V_D = \mu V_x = \mu V_C}$$

③  $\Rightarrow$ 

$$G_1(V_B - V_A) + G_2(V_B - V_C) + SC_2[V_B(s) - V_D(s)] - C_2 V_{C2}(0) = 0$$

$$\boxed{(G_1 + G_2 + SC_2)V_B(s) - (G_2 + \mu SC_2)V_C(s) = G_1 V_S + C_2 V_{C2}(0)}$$

$$\textcircled{4} \quad G_2(V_C - V_B) + SC_1 V_C(s) - C_1 V_{C1}(0) = 0$$

$$\boxed{-G_2 V_B(s) + (G_2 + SC_1)V_C(s) = C_1 V_{C1}(0)}$$


And  $V_B(s), V_C(s) \Rightarrow V_D(s) = \mu V_C(s) \Rightarrow$  then can find any current/voltage.

$\Rightarrow \mathcal{L}^{-1}\{ \} \Rightarrow$  can find  $i(t), v(t)$

### 10.5 MESH EQUATIONS

- \* Write KVL mesh eqns
- \* Express each voltage in terms of mesh currents. If you can't a branch voltage can't be expressed in terms of mesh currents, leave it as an unknown
- \* Add the branch relations for such branches in the list of equations.

Example: (p. 520)

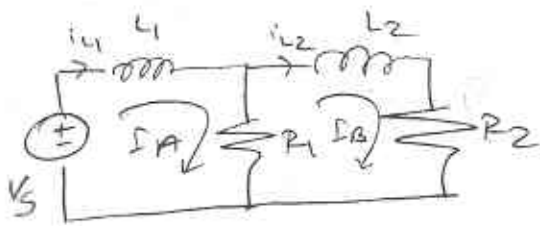

mesh A


$$V_s = sL_1 I_A(s) - L_1 i_{L1}(0) + R_1 (I_A - I_B)$$

$$\Rightarrow (sL_1 + R_1) I_A - R_1 I_B = V_s + L_1 i_{L1}(0)$$

mesh B:

$$sL_2 I_B(s) - L_2 i_{L2}(0) + R_2 I_B + R_1 (I_B - I_A) = 0$$
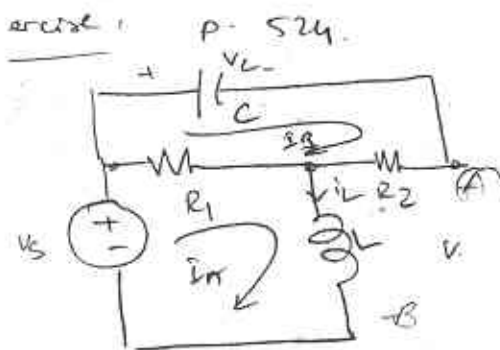
$$\Rightarrow -R_1 I_A + (sL_2 + R_1 + R_2) I_B = L_2 i_{L2}(0)$$



$$V_s = R_1 (I_A - I_B) + sL_1 I_A - L_1 i_{L1}(0)$$

$$\Rightarrow (R_1 + sL_1) I_A - R_1 I_B = V_s + L_1 i_{L1}(0)$$

$$\frac{1}{Cs} I_B + \frac{1}{s} v_C(0) + R_2 I_B + R_1 (I_B - I_A) = 0$$

$$\Rightarrow -R_1 I_A + (R_1 + R_2 + \frac{1}{Cs}) I_B = -\frac{1}{s} v_C(0)$$

$\Rightarrow$  Find  $I_A(s)$ ,  $I_B(s) \Rightarrow$  Find any  $I(s)$ ,  $V(s)$

$\Rightarrow \mathcal{L}^{-1}\{ \} \Rightarrow$  find  $i(t)$ ,  $v(t)$ .