
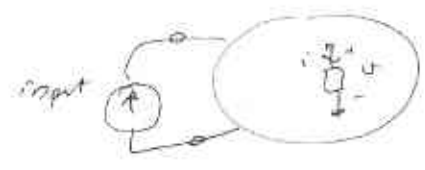


Chp 11: Network Function

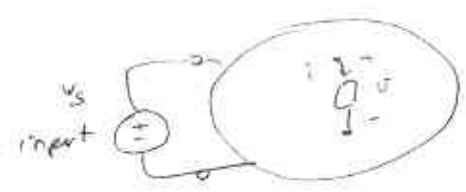

Network Function = $\frac{\mathcal{L}\{\text{zero-state response of output}\}}{\mathcal{L}\{\text{input}\}}$


zero-state response: response when initial conditions are zero (solution)

- Methodology: Use Node or mesh analysis, use zero-initial conditions. Find the Laplace transform of the output in question.

$H(s) = \frac{O(s)}{I(s)} \Rightarrow \boxed{O(s) = H(s) \cdot I(s)}$

$\Rightarrow$ can find the output (zero-state response) when the input is specified.

EXAMPLE: (p 548)

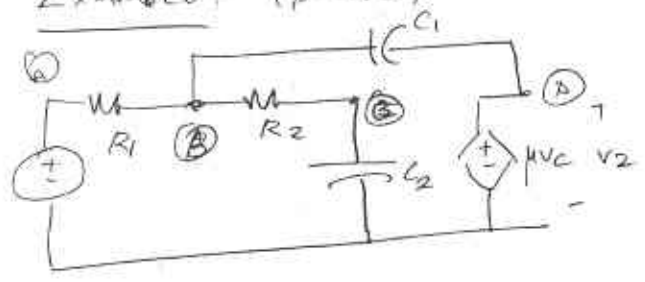

Find $\boxed{H(s) = \frac{V_2(s)}{V_1(s)}}$

$\Rightarrow G_1(V_B - V_1) + G_2(V_B - V_C) + sC_1(V_B - V_D) = 0$ ($V_C(0) = 0$)
($V_C(0) = 0$)

$\Rightarrow G_2(V_C - V_B) + sC_2 V_C = 0$

$V_D = \mu V_C$

$\Rightarrow \boxed{\begin{aligned} (G_1 + G_2 + sC_1)V_B - (G_2 + \mu sC_1)V_C &= G_1 V_1 \\ -G_2 V_B + (G_2 + sC_2)V_C &= 0 \end{aligned}}$

Find V_C in terms of $V_1 \rightarrow V_2 = \mu V_C \Rightarrow$ find $H(s)$


$$V_B = \frac{G_2 + sC_2}{G_2} V_C$$

$$\rightarrow \left[(G_1 + G_2 + sC_1) \frac{G_2 + sC_2}{G_2} - (G_2 + \mu sC_1) \right] V_C = G_1 V_1$$

$$\Rightarrow V_C = \frac{G_1 G_2}{s^2 C_1 C_2 + s(G_1 G_2(1-\mu) + C_2(G_1 + G_2)) + G_1 G_2} \cdot \frac{R_1 R_2}{R_1 R_2} \Rightarrow V_1$$

$$V_C = \frac{1}{s^2 C_1 C_2 R_1 R_2 + s(G_1 R_1(1-\mu) + C_2(R_1 + R_2)) + 1} \cdot V_1$$
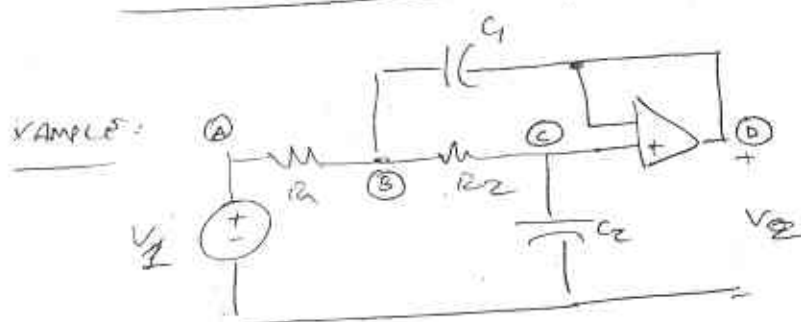
$$H(s) = \frac{V_C}{V_1} = \frac{\mu}{s^2 C_1 C_2 R_1 R_2 + s(G_1 R_1(1-\mu) + C_2(R_1 + R_2)) + 1}$$



$$H(s) = \frac{V_2}{V_1} = ?$$

Note that $V_C = V_D \Rightarrow$ previous derivation with $\mu = 1$

$$H(s) = \frac{1}{s^2 C_1 C_2 R_1 R_2 + s C_2 (R_1 + R_2) + 1}$$

ex. $R_1 = R_2 = 1\Omega$ $C_1 = 1F$ $C_2 = 1/2F$

$$H(s) = \frac{1}{s^2 \cdot \frac{1}{2} + s \cdot \frac{1}{2} \cdot 2 + 1} = \frac{2}{s^2 + 2s + 2}$$

if $V_1(t) = 1(t)$ find $V_2(t)$

$$V_1(s) = \frac{1}{s}$$

$$V_2(s) = H(s) \cdot V_1(s) = \frac{2}{s^2 + 2s + 2} \cdot \frac{1}{s} = \frac{2}{s(s - (-1+j))(s - (-1-j))}$$

$$V_2(s) = \frac{k_1}{s} + \frac{k_2}{s - (-1+j)} + \frac{k_2^*}{s - (-1-j)}$$

$$k_1 = s V_2(s) \Big|_{s=0} = 1$$

$$k_2 = (s - (-1+j)) V_2(s) \Big|_{s=-1+j} = \frac{1}{\sqrt{2}} e^{-j225^\circ}$$

$$v_o(t) = \left(1 + \frac{2}{\sqrt{2}} e^{-t} \cos(t - 225^\circ) \right) u(t)$$

* NETWORK FUNCTIONS AND IMPULSE RESPONSE (11.3)

Let input be an impulse
 $\Rightarrow$ zero-state response in this case is called impulse response.

$$H(s) = \frac{\mathcal{L}\{\text{zero-state-response}\}}{\mathcal{L}\{\text{input}\}}$$

$$H(s) = \frac{\mathcal{L}\{\text{impulse-response}\}}{\mathcal{L}\{\text{impulse}\}} = \mathcal{L}\{\text{impulse-response}\}$$

$$\boxed{\mathcal{L}\{\text{impulse-response}\} = H(s)}$$

$$h(t) = \mathcal{L}^{-1}\{H(s)\} = \text{impulse response}$$

$\Rightarrow$ CONVOLUTION

$$\text{area of } H(s) = ?$$

Combined constraints:

CL: $A I(s) \Rightarrow$

VL: $B V(s) \Rightarrow$

node: $M(s) V(s) + N(s) I(s) = U(s)$

$M(s)$: form of $sL \Rightarrow$ polynomial in s

$N(s)$: form of $sL \Rightarrow$ polynomial in s

$$\Rightarrow \begin{bmatrix} 0 & A \\ B & 0 \\ M(s) & N(s) \end{bmatrix} \begin{bmatrix} V(s) \\ I(s) \end{bmatrix} = \begin{bmatrix} 0 \\ U(s) \end{bmatrix}$$


$T(s)$: entries are polynomial in s .

$$\begin{bmatrix} V(s) \\ I(s) \end{bmatrix} = \frac{1}{\det T(s)} \begin{bmatrix} \text{cofactor} \\ \text{matrix} \end{bmatrix} \begin{bmatrix} 0 \\ U(s) \end{bmatrix}$$

polynomial in s

$$\Rightarrow H(s) = \frac{\text{polynomial in } s}{\text{polynomial in } s} = \frac{a_m s^m + a_{m-1} s^{m-1} + \dots + a_1 s + a_0}{b_n s^n + b_{n-1} s^{n-1} + \dots + b_1 s + b_0}$$

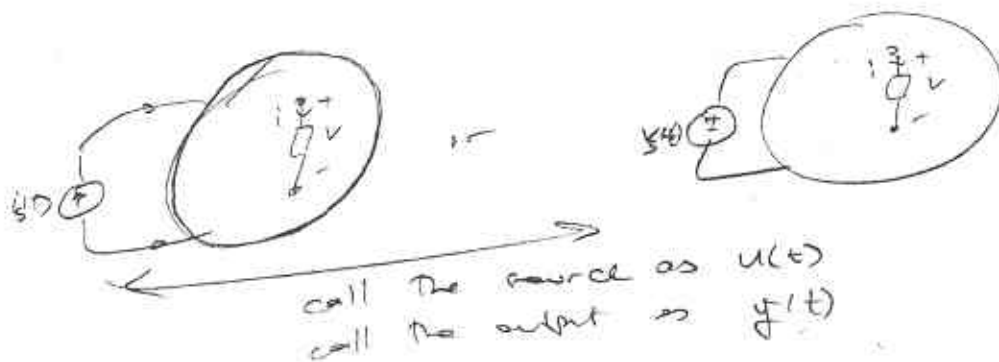* RELATION WITH SINUSOIDAL STEADY STATE : (17.5)



$$H(s) = \frac{Y(s)}{U(s)} \Rightarrow Y(s) = H(s) \cdot U(s) \quad (\text{zero state response})$$

Let us assume that $u(t)$ is sinusoidal :

$$u(t) = U_m \cos(\omega t + \phi) = \text{Re} \{ U_m e^{j\phi} e^{j\omega t} \} = \text{Re} \{ \hat{U} e^{j\omega t} \}$$

$$= \frac{1}{2} \hat{U} e^{j\omega t} + \frac{1}{2} \bar{\hat{U}} e^{-j\omega t}$$

$$\angle \{ u(t) \} = \frac{1}{2} \hat{U} \cdot \frac{1}{s - j\omega} + \frac{1}{2} \bar{\hat{U}} \cdot \frac{1}{s + j\omega}$$

$$Y(s) = H(s) \cdot \left\{ \frac{1}{2} \hat{U} \frac{1}{s - j\omega} + \frac{1}{2} \bar{\hat{U}} \frac{1}{s + j\omega} \right\}$$

$$= \frac{1}{2} H(s) \hat{U} \cdot \frac{1}{s - j\omega} + \frac{1}{2} H(s) \bar{\hat{U}} \cdot \frac{1}{s + j\omega}$$

$$\text{Let } H(s) = \frac{n(s)}{d(s)} = \frac{n(s)}{(s - p_1)(s - p_2) \dots (s - p_n)}$$

$$Y(s) = \underbrace{\frac{k_1}{s-p_1} + \dots + \frac{k_m}{s-p_m}}_{\text{natural response}} + \underbrace{\frac{k}{s-j\omega} + \frac{k^*}{s+j\omega}}_{\substack{\text{forced response} \\ (\text{sinusoidal steady state solution})}}$$

$$k = (s-j\omega) Y(s) \Big|_{s=j\omega} = \left(\frac{1}{2} H(s) \hat{u} + \frac{1}{2} H(s) \bar{\hat{u}} \cdot \frac{s-j\omega}{s+j\omega} \right) \Big|_{s=j\omega}$$

$$= \frac{1}{2} H(j\omega) \hat{u}$$


$$\Rightarrow y(t) = \frac{1}{2} H(j\omega) \hat{u} e^{j\omega t} + \frac{1}{2} \overline{H(j\omega)} \bar{\hat{u}} e^{-j\omega t} + \sum_{i=1}^n k_i e^{p_i t}$$

$$= \underbrace{\text{Re} \{ H(j\omega) \hat{u} \cdot e^{j\omega t} \}}_{\substack{\text{sinusoidal steady state} \\ \text{response}}} + \sum_{i=1}^n k_i e^{p_i t}$$

But then: output phasor = $H(j\omega) \cdot \hat{u}$

$$\Rightarrow \text{transfer function in phasor} = \frac{\text{output phasor}}{\text{input phasor}} = H(j\omega)$$

$$= H(s) \Big|_{s=j\omega}$$

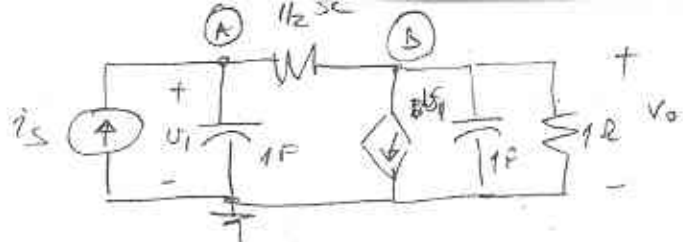

$$I_s = sV_A + 2(V_A - V_B) = (s+2)V_A - 2V_B$$

$$0 = 2(V_B - V_A) + V_A + sV_B + V_B = -V_A + (s+3)V_B$$

$$\Rightarrow V_A = (s+3)V_B$$

$$I_s = [(s+2)(s+3) - 2] V_B = [s^2 + 5s + 6 - 2] V_B = (s^2 + 5s + 4) V_B$$

$$\Rightarrow \boxed{H(s) = \frac{V_B}{I_s} = \frac{1}{s^2 + 5s + 4}} \quad *$$

$$\textcircled{*} \quad i_s(t) = u(t) \Rightarrow V_B(s) = H(s) \cdot i_s(s) = \frac{1}{s^2 + 5s + 4} \cdot \frac{1}{s}$$

$$= \frac{1}{s(s+1)(s+4)} = \frac{k_1}{s} + \frac{k_2}{s+1} + \frac{k_3}{s+4}$$

$$k_1 = s V_B(s) \Big|_{s=0} = \frac{1}{4}$$

$$k_2 = (s+1) V_B(s) \Big|_{s=-1} = -\frac{1}{3}$$

$$k_3 = (s+4) V_B(s) \Big|_{s=-4} = \frac{1}{-4-3} = -\frac{1}{7}$$

$$\boxed{v_o(t) = \left(\frac{1}{4} - \frac{1}{3} e^{-t} + \frac{1}{12} e^{-4t} \right) \quad t \geq 0}$$

ZERO-STATE
RESPONSE

→ this is also the step response

→ impulse response = $\mathcal{L}^{-1}\{H(s)\}$

$$H(s) = \frac{1}{s^2 + 5s + 4} = \frac{k_1}{s+1} + \frac{k_2}{s+4}$$

$$k_1 = \frac{1}{3} \quad k_2 = -\frac{1}{3}$$

$$h(t) = \frac{1}{3} e^{-t} - \frac{1}{3} e^{-4t}$$

STEP RESPONSE

$$Y(s) = H(s) U(s)$$

step response: zero-state solution when $u(t) = 1(t) \Rightarrow U(s) = \frac{1}{s}$.

$$Y(s) = \frac{1}{s} H(s) \quad \Rightarrow \quad y(t) = \int_0^t h(\tau) d\tau \quad (\Rightarrow \quad \dot{y}(t) = h(t) \text{ (generalized derivative)})$$


$$h(t) = \mathcal{L}^{-1}\{H(s)\}$$

= impulse response.

$$H(s) = \frac{2}{s^2 + 2s + 2} = \frac{2}{[s - (-1 + j)][s - (-1 - j)]} = \frac{k}{s - (-1 + j)} + \frac{k^*}{s - (-1 - j)}$$

$$k = \left. [s - (-1 + j)] H(s) \right|_{s = -1 + j} = \frac{2}{-1 + j - (-1 - j)} = \frac{2}{2j} = \frac{1}{j} = -j = 1e^{-j90^\circ}$$
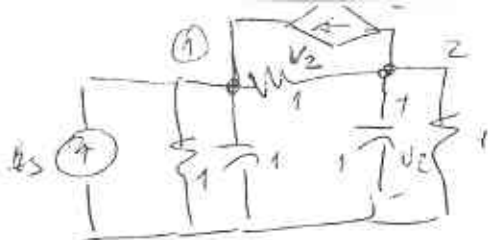
$$h(t) = \mathcal{L}^{-1}\{H(s)\} = 2e^{-t} \cos(t - 90^\circ)$$



$$\begin{bmatrix} s+2 & -1 \\ -1 & s+2 \end{bmatrix} \begin{bmatrix} E_1 \\ E_2 \end{bmatrix} = \begin{bmatrix} I_s + E_2 \\ -E_2 \end{bmatrix}$$

$$\rightarrow \begin{bmatrix} s+2 & -2 \\ -1 & s+3 \end{bmatrix} \begin{bmatrix} E_1 \\ E_2 \end{bmatrix} = \begin{bmatrix} I_s \\ 0 \end{bmatrix}$$

$$\rightarrow \Delta(s) = (s+2)(s+3) - 2 = s^2 + 5s + 6 - 2 = s^2 + 5s + 4$$

$$\begin{bmatrix} E_1 \\ E_2 \end{bmatrix} = \frac{1}{(s+1)(s+4)} \begin{bmatrix} s+3 & 2 \\ 1 & s+2 \end{bmatrix} \begin{bmatrix} I_s \\ 0 \end{bmatrix}$$

$$E_2 = \frac{1}{(s+1)(s+4)} I_s$$

$$H(s) = \frac{1}{(s+1)(s+4)}$$

when $i_s(t) = \delta(t) \rightarrow I_s = 1$

$$E_2 = \frac{1}{(s+1)(s+4)} = \frac{k_1}{s+1} + \frac{k_2}{s+4}$$

$$k_1 = (s+4)E_2 \Big|_{s=-1} = \frac{1}{3}$$

$$k_2 = (s+4)E_2 \Big|_{s=-4} = -\frac{1}{3}$$

$$e_2(t) = \frac{1}{3} e^{-t} - \frac{1}{3} e^{-4t} \quad \text{impulse response}$$

when $i_s(t) = 1(t) \rightarrow I_s = \frac{1}{s}$

$$\rightarrow I_s = \frac{1}{s}$$

$$E_2 = \frac{1}{s(s+1)(s+4)} = \frac{k_1}{s} + \frac{k_2}{s+1} + \frac{k_3}{s+4}$$

$$k_1 = sE_2 \Big|_{s=0} = \frac{1}{4}$$

$$k_2 = (s+1)E_2 \Big|_{s=-1} = -\frac{1}{3}$$

$$k_3 = (s+4)E_2 \Big|_{s=-4} = \frac{1}{12}$$

$$e_2(t) = \frac{1}{4} - \frac{1}{3} e^{-t} + \frac{1}{12} e^{-4t} \quad \text{step response}$$

$\Rightarrow$

step

$$\text{impulse response} = \frac{d}{dt} (\text{step response})$$

why?

$$E_{2im} = H(s)$$

$$E_{2st} = \frac{1}{s} H(s)$$

step impulse

step response!

$\Rightarrow$ use integral rule.

$$\Rightarrow E_{2st} = \int_0^t e_{2im}(\tau) d\tau$$