


$$Z(s) = \frac{V(s)}{I(s)}$$

impedance in s domain
→ a network fn. where initial conditions are set to zero.

$$Y(s) = \frac{I(s)}{V(s)}$$


admittance in s domain
a network fn.

$$Z = \frac{1}{Y}$$

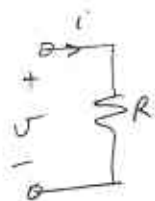

$$\Rightarrow Z_R(s) = R$$


$$Y_R(s) = \frac{1}{R}$$

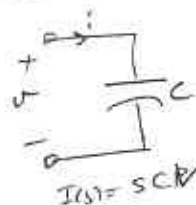

$$Y_C(s) = sC$$

$$Z_C(s) = \frac{1}{sC}$$

$$I(s) = sC V(s)$$

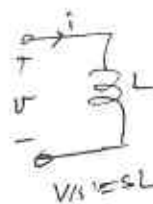


$$Z_L(s) = sL$$

$$Y_L(s) = \frac{1}{sL}$$

$$V(s) = sL I(s)$$

Series Connection:

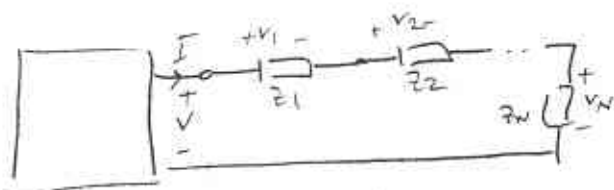


$$V = V_1 + \dots + V_N$$

$$I = I_1 = \dots = I_N$$


$$V_j = Z_j I_j$$

$$V = (Z_1 + \dots + Z_N) I$$
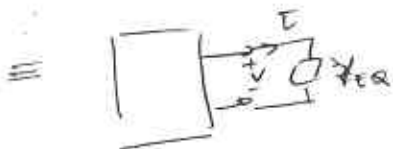
$$Z_{eq} = \frac{V}{I} = Z_1 + \dots + Z_N$$



* PARALLEL CONNECTION

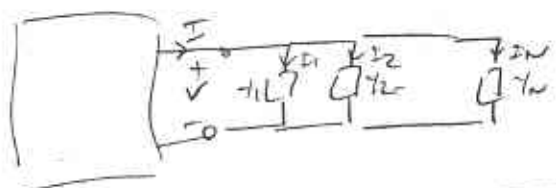


$$I = I_1 + \dots + I_N$$

$$V = V_1 = \dots = V_N$$


$$I_j = Y_j V_j$$

$$I = (Y_1 + \dots + Y_N) V$$

$$Y_{eq} = Y_1 + \dots + Y_N$$

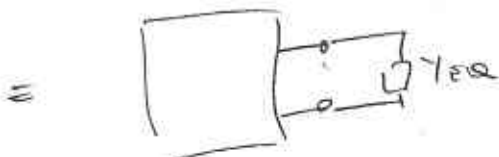


VOLTAGE DIVISION

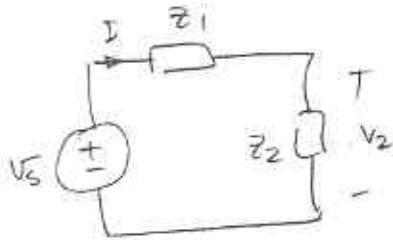

$$\left. \begin{aligned} V_s &= (Z_1 + Z_2) I \\ V_2 &= Z_2 I \end{aligned} \right\} \Rightarrow \boxed{V_2 = \frac{Z_2}{Z_1 + Z_2} V_s}$$


CURRENT DIVISION

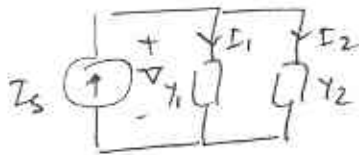

$$\left. \begin{aligned} I_s &= (Y_1 + Y_2) V \\ I_1 &= Y_1 V \end{aligned} \right\} \Rightarrow \boxed{I_1 = \frac{Y_1}{Y_1 + Y_2} I_s = \frac{Z_2}{Z_1 + Z_2} I_s}$$

EXAMPLE P. 493

$$\Rightarrow \text{I.C.} = 0$$

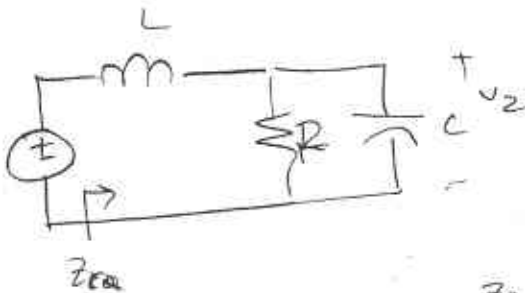


$$Z_1 = sL \quad Z_2 = \frac{R \cdot 1/sC}{R + 1/sC} = \frac{R}{sCR + 1}$$

$$Z_1 + Z_2 = sL + \frac{R}{sCR + 1} = \frac{s^2 LCR + sL + R}{sCR + 1}$$

$$V_2 = \frac{Z_2}{Z_1 + Z_2} V_s = \frac{R/sCR + 1}{\frac{s^2 LCR + sL + R}{sCR + 1}} V_s = \frac{R}{s^2 LCR + sL + R} \cdot V_s$$

EXERCISE P. 494

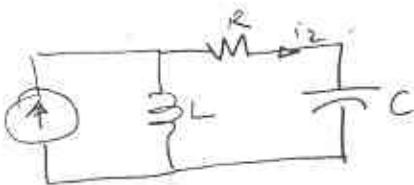

$$Z_2 = R + \frac{1}{sC} = \frac{sCR + 1}{sC} \quad Y_2 = \frac{sC}{sCR + 1}$$


$$Z_1 = sL \Rightarrow Y_1 = 1/sL$$

$$Z_1 + Z_2 = sL + \frac{sCR + 1}{sC}$$

$$I_2 = \frac{Y_2}{Y_1 + Y_2} I_s$$

$$= \frac{Z_1}{Z_1 + Z_2} I_s$$

$$= \frac{s^2 LC + sCR + 1}{sC}$$

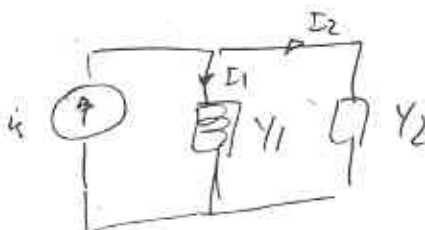

$$\boxed{I_2 = \frac{sL}{\frac{s^2 LC + sCR + 1}{sC}} = \frac{s^2 LC}{s^2 LC + sCR + 1} I_s}$$

SUPERPOSITION IN S DOMAIN:

89


any solution = zero-state solution + zero-input solution

zero-state solution = initial conditions are zero
only input is effective

zero-input solution = inputs are zero, only initial conditions are effective.

How to DEAL WITH THE INITIAL CONDITIONS:

capacitor

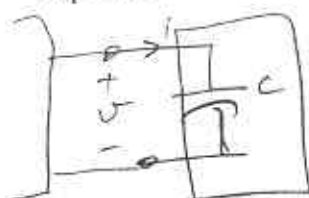

$$i = C \frac{dv}{dt} \Rightarrow$$

$$I(s) = sC V(s) - C v(0)$$

$\Rightarrow$




in time domain

in s domain


or equivalently we may use

$$V(s) = \frac{1}{sC} I(s) + \frac{v(0)}{s}$$

$\Rightarrow$

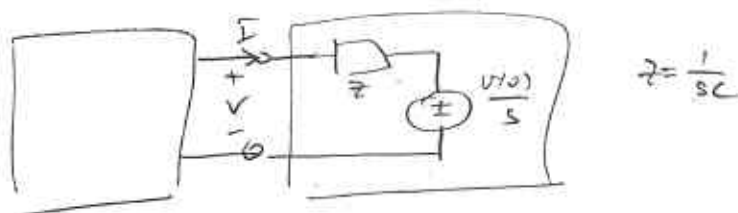


for inductor

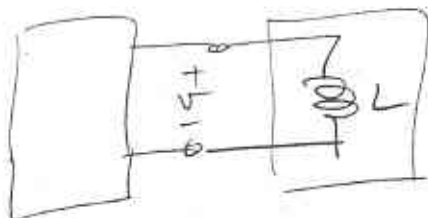


$$v = L \frac{di}{dt} \Rightarrow$$

$$V(s) = sL I(s) - L i(0)$$

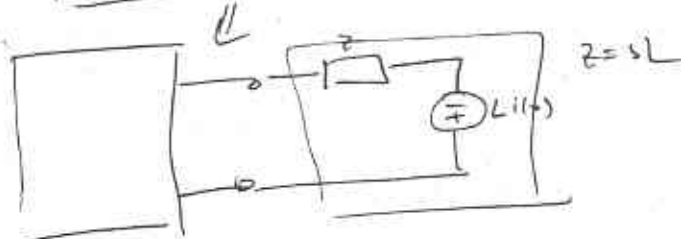

or equivalently
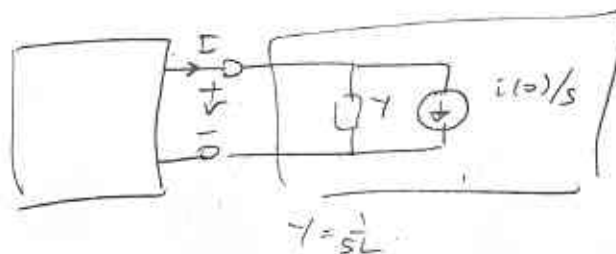
$$I(s) = \frac{1}{sL} V(s) + \frac{i(0)}{s} \Rightarrow$$




These transformations are known as initial condition transformations.


Application of superposition is as follows:

- Apply an appropriate initial condition transformation
- Treat initial conditions as equivalent independent sources in s-domain
- Apply the superposition to this circuit in s-domain
- The contributions of equivalent sources due to initial conditions give the zero-input response
- The contributions of independent sources alone give the zero-state response.


EXAMPLE: p. 488

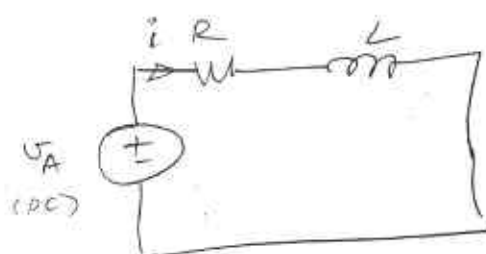

$i_L(0)$ is given

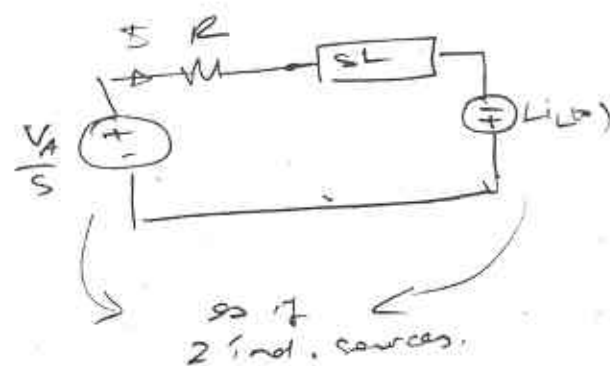


Contribution of V_A :

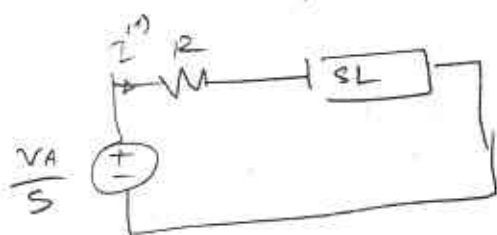

$$I = \frac{V_A/s}{R/s + sL} = \frac{V_A/L}{s(s + R/L)}$$

This is zero-state solution.

Contribution of $i_L(0)$:

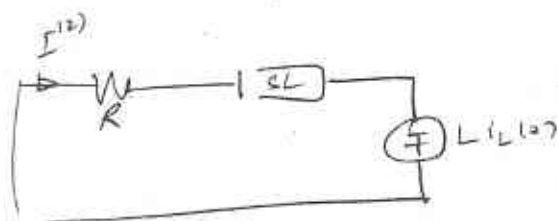

$$I^{(2)} = \frac{L i_L(0)}{R/s + sL} = \frac{i_L(0)}{s + R/L}$$

This is the zero-input solution.

$$I(s) = I^{(1)} + I^{(2)} = \underbrace{\frac{V_A/L}{s(s + R/L)}}_{\text{zero-state}} + \underbrace{\frac{i_L(0)}{s + R/L}}_{\text{zero-input}}$$

$$I(s) = \frac{k_1}{s} + \frac{k_2}{s + R/L} + \frac{i_L(0)}{s + R/L}$$

$$k_1 = s I(s) \Big|_{s=0} = V_A/R$$


$$k_2 = (s + R/L) I(s) \Big|_{s=-R/L} = -V_A/R$$

$$i(t) = \underbrace{\left\{ \frac{V_A}{R} - \frac{V_A}{R} e^{-R/L t} \right\}}_{\text{zero-state}} + \underbrace{i_L(0) e^{-R/L t}}_{\text{zero-input}} \quad \text{u(t)}$$

particular (forced) homogeneous (natural)

Example (p. 498)

in steady-state C → open
L → short

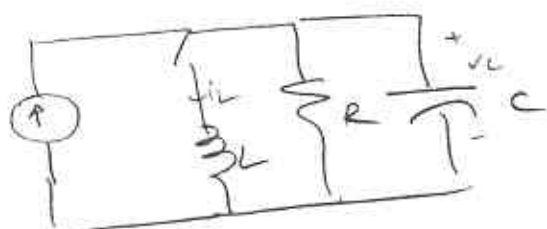

$$\Rightarrow V_C(0) = R I_A$$

$$i_L(0) = 0$$

Time domain




$$Y(s) = \frac{1}{sL} + \frac{1}{R} + sC = \frac{s^2 LCR + sL + R}{sLR}$$



$$V^{(1)}(s) = \frac{I_A/s}{Y(s)} = \frac{I_A/s \cdot sLR}{s^2 LCR + sL + R} = \frac{I_A L C}{s^2 + s \frac{1}{CR} + \frac{1}{LC}}$$

zero-state response

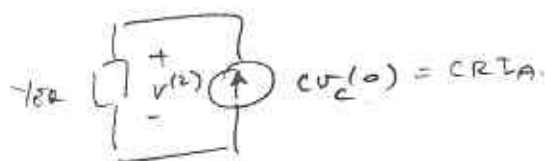


$$V^{(2)}(s) = \frac{C R I_A}{Y(s)} = \frac{C R I_A \cdot sLR}{s^2 LCR + sL + R}$$

$$= \frac{R I_A s}{s^2 + s \frac{1}{CR} + \frac{1}{LC}} \Rightarrow \text{zero-input solution}$$


$$I(s) = V^{(1)} + V^{(2)} = \frac{R I_A s + I_A L C}{s^2 + s \frac{1}{CR} + \frac{1}{LC}}$$

THEVENIN - NORTON EQUIVALENT CIRCUITS


92

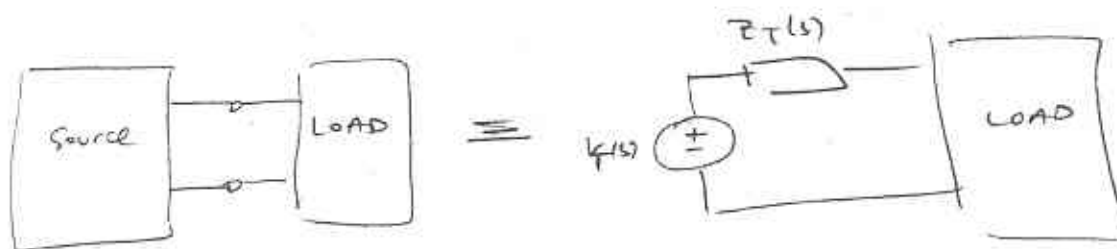

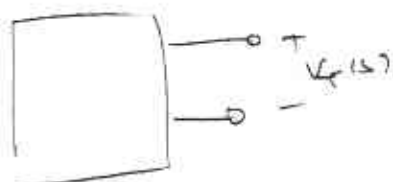Finding $V_T(s)$ and $Z_T(s)$ are the same as before.



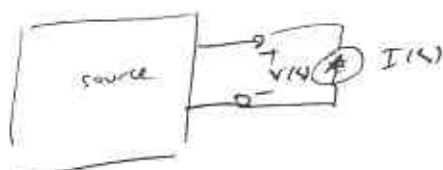
open circuit - keep all ind. sources inside the source part (possibly initial cond. as well)



set all ind. sources inside source part (including the initial cond.)


$$Z_T(s) = \frac{V_T(s)}{I(s)}$$

NORTON: (SIMILAR)

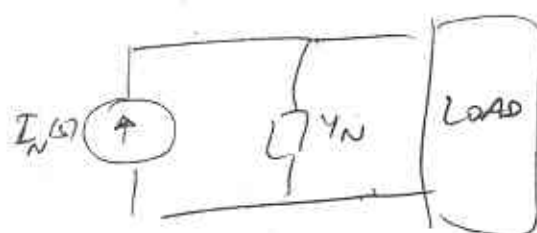

$$V_T(s) = I_N(s) / Y_N$$


$$Z_T = 1 / Y_N$$

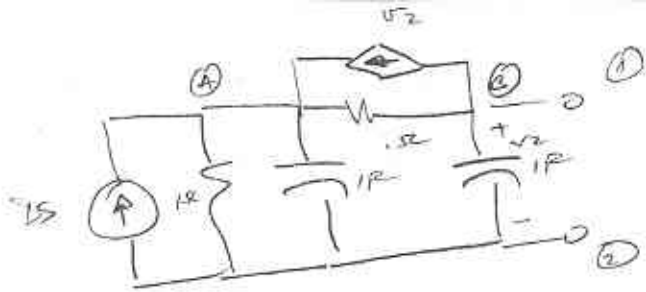

$$I_s = (s+2)V_A - V_B - V_B = (s+2)V_A - 2V_B$$

$$0 = (s+2)V_B - V_A + V_B = (s+2)V_B - V_A \Rightarrow V_A = (s+2)V_B$$

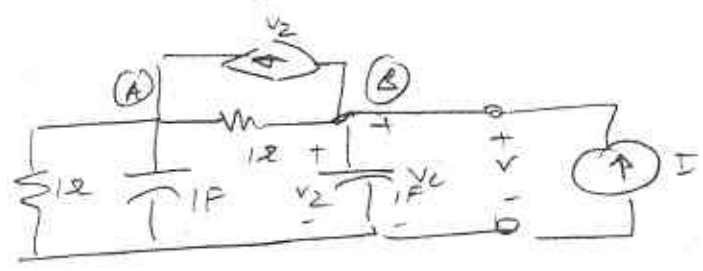
$$\Rightarrow I_s = [(s+2)(s+2) - 2] V_B = (s^2 + 4s + 2) V_B \Rightarrow \boxed{V_B = \frac{I_s}{s^2 + 4s + 2}}$$



$$(s+2)V_A - V_B = V_B = V \Rightarrow \boxed{V_A = \frac{2}{s+2} V}$$

$$I = (s+1)V_B - V_A + V_B = (s+2)V_B - V_A = (s+2)V - \frac{2}{s+2}V = \frac{s^2 + 4s + 2}{s+2} V$$
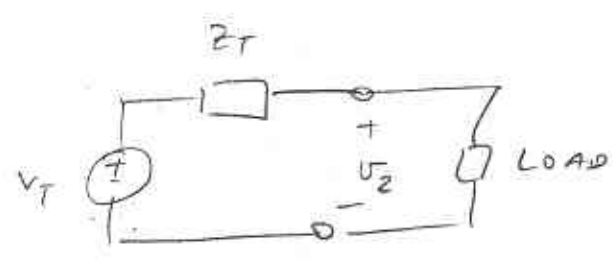
$$Z_T = \frac{V}{I} = \frac{s+2}{s^2 + 4s + 2} \Rightarrow \boxed{Z_T = \frac{s+2}{s^2 + 4s + 2}}$$



Let Load = 1R

$$\Rightarrow V_2 = \frac{1}{1 + Z_T} V_T$$

$$V_2 = \frac{1}{1 + \frac{s+2}{s^2 + 4s + 2}} \cdot \frac{I_s}{s^2 + 4s + 2} = \frac{I_s}{s^2 + 5s + 4} \Rightarrow \boxed{\frac{V_2}{I_s} = \frac{1}{s^2 + 5s + 4}} \checkmark$$