
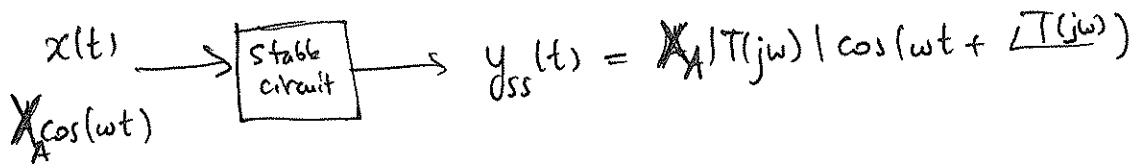


Recall from last lecture:



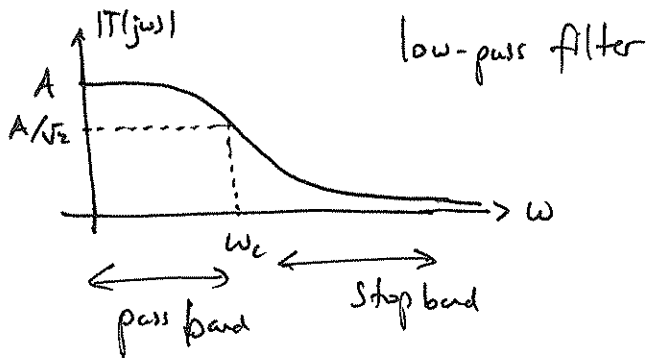


We would like to see the function $|T(j\omega)|$ as a function of ω (same for $\angle T(j\omega)$).

Examples:



ω_c : cut-off frequency

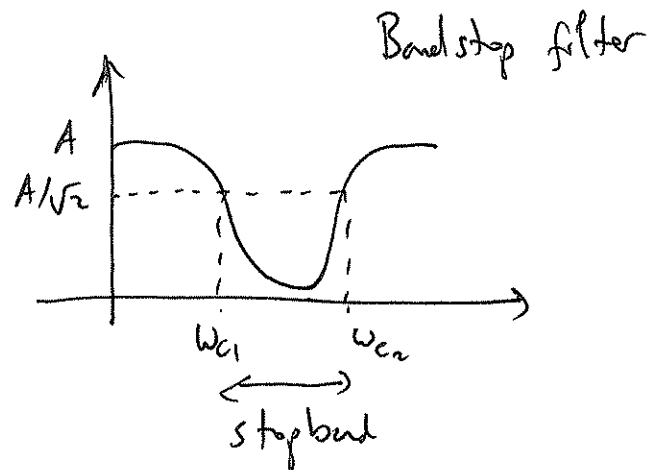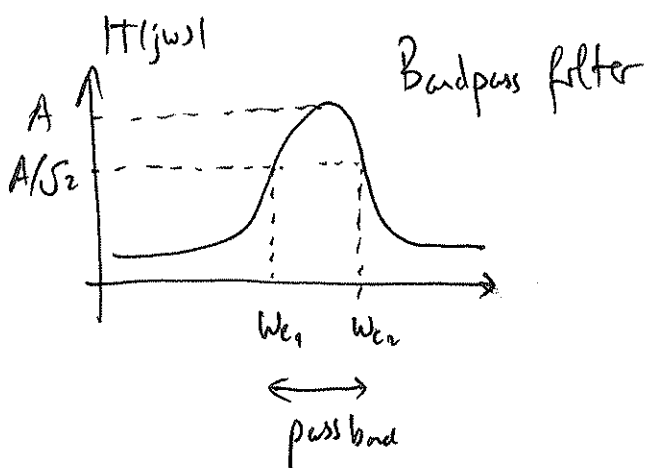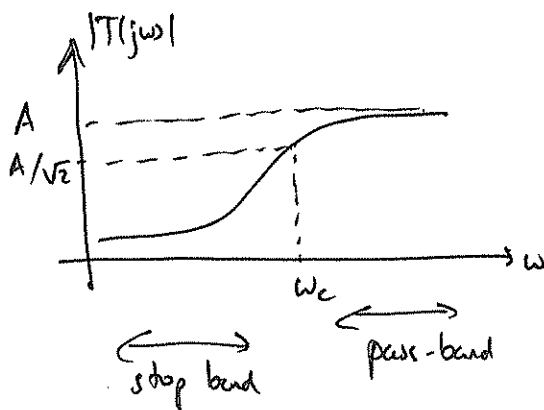

Bode Plots : graph of $20 \log_{10} |T(j\omega)|$ and $\angle T(j\omega)$
in log-scale of ω


$$20 \log_{10} \frac{A}{\sqrt{2}} = 20 \log_{10} A - 20 \log_{10} \sqrt{2} = 20 \log_{10} A - 3 \text{ dB}$$

$$|T(j\omega)|_{\text{dB}} = 20 \log |T(j\omega)| \text{ in dB}$$


Bode Plots of First order low-pass and highpass filters :

$$T(s) = \frac{K}{s + \alpha} = \frac{K/\alpha}{s/\alpha + 1} \quad T(j\omega) = \frac{K/\alpha}{1 + j\omega/\alpha} \quad K > 0$$

$$|T(j\omega)| = \frac{K/\alpha}{\sqrt{1 + \omega^2/\alpha^2}} \quad \angle T(j\omega) = -\tan^{-1} \frac{\omega}{\alpha}$$

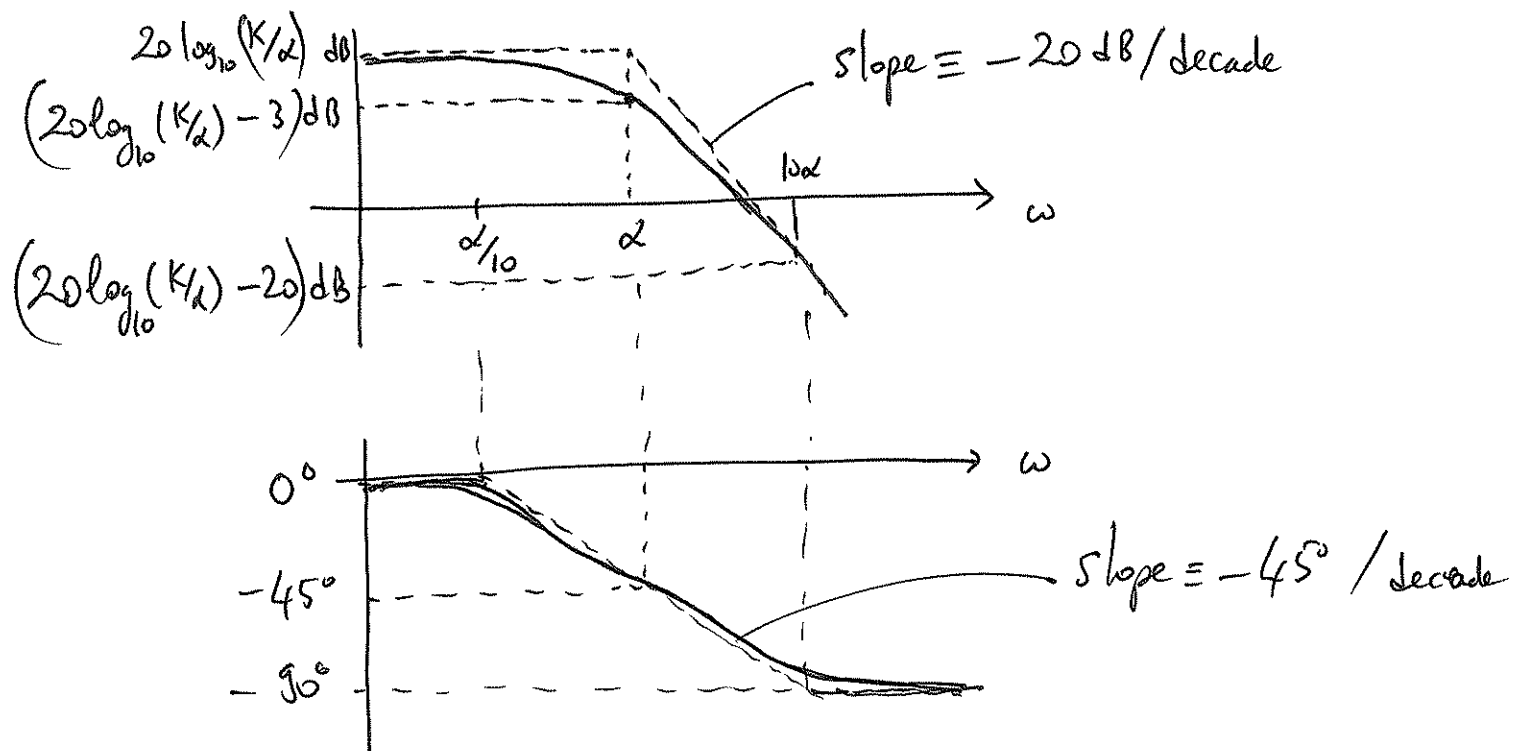

Example of a low pass filter:

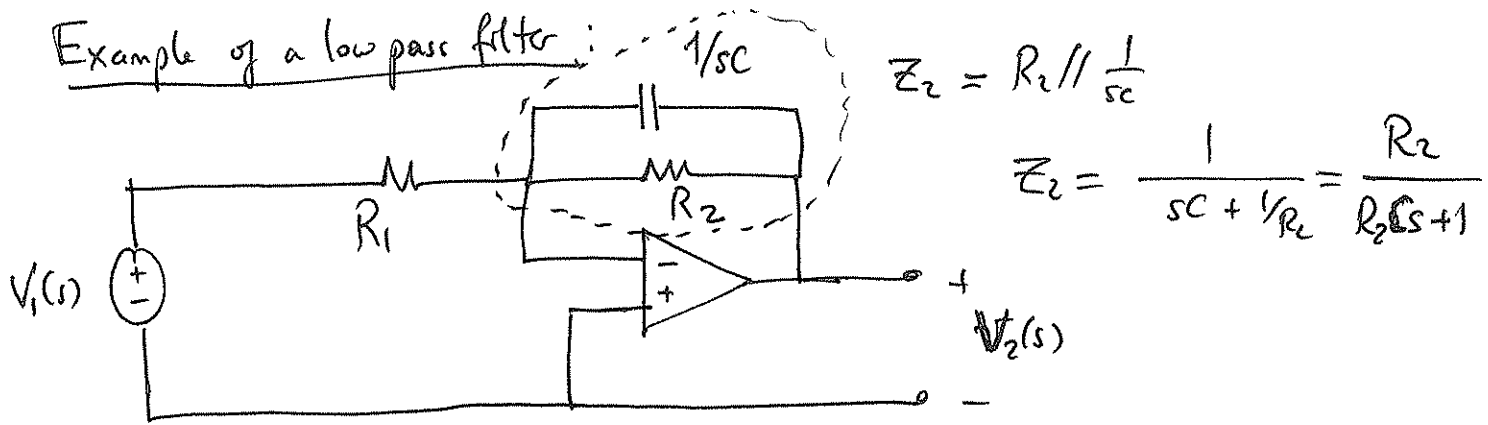

$$V_2(s) = - \frac{Z_2(s)}{R_1} = - \frac{R_2/R_1}{R_2 s + 1} = - \frac{1/C R_1}{s + 1/R_2 C}$$


$$K = (-1/C R_1) \quad |K| = \frac{1}{R_1 C} \quad \angle K = -180^\circ$$

$$\alpha = 1/R_2 C \quad (K/\alpha) = -R_2/R_1$$

$$|T(j\omega)| = \frac{R_2/R_1}{\sqrt{1 + \omega^2 (R_2 C)^2}}$$

cut-off freq $\omega_c = 1/R_2 C$
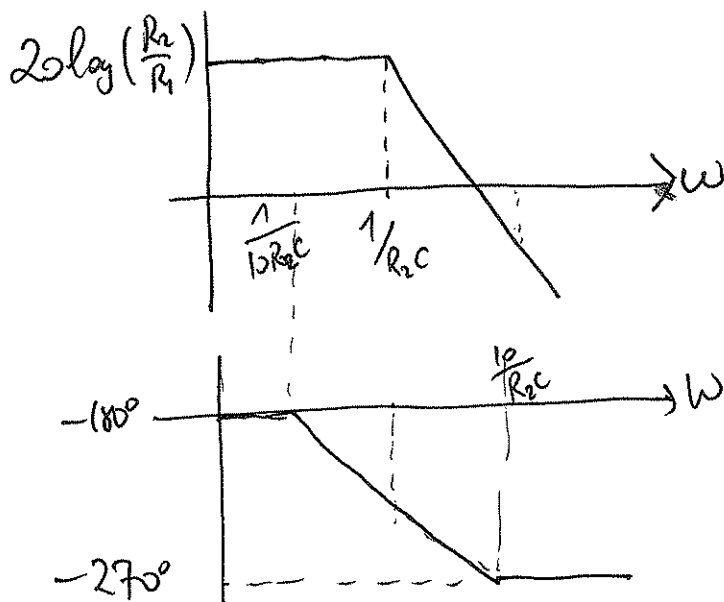
$$\angle T(j\omega) = -180^\circ - \tan^{-1} \omega R_2 C$$



Example select R_1, R_2, C

s.t. passband gain = 4
cut off freq = 100

$$R_2/R_1 = 4$$

$$\frac{1}{R_2 C} = 100$$

$$C = \frac{1}{100 R_2} \quad R_1 = \frac{R_2}{4}$$

Let $R_2 = 1k\Omega$ $R_1 = 250\Omega$


$$C = 10\mu F$$

First-Order Highpass Filter

$$T(s) = \frac{K s}{s + \alpha} \qquad |T(j\omega)| = \frac{|K| \omega}{\sqrt{1 + \omega^2/\alpha^2}}$$


$$\alpha > 0$$
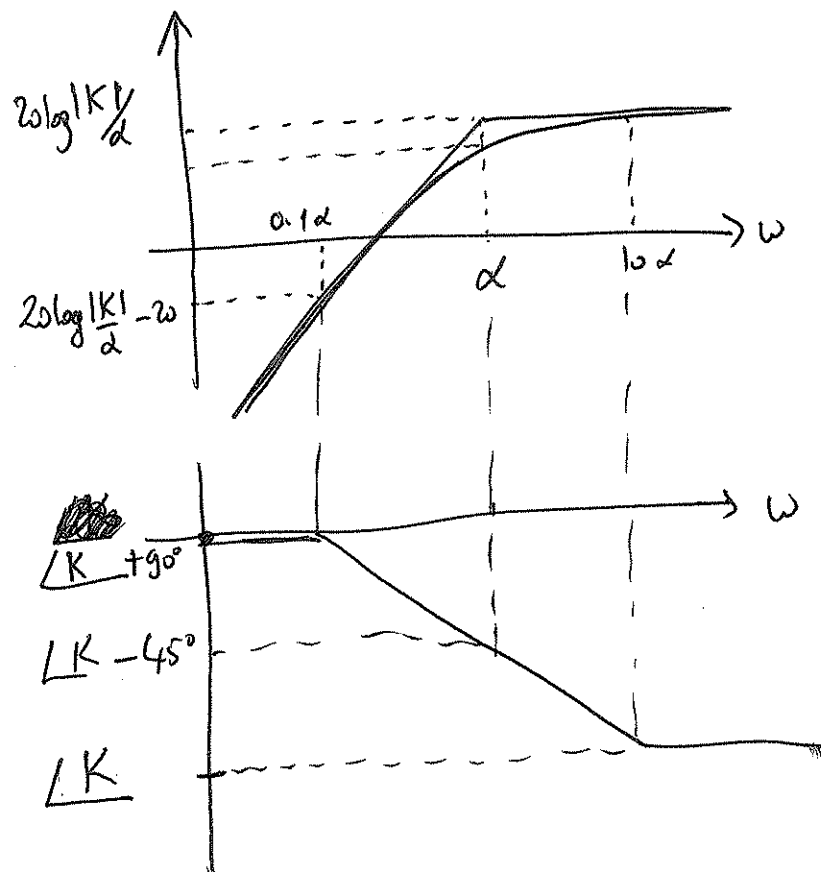
$$\angle T(j\omega) = \angle K + 90^\circ - \tan^{-1} \frac{\omega}{\alpha}$$





$$V_2(s) = \frac{sL}{R + sL} V_1(s)$$

Example

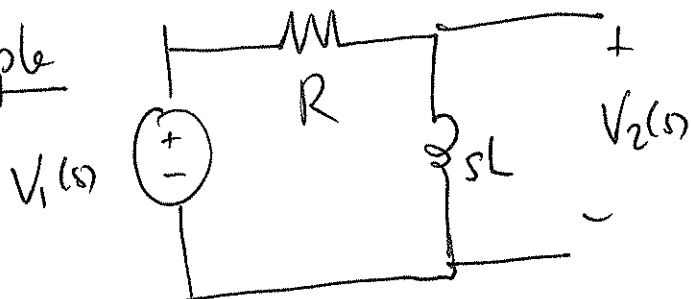

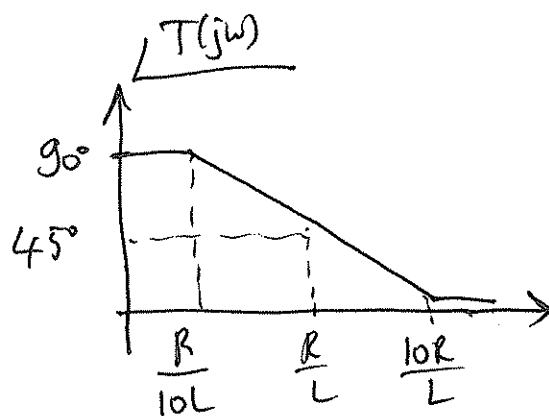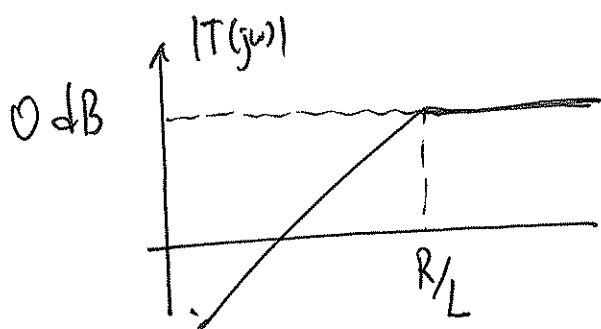
$$T(s) = \left(\frac{L/R s}{1 + sL/R} \right)$$



Bandpass-filter

$$T(s) = T_1(s) T_2(s) \quad (\text{no loading}) \quad \text{Cascade stages}$$

$$20 \log |T(j\omega)| = \underbrace{20 \log |T_1(j\omega)|}_{\text{High Pass}} + \underbrace{20 \log |T_2(j\omega)|}_{\text{low-pass}}$$

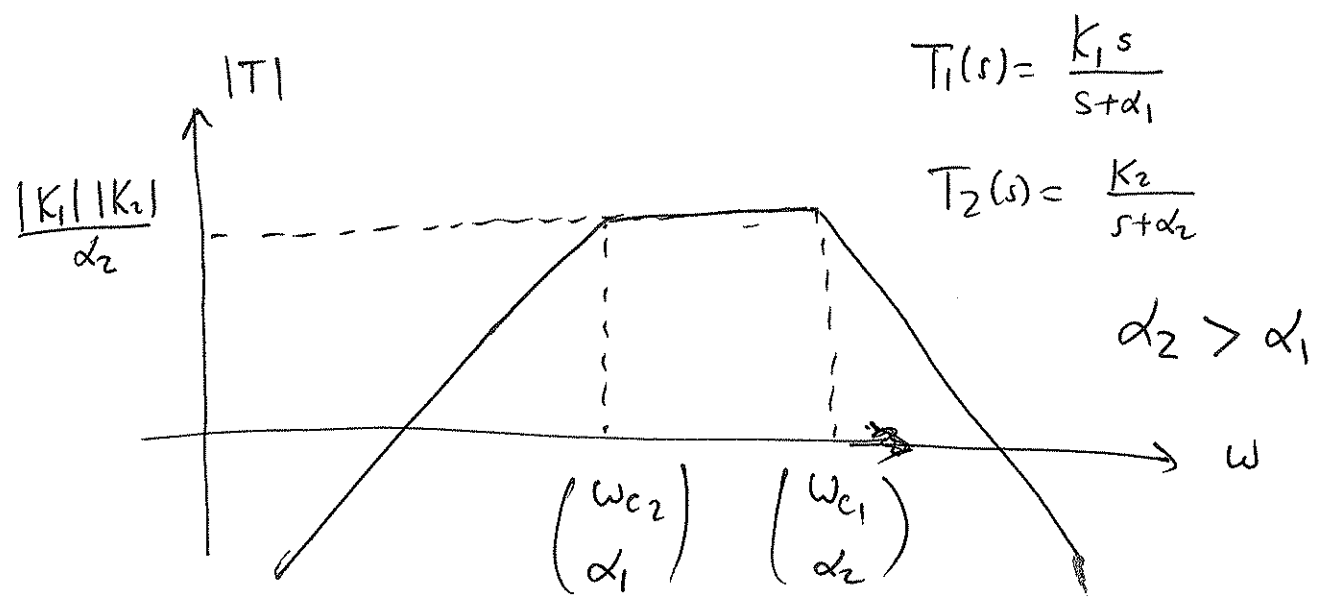

low freq: $|T(j\omega)| \rightarrow \frac{|K_1| \omega}{\alpha_1} \cdot \frac{|K_2|}{\alpha_2} = \frac{|K_1| |K_2|}{\alpha_1 \alpha_2} \omega$

high freq: $|T(j\omega)| \rightarrow \frac{|K_1| \cancel{\omega}}{\cancel{\omega}} \cdot \frac{|K_2|}{\omega} = \frac{|K_1| |K_2|}{\omega}$

mid freq. $|T(j\omega)| \rightarrow \frac{|K_1| \cdot |K_2|}{\alpha_2}$

Band-stop Filter

Parallel stages $T_1(s) = \frac{K_1 s}{s + \alpha_1}$ $T_2(s) = \frac{K_2}{s + \alpha_2}$

$$T(s) = T_1(s) + T_2(s) \quad \alpha_2 < \alpha_1$$

low freq: $\omega \ll \alpha_2$

$$|T(j\omega)| \cong \frac{|K_2|}{\alpha_2}$$


high freq: $\omega \gg \alpha_1$

$$|T(j\omega)| \cong |K_1|$$


Choose $|K_1| = \frac{|K_2|}{\alpha_2}$
 $\alpha_2 = \frac{|K_2|}{|K_1|}$

mid freq: $\alpha_2 \ll \omega \ll \alpha_1$

$$|T(j\omega)| = \frac{|K_1| \omega}{\alpha_1} + \frac{|K_2|}{\omega}$$

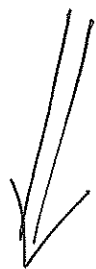

intersection frequency $\frac{|K_1| \omega_0}{\alpha_1} = \frac{|K_2|}{\omega_0} \Rightarrow \omega_0 = \sqrt{\alpha_1 \alpha_2}$

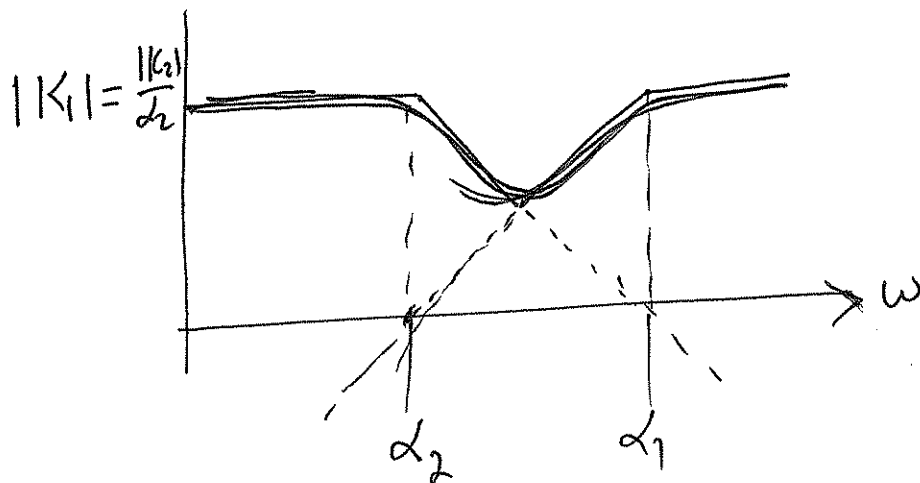


Example : Design a bandpass circuit with a passband gain of 10 and cut-off frequencies at 20Hz and 20kHz

$$20\text{Hz} \rightarrow \omega_1 = 2\pi \times 20 = 40\pi \text{ rad/sec} = \alpha_1$$

$$20\text{kHz} \rightarrow \omega_2 = 40000\pi \text{ rad/sec} = \alpha_2$$

$$\frac{|K_1 K_2|}{\alpha_2} = 10$$
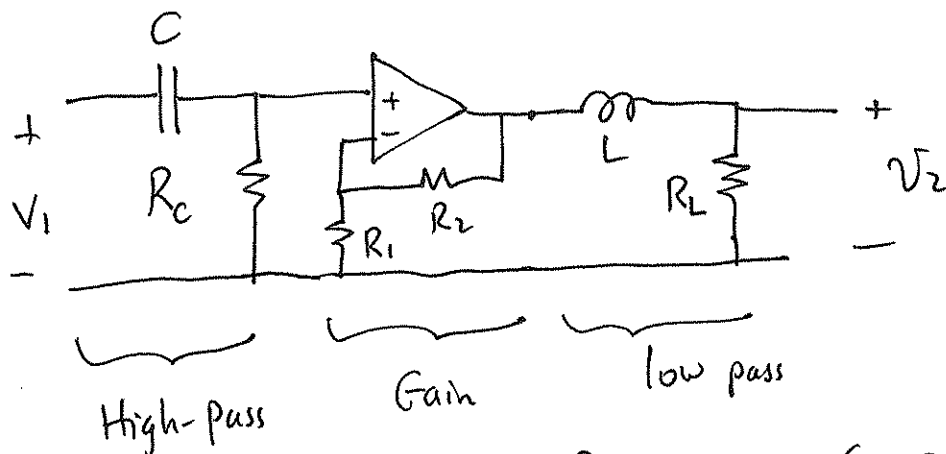
$$T(j\omega) = \frac{K_1 s}{s + \alpha_1} \cdot \frac{K_2}{s + \alpha_2} = \left(\frac{K_1 K_2}{\alpha_2} \right) \left(\frac{s}{s + \alpha_1} \right) \left(\frac{\alpha_2}{s + \alpha_2} \right)$$



$$T_1(s) = \frac{R_c}{R_c + \frac{1}{sC}} = \frac{R_c s}{R_c s + 1} = \left(\frac{s}{s + 1/R_c C} \right)$$

$$\alpha_1 = 1/R_c C = 40\pi$$

Gain: $\frac{R_2 + R_1}{R_1} > 1$


choose $\frac{R_2 + R_1}{R_1} = 10$

$$T_2(s) = \frac{R_L}{sL + R_L} = \frac{R_L/L}{s + R_L/L}$$

$$\alpha_2 = R_L/L = 40000\pi$$

RLC circuits Bode Plots

Series RLC band-pass circuit

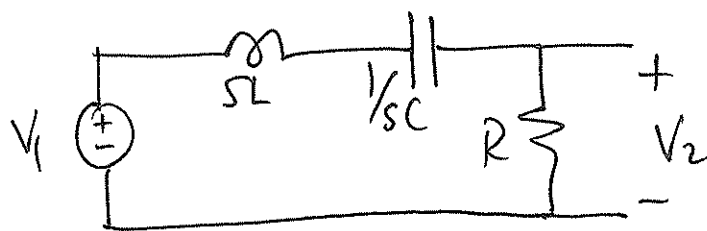

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\frac{2\xi}{\omega_0} = RC \quad \xi = \frac{R}{2} \sqrt{\frac{C}{L}}$$

$$T(s) = \frac{R}{sL + \frac{1}{sC} + R} = \frac{RCs}{LCs^2 + RCs + 1} = \frac{2\xi s/\omega_0}{s^2/\omega_0^2 + 2\xi s/\omega_0 + 1}$$


$$|T(j\omega)| = \frac{2\xi \frac{\omega}{\omega_0}}{\left[\left(1 - \frac{\omega^2}{\omega_0^2}\right)^2 + \left(2\xi \frac{\omega}{\omega_0}\right)^2 \right]^{1/2}} = \frac{1}{\left[1 + \left(\frac{1 - \omega^2/\omega_0^2}{2\xi \omega/\omega_0} \right)^2 \right]^{1/2}}$$

~~When~~ When $\omega \ll \omega_0$

$$|T(j\omega)| \rightarrow 2\xi \frac{\omega}{\omega_0} = RC\omega$$

When $\omega \gg \omega_0$

$$|T(j\omega)| \rightarrow \frac{RC\omega}{\omega^2 LC} \rightarrow \left(\frac{R}{L} \frac{1}{\omega} \right)$$

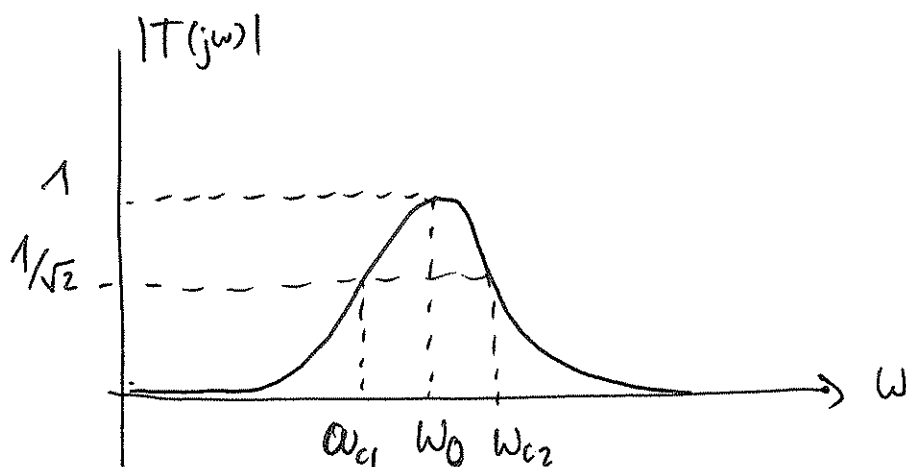


$$\omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_{c2} = +\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_{c1} \omega_{c2} = \frac{1}{LC} = \omega_0^2$$
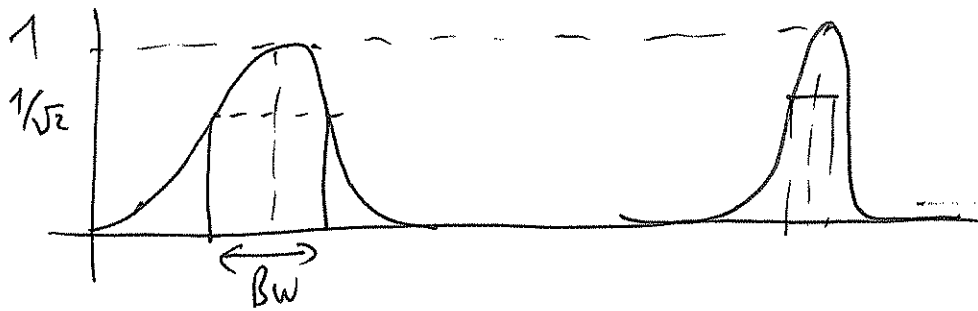
$$\text{Quality factor} = Q = \frac{\omega_0}{BW}$$



In our case $BW = \omega_{c2} - \omega_{c1} = \frac{R}{L}$ $\omega_0 = \frac{1}{\sqrt{LC}}$

$$Q = \frac{1/\sqrt{LC}}{R/L} = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{2\zeta}$$

Bode Plots with real poles and zeros

$$T(s) = \frac{Ks(s+\alpha_1)}{(s+\alpha_2)(s+\alpha_3)}$$


zeros at $s=0$, $s=-\alpha_1$
poles at $s=-\alpha_2$, $s=-\alpha_3$

$$T(j\omega) = \frac{(K\alpha_1)}{(\alpha_2\alpha_3)} \frac{s(s/\alpha_1+1)}{(s/\alpha_2+1)(s/\alpha_3+1)}$$


$$|T(j\omega)| = \left| \frac{K\alpha_1}{\alpha_2\alpha_3} \right| \frac{|j\omega| \cdot |j\omega/\alpha_1+1|}{|j\omega/\alpha_2+1| \cdot |j\omega/\alpha_3+1|} = \underbrace{\left| \frac{K\alpha_1}{\alpha_2\alpha_3} \right|}_{K_0} \frac{\omega \sqrt{1+(\omega/\alpha_1)^2}^{M_1}}{\underbrace{\sqrt{1+(\omega/\alpha_2)^2}}_{M_2} \underbrace{\sqrt{1+(\omega/\alpha_3)^2}}_{M_3}}$$

$$20\log|T(j\omega)| = 20\log|K_0| + 20\log\omega + \underbrace{20\log}_{M_1} - \underbrace{20\log}_{M_2} - \underbrace{20\log}_{M_3}$$


$20\log|K_0|$

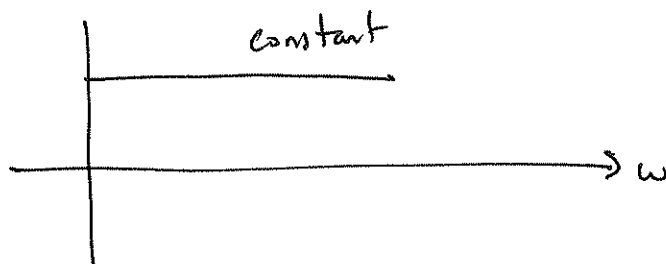

$20\log\omega$

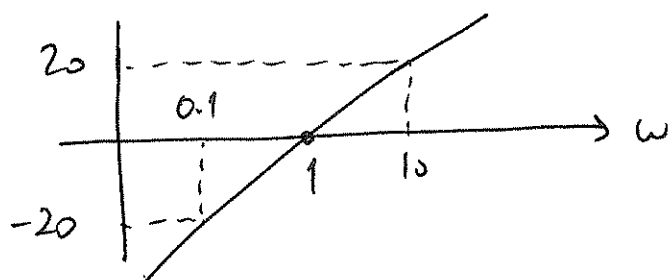

$20\log M_1$

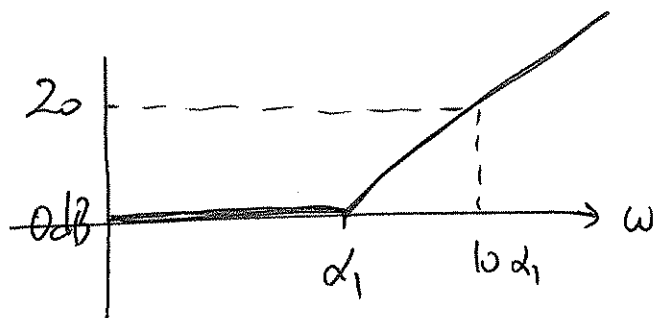


Example: $T(s) = \frac{10 s^2}{(s+40)(s+200)} = \left(\frac{10}{40 \times 200}\right) \frac{s^2}{(1+s/40)(1+s/200)}$ 109

$$T(j\omega) = \left(\frac{-1}{800}\right) \frac{\omega^2}{(1+j\omega/40)(1+j\omega/200)}$$

$$20 \log \frac{1}{800} = -20 \log 800 = -20 (\log 8 + \log 100)$$
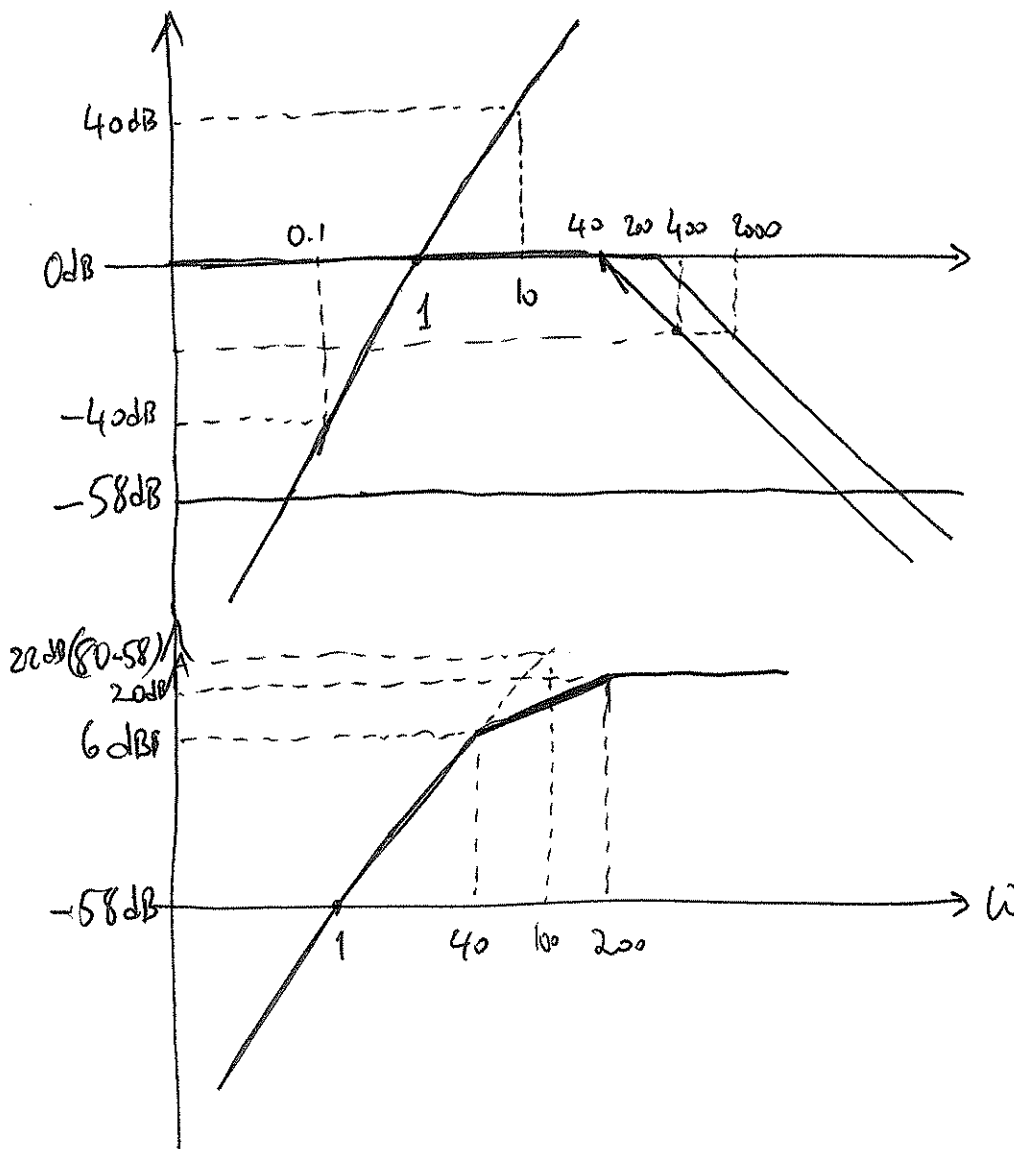
$$= \underbrace{-20 \log 2^3}_{-3 \times 6} + \underbrace{(-20 \log 100)}_{-40 \text{ dB}} = -58 \text{ dB}$$




Phase

$$\angle T(j\omega) = -\pi$$

$$-\tan^{-1}\left(\frac{\omega}{40}\right)$$

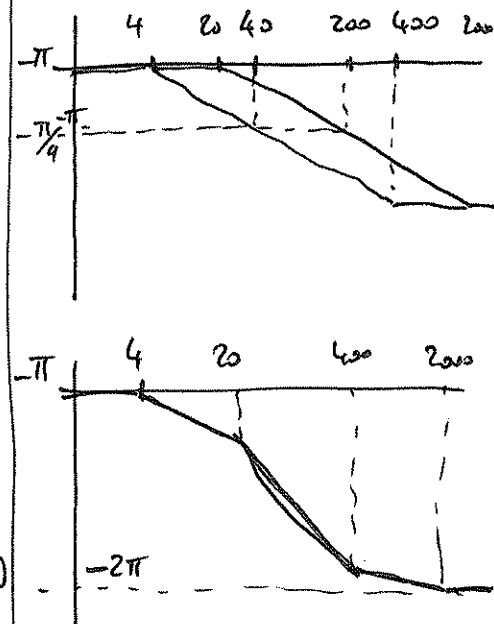
$$-\tan^{-1}\left(\frac{\omega}{200}\right)$$



Bode Diagrams with complex poles and zeros

$$T(s) = \frac{\omega_0^2}{(s^2 + 2\zeta\omega_0 s + \omega_0^2)} \Rightarrow \frac{1}{(1 - (\omega/\omega_0)^2) + j2\zeta(\omega/\omega_0)} = T(j\omega)$$

$$|T(j\omega)| = \frac{1}{\sqrt{(1 - (\omega/\omega_0)^2)^2 + 4\zeta^2(\omega/\omega_0)^2}}$$

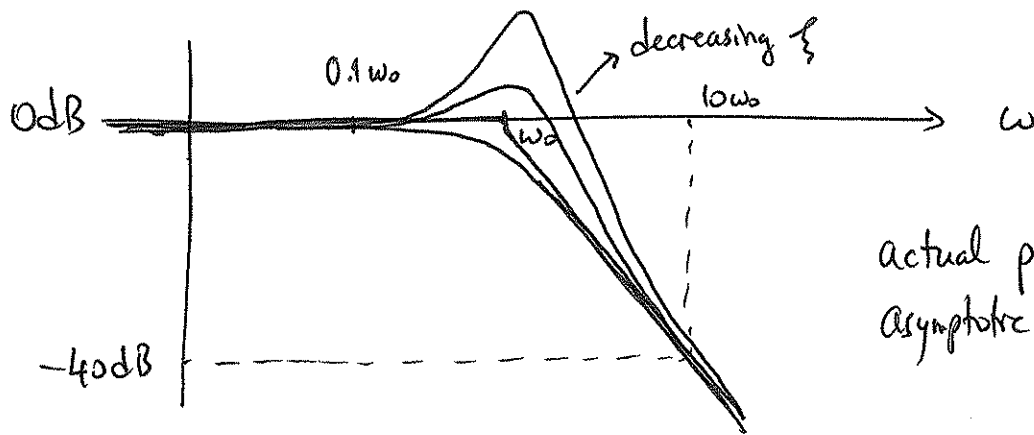

actual plot is below the asymptotic plot if $\zeta > 0.7/\sqrt{2}$


$$|T(j\omega)| = \frac{1}{\sqrt{1 + (\omega/\omega_0)^4}} \quad \text{if } \zeta = \frac{1}{\sqrt{2}}$$

$$\text{at } \omega = \omega_0 \quad |T(j\omega)| = \frac{1}{\sqrt{2}} \equiv -3 \text{ dB} \quad \text{if } \zeta = \frac{1}{\sqrt{2}}$$

$$|T(j\omega)| \geq \begin{cases} \frac{1}{\sqrt{1 + (\omega/\omega_0)^4}} & \text{if } \zeta < \frac{1}{\sqrt{2}} \\ \frac{1}{\sqrt{2}} & \text{if } \zeta = \frac{1}{\sqrt{2}} \\ \frac{1}{\sqrt{1 + (\omega/\omega_0)^4}} & \text{if } \zeta > \frac{1}{\sqrt{2}} \end{cases}$$

$$\text{When } \zeta = 0 \quad |T(j\omega)| = \frac{1}{|1 - (\omega/\omega_0)^2|}$$
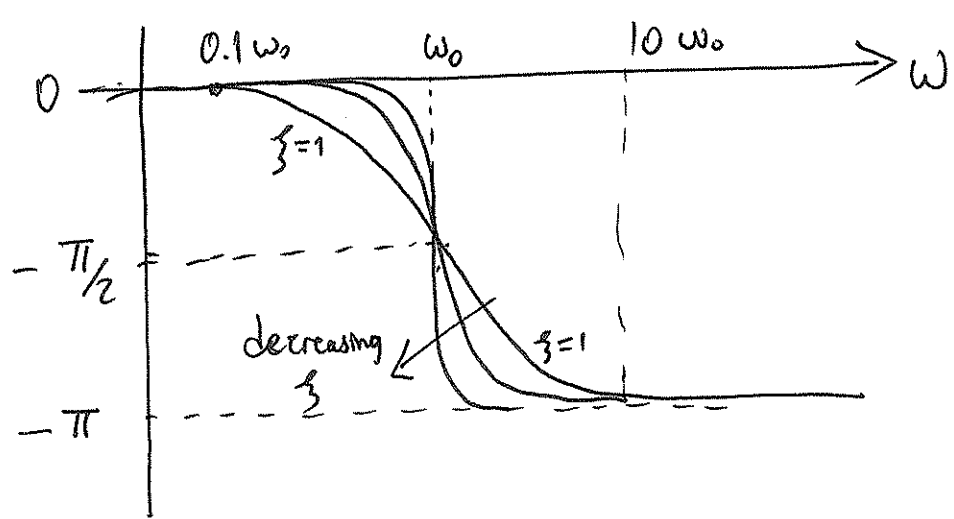
$$\angle T(j\omega) = -\tan^{-1}\left(\frac{2\zeta(\omega/\omega_0)}{1-(\omega/\omega_0)^2}\right)$$



Maximum gain is attained at $\omega_m = \omega_0 \sqrt{1-2\zeta^2}$ (for $\zeta < \frac{1}{\sqrt{2}}$)

$$\omega_m = \omega_0 \sqrt{1-2\zeta^2}$$

$$|T(j\omega_m)| = \frac{1}{2\zeta \sqrt{1-\zeta^2}}$$

exercise :
verify this