Circuit Theory

Basic Circuit Analysis

• Skip to Sec. 2.2 \rightarrow Connection Constraints \rightarrow KCL, KCVL

• Kirchhoff's Current Law (KCL) based on Nodes

• Kirchhoff's Current Law : Algebraic sum of currents entering any node is zero.

• Some books use **leaving** convention. Its essentially the same.

• Physical Reason : conservation of charge. \rightarrow rate of change of total charge at any node is zero \rightarrow KCL

- Example on p. 21-22, Fig. 2-11
- **A:** $-i_1 i_2 = 0$, **B:** $i_1 i_3 i_4 + i_5 = 0$, **C:** $i_2 + i_3 + i_4 i_5 = 0$,

• Linear dependence : A set of equations are linearly dependent if a linear combination of them is exactly zero. \rightarrow some equations can be derived from the others, hence unnecessary.

• Example : L1 : $x_1 + x_2 = 1$, L2 : $2x_1 + 2x_2 = 2 \rightarrow 2L1$ - L2 = $0 \rightarrow$ L1 and L2 are linearly dependent. \rightarrow One equation is redundant.

- In the above example, we have $\mathbf{A} + \mathbf{B} + \mathbf{C} = 0$.
- Conclusion : All node equations are linearly dependent

• Question : Assume that there are n nodes. How many node KCL equations are linearly independent ?

• Any n-1 of KCL node equations are **linearly independent**.

• Exercise 2.1 on p. 23, Fig. 2-12

• A: $-i_1 - i_2 = 0$, B: $i_2 - i_3 - i_4 = 0$, C: $i_4 - i_5 - i_6 = 0$, D: $i_1 + i_3 + i_5 + i_6 = 0$

• Check that $\mathbf{A} + \mathbf{B} + \mathbf{C} + \mathbf{D} = 0$.

• Given $i_1 = -1 \ mA$, $i_3 = 0.5 \ mA$, $i_6 = 0.2 \ mA \rightarrow i_2 = 1 \ mA$ (from **A**), $i_4 = 0.5 \ mA$ (from **B**), $i_5 = 0.3 \ mA$ (from **C**).

• An alternative view of KCL : Take any spherical volume, place it inside the circuit. Algebraic sum of currents **entering** to the volume is zero.

• Physical Reason : conservation of charge in any volume.

• Place the volume around any node \rightarrow KCL node equation.

• Matrix Formulation : KCL equations can be written in matrix form as Ai = 0. Here, A is called **incidence** matrix, i is a vector containing all currents.

•
$$\begin{pmatrix} -1 & -1 & 0 & 0 & 0 \\ 1 & 0 & -1 & -1 & 1 \\ 0 & 1 & 1 & 1 & -1 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{pmatrix} = 0$$

• Due to redundancy, we may delete any row of matrix A.

• Kirchhoff's Voltage Law (KVL) based on Loops

• Loop : A closed path formed by tracing through an ordered sequence of nodes without passing any node more than once.

• Closed path : starts and end at the same node.

• Closed node sequence : Same as loop, without the "passing any node more than once" requirement \rightarrow actually union of loops.

• Kirchhoff's Voltage Law : Algebraic sum of voltages around any loop (or any closed node sequence) is zero.

• Physical Reason : Due to conservative field, the potential difference between point A nd A is zero...The work done by moving a unit charge from point A to A is zero...

• Let $A - B - C - \dots - A$ be the nodes in the loop.... $w_{A-A} = 0 \rightarrow w_{A-A} = w_{A-B} + w_{B-C} + \dots \rightarrow dw_{A-A}/dq = 0 \rightarrow dw_{A-B}/dq + dw_{B-C}/dq + \dots = 0 \rightarrow w_{A-B} + v_{B-C} + \dots = 0$

• Example on p. 24, Fig. 2-13

• Loop 1 : $-v_1 + v_2 + v_3 = 0$, Loop 2 : $-v_3 + v_4 + v_5 = 0$, Loop 3 : $-v_1 + v_2 + v_4 + v_5 = 0$

- Example 2-5 on p. 24, Fig. 2-13
- $v_1 = 5 V, v_2 = -3 V, v_4 = 10 V \rightarrow$
- Loop $1 \rightarrow v_3 = 8 V$, Loop $2 \rightarrow v_5 = -2 V$.

• Question : Do we need all of these loop equations ? \rightarrow Are they linearly independent?

• Loop 1 + Loop 2 - Loop 3 = 0.

• All loop equations are linearly dependent. \rightarrow How many loop equations do we need ?

• b: number of two terminal elements, n: number of nodes \rightarrow There are b - n + 1 linearly independent loop equations... \rightarrow Meshes

• Matrix Formulation : KVL equations can be written in matrix form as Bv = 0. Here, B is called **loop** matrix, v is a vector containing all voltages.

•
$$\begin{pmatrix} -1 & 1 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 1 \\ -1 & 1 & 0 & 1 & 1 \end{pmatrix} \begin{pmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{pmatrix} = 0$$

• Skip to Sec. $2.1 \rightarrow$ Element Constraints

• Element constraints are algebraic or differential relations between terminal voltage(s) and current(s) of the device in question.

• **Resistors :** Defined by an **algebraic** relation between terminal v and *i*.

• Linear Resistor :algebraic relation is linear $\rightarrow av + bi = 0$



• $a \neq 0 \rightarrow v = Ri \rightarrow R$: Resistance \rightarrow unit : Ohm $\Omega \rightarrow$ Ohm = V/A.

• $b \neq 0 \rightarrow i = Gi \rightarrow G$: Conductance \rightarrow unit : Siemens S \rightarrow Siemens = A/V.

- if $G \neq 0 \rightarrow R = 1/G$, if $R \neq 0 \rightarrow G = 1/R$,
- $a = 0, b \neq 0 \rightarrow i = 0$ (v is arbitrary) \rightarrow **Open Circuit**.
- $a \neq 0, b = 0 \rightarrow v = 0$ (*i* is arbitrary) \rightarrow Short Circuit.
- Ideal Switch A switch which changes between open and short circuits...

• **Practical Switch** has a small resistance when short and large resistance when open...

•
$$R_S = \begin{cases} R_s & \text{short} \\ R_o & \text{open} \end{cases}$$



• Ideal Sources : Generates power for the circuit...



• Ideal Current Sources : i = I (DC source), or $i = i_s(t)$ (a given time function).

• Ideal Voltage Sources : v = E (DC source), or $v = v_s(t)$ (a given time function).

• Practical Current Sources : An ideal current source parallel to a linear resistor $i = v/R_p + i_s$

• Practical Voltage Sources : An ideal voltage source series to a linear resistor $v = R_s i + v_s$

• Skip to Sec. $2.3 \rightarrow$ Combined Constraints

 \bullet When we write KCL + KVL + Element constraints \rightarrow Combined constraints.

• Assume that we have n nodes and b elements. Each element has its v and i as unknowns $\rightarrow 2b$ unknowns. Need that many linearly independent equations.

• How many equations do we have ?

- KCL equations $\rightarrow n-1$
- KVL equations $\rightarrow b n + 1$
- Element Constraints : b
- Total Equations : 2b.

• If all of these equations are linearly independent \rightarrow circuit has a unique solution.

• Example 2.8 on p. 29-30, Fig. 2-21

- unknowns $\rightarrow v_A$, $i_A, v_1, i_1, v_2, i_2 \rightarrow 6$.
- KCL equations $\rightarrow \mathbf{A} : -i_A i_1 = 0, \mathbf{B} : i_1 i_2 = 0$
- KVL equations \rightarrow Loop 1 $-v_A + v_1 + v_2 = 0$
- Element Constraints : **D1** : $v_A = V_0$, **D2** : $v_1 = R_1 i_1$, **D3** : $v_2 = R_2 i_2$,

- $V_0 = 10 V, R_1 = 2 K\Omega, R_2 = 3 K\Omega$
- KCL equations $\rightarrow -i_A = i_1 = i_2 = i$
- KVL + Element Constraints \rightarrow
- $V_0 = (R_1 + R_2)i \rightarrow i = V_0/(R_1 + R_2) = 2 \ mA$
- Can find the rest of the variables by using i.

• Tableau Equations

- Write KCL+ KVL + Element Constraints in **matrix** form...
- $\operatorname{KCL} \to Ai = 0$

•
$$\operatorname{KVL} \to Bv = 0$$

• Element Constraints $\rightarrow Mv + Ni = u \rightarrow M$ and N depends on resistors, u depends on sources.

•
$$\begin{pmatrix} B & 0 \\ 0 & A \\ M & N \end{pmatrix}$$
 $\begin{pmatrix} v \\ i \end{pmatrix} = \begin{pmatrix} 0 \\ 0 \\ u \end{pmatrix}$ $\rightarrow Tx = u_s$

• If T is invertible $\rightarrow x = T^{-1}u_s$.

• If T is not invertible \rightarrow circuit either has no solution, or have infinitely many solutions...

• Sec. $2.4 \rightarrow$ Equivalent circuits

• Two circuits are said to be equivalent if they have identical i - v relation between a specified pair of terminals.

• **Result** : The electrical behaviour inside the **rest of the circuit** will not change if we replace two identical circuits connected to it.

• Equivalent Resistance : Series Combination : (Fig. 2.25 and Fig 2.35).

- KCL : $i = i_1 = i_2 = i_3$, KVL : $v = v_1 + v_2 + v_3$,
- Elements : $v_j = R_j i_j, \ j = 1, 2, 3$
- $\rightarrow v = (R_1 + R_2 + R_3)i \rightarrow v = R_{eq}i, \quad R_{eq} = R_1 + R_2 + R_3$

• Equivalent Resistance : Parallel Combination : (Fig. 2.26 and Fig. 2.41).

- KCL : $i = i_1 + i_2 + i_3$, KVL : $v = v_1 = v_2 = v_3$,
- Elements : $v_j = R_j i_j$, $\rightarrow i_j = G_j v_j$ j = 1, 2, 3
- $\rightarrow i = (G_1 + G_2 + G_3)v \rightarrow i = G_{eq}V, \quad G_{eq} = G_1 + G_2 + G_3$
- $\rightarrow \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$

•
$$j = 2 \rightarrow \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \rightarrow R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$
 (Fig. 2.26)

- Voltage Sources in series : (Fig. 2.34)
- KCL : $i = i_1 = i_2$, KVL : $v = v_1 + v_2$, Elements : $v_1 = V_1$, $v_2 = V_2$

$$\bullet \to v = V_{eq} = V_1 + V_2$$

- Current Sources in parallel : (Fig. 2.34)
- KCL : $i = i_1 + i_2$, KVL : $v = v_1 = v_2$, Elements : $i_1 = I_1$, $i_2 = I_2$
- $\bullet \to i = I_{eq} = I_1 + I_2$
- Equivalence of practical sources : (Fig. 2.29)

 - Practical Current Source :
 $i=v/R_p+i_s,$ Practical Voltage Source :
 $v=R_si+v_s$

- Equivalence when $R_p = R_s$, $v_s = -R_p i_s$
- $\bullet \rightarrow {\bf The venin-Norton \ equivalent \ circuits}$
- A Voltage source parallel to a resistor case : (Fig. 2.32)
- $v = v_s \rightarrow \text{Resistance can be omitted }!$
- A Current source series to a resistor case : (Fig. 2.33)

- $i = i_s \rightarrow \text{Resistance can be omitted }!$
- Sec. $2.5 \rightarrow$ Voltage and Current Division :
- Voltage Division : (Fig. 2.35)
- $\rightarrow v = R_{eq}i, \quad R_{eq} = R_1 + R_2 + R_3, \quad i = i_1 = i_2 = i_3, \quad v_j = R_j i_j$
- $\rightarrow v_j = \frac{R_j}{R_1 + R_2 + R_3} v$ (Note that $v = v_s$).
- Current Division : (Fig. 2.41)
- $\rightarrow i = G_{eq}v, \quad G_{eq} = G_1 + G_2 + G_3, \quad i = i_1 + i_2 + i_3, \quad i_j = G_jv_j$

•
$$\rightarrow i_j = \frac{G_j}{G_1 + G_2 + G_3} i$$
 (Note that $i = i_s$).

- \rightarrow For 2 resistors \rightarrow , $i_1 = \frac{G_1}{G_1 + G_2} i = \frac{R_2}{R_1 + R_2} i$ (Fig. 2.42)
- \rightarrow For 2 resistors \rightarrow , $i_2 = \frac{G_2}{G_1 + G_2}i = \frac{R_1}{R_1 + R_2}i$
- Sec. $2.6 \rightarrow$ Circuit Reduction

• Sometimes, by replacing certain parts of a given circuits by their equivalent circuits, by using series/parallel combinations, we may simplify a given circuit. This is called circuit reduction technique. Works in some simple circuits, and some parts of complicated circuits, but may not be applicable to some complex circuits. Typical application \rightarrow ladder circuits, see Fig. 2.48.

• Example 2.22, p. 49-50

• Note that not all resistors are linear. A typical example is a diode, which is a nonlinear resistor. $(i = I_s(e^{v/v_T} - 1))$. This model can be simplified (piecewise linear-switch)

• A resistor is called **passive** if we have $p = vi \ge 0$ for all possible cases. Otherwise, it is called **active**.

• A resistor is called **time varying**, if its i - v behaviour changes with time.

• A resistor is called **bilateral**, if nothing changes when we replace the terminal connections \rightarrow its i - v relation is symmetric with respect to the origin.