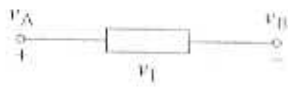


Case A



Case B

FIGURE 3-2 Two possible connections of a two-terminal element.

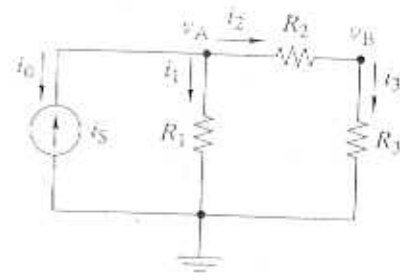


FIGURE 3-4 Circuit for demonstrating node-voltage analysis.

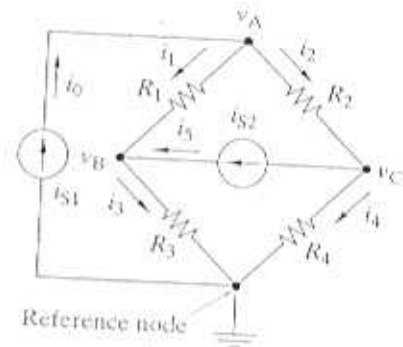


FIGURE 3-5

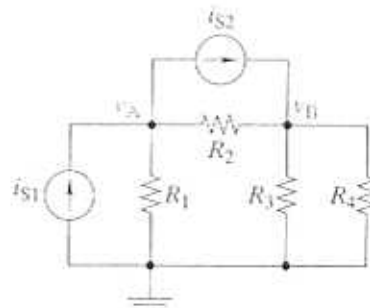


FIGURE 3-6 Circuit for demonstrating writing node-voltage equations by inspection.

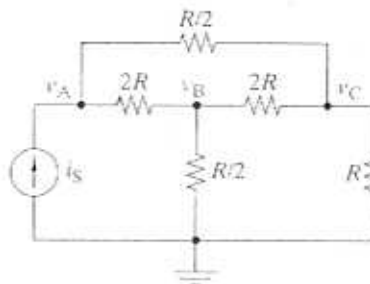


FIGURE 3-7


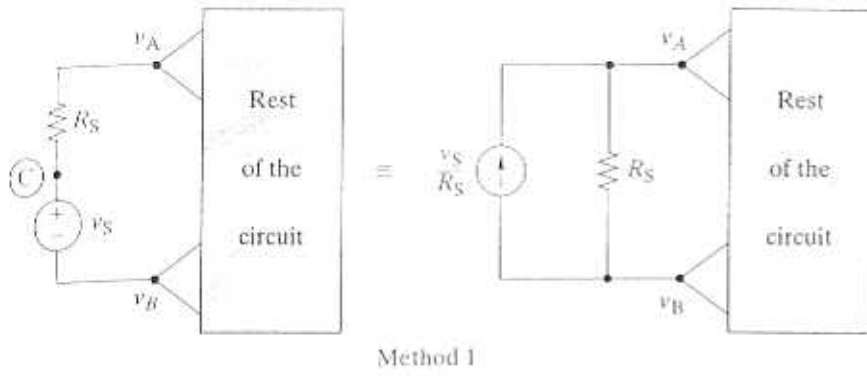
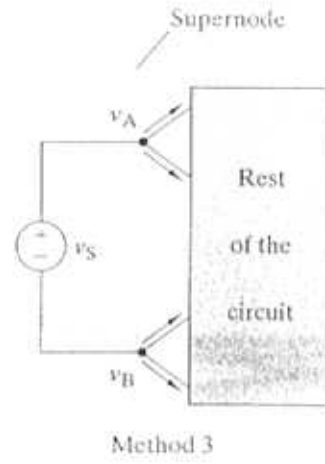



FIGURE 3-11 Three methods of treating voltage sources in node analysis.

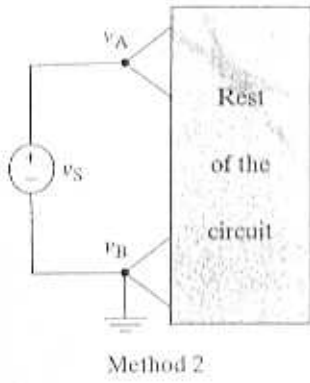

EXAMPLE 3-4

Use node-voltage analysis to find v_O in the circuit in Figure 3-12(a).



FIGURE 3-12

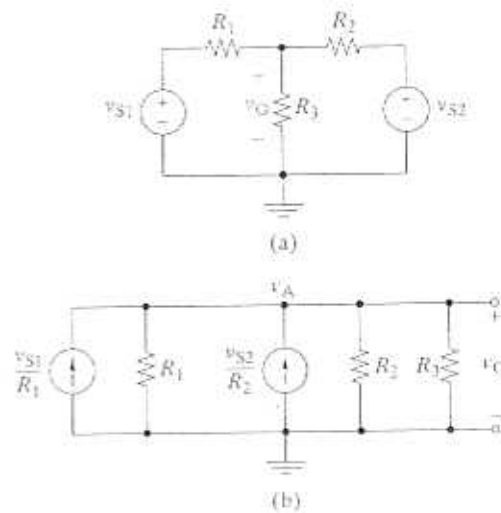

EXAMPLE 3-5

Find the input resistance of the circuit in Figure 3-13.

FIGURE 3-13

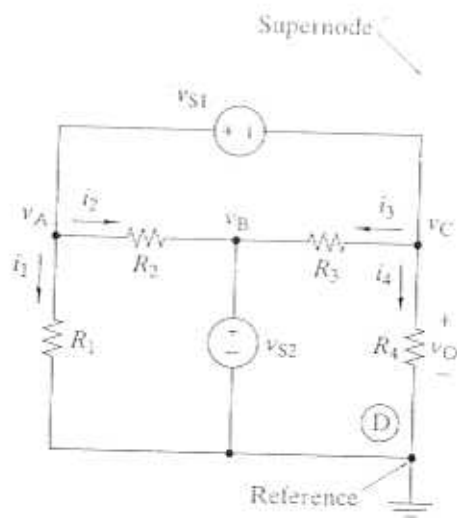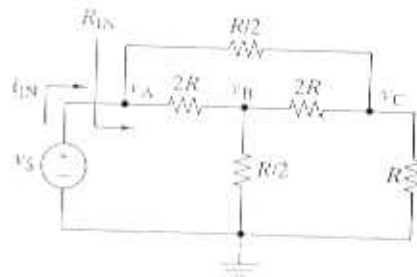

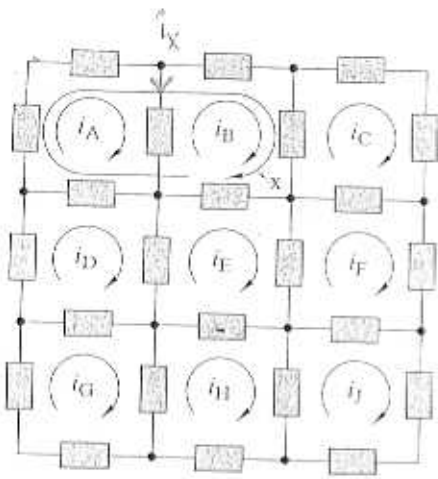


FIGURE 3-16 Meshes in a planar circuit.

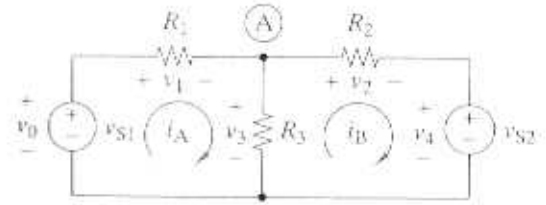


FIGURE 3-18 Circuit for demonstrating mesh-current analysis.

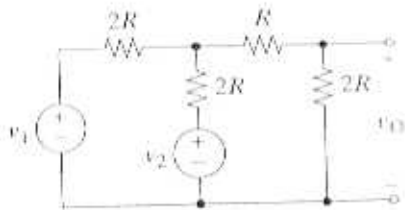


FIGURE 3-24

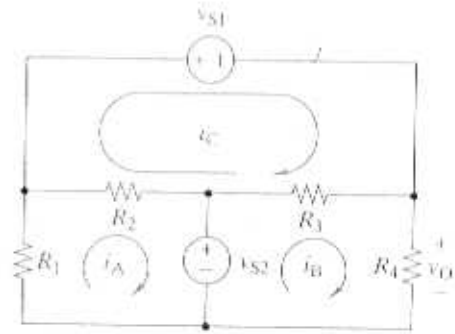


FIGURE 3-19



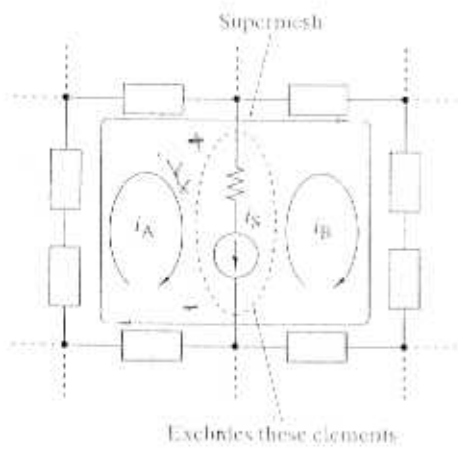


FIGURE 3-20 Example of a supermesh.

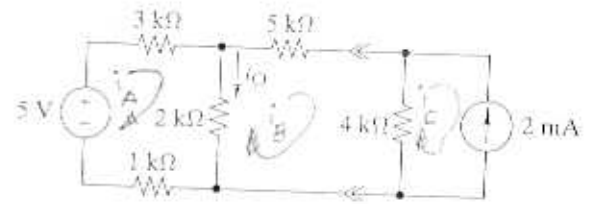

(a)

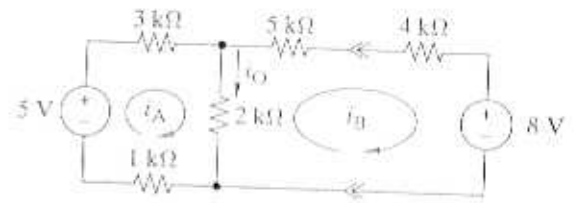

(b)

FIGURE 3-21

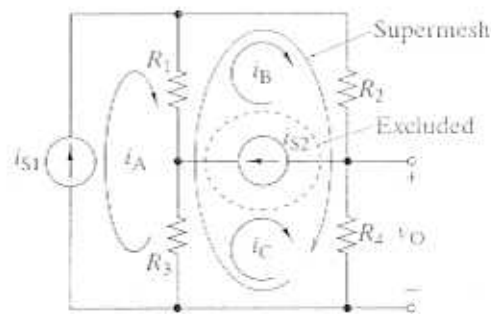


FIGURE 3-22

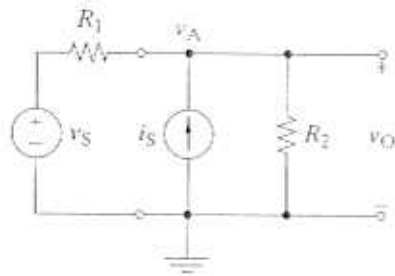


FIGURE 3-31 Circuit used to demonstrate superposition.

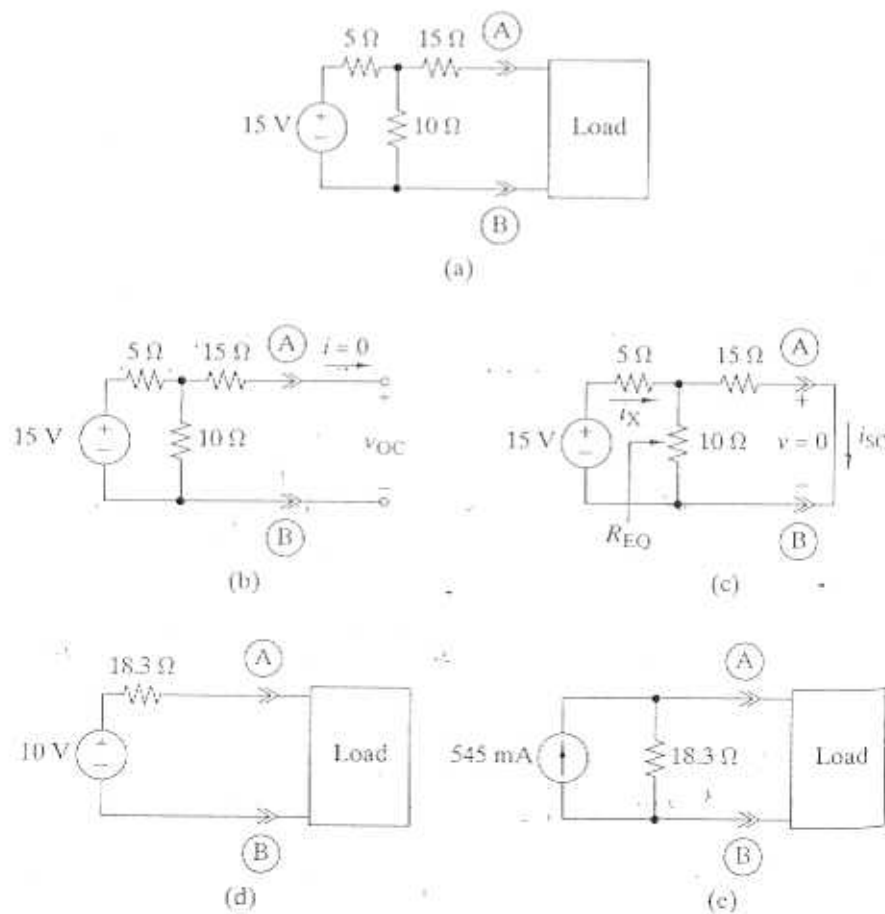


FIGURE 3-39 Example of finding the Thévenin and Norton equivalents of circuits: (a) The given circuit. (b) Open circuit yields the Thévenin voltage. (c) Short circuit yields the Norton current. (d) Thévenin equivalent circuit. (e) Norton equivalent circuit.

