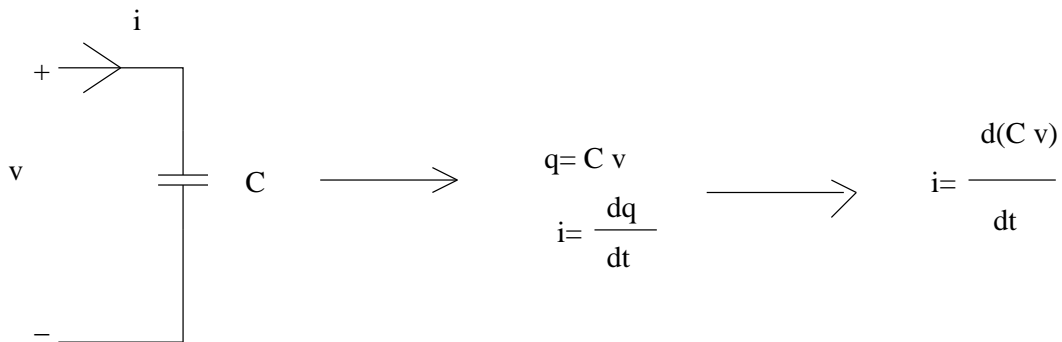


Circuit Theory

Chapter 6 : Capacitors and Inductors


- Linear capacitor



- If C is time-invariant (i.e. a **constant**) $\Rightarrow i = C \frac{dv}{dt}$

The unit of C : Capacitance $\Rightarrow [C] = \frac{As}{V} = \frac{s}{\Omega} = F$ (Farad).

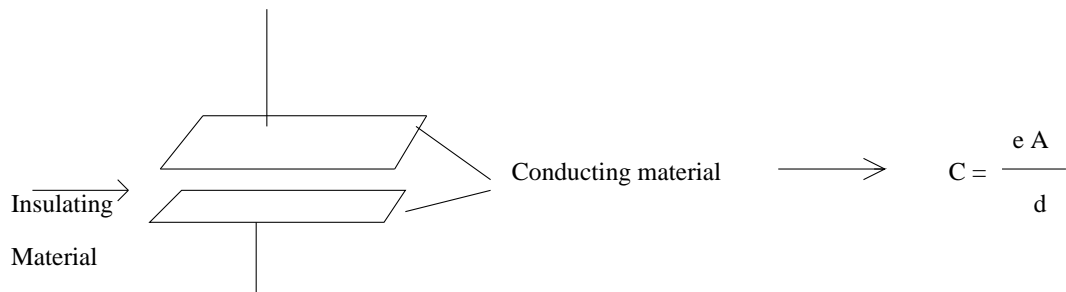- Typical example : parallel conducting plates separated by insulating material



- Here A is the area, d is the distance between plates, and ϵ is the dielectric constant of the insulating material.

- $i = C \frac{dv}{dt} \Rightarrow \frac{dv}{dt} = \frac{i}{C} \Rightarrow \int_{t_0}^{t_1} \dot{v}(\tau) d\tau = \frac{1}{C} \int_{t_0}^{t_1} i(\tau) d\tau \Rightarrow \dot{v} = \frac{d}{dt}$

- $v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^{t_1} i(\tau) d\tau$

- **Result 1 :** If $i(\cdot)$ is bounded on an interval, then $v(\cdot)$ is continuous...

- $v(t+\Delta t) = v(t) + \frac{1}{C} \int_t^{t+\Delta t} i(\tau) d\tau \Rightarrow v(t+\Delta t) - v(t) = \frac{1}{C} \int_t^{t+\Delta t} i(\tau) d\tau$

- $|i(\tau)| < M \Rightarrow |v(t+\Delta t) - v(t)| \leq \frac{1}{C} \int_t^{t+\Delta t} M d\tau = \frac{M}{C} \Delta t$

- $\lim_{\Delta t \rightarrow 0} v(t+\Delta t) = v(t) \Rightarrow v(\cdot)$ is **continuous**.

- **Result 2 :** If $i(t) = 0$ on $[t_0, t_1] \Rightarrow v(t) = v(t_0) = \text{constant}$ on $[t_0, t_1]$.

- **Result 3 :** If $v(t) = v(t_0) = \text{constant}$ on $[t_0, t_1] \Rightarrow i(t) = 0$ on $[t_0, t_1]$ (**open circuit**)

- **Power and Energy**

- Here we assume that C is constant.

- $p(t) = v(t)i(t) = v(t)C \frac{dv}{dt} \Rightarrow p(t) = \frac{d}{dt} \left(\frac{1}{2} C v^2(t) \right)$

- Since $p(t) = \frac{d}{dt} (\text{Energy}) \Rightarrow E(t) = \frac{1}{2} C v^2(t)$


- Analogous with kinetic energy of a particle mass m with velocity v .

- $W(t_0, t_1) = \text{Total power received by the element in the interval } [t_0, t_1]$

- $W(t_0, t_1) = \int_{t_0}^{t_1} p(t) dt$

- For a resistor : $W(t_0, t_1) = \int_{t_0}^{t_1} p(t)dt = R \int_{t_0}^{t_1} i^2(t)dt > 0$
- For a capacitor : $W(t_0, t_1) = \int_{t_0}^{t_1} p(t)dt = \frac{1}{2} C v^2(t_1) - \frac{1}{2} C v^2(t_0) = E(t_1) - E(t_0)$
- Hence, if $v(t_1) = v(t_0) \Rightarrow W(t_0, t_1) = 0$
- Assume that the capacitor operates under the periodic regime
- $\Rightarrow i(t + T) = i(t) \forall t \Rightarrow v(t + T) = v(t) \forall t$
- $\Rightarrow W(t_0, t_0 + T) = 0 !$
- Under the periodic regime, within periods, capacitor does not receive total power
- \Rightarrow **Lossless device**
- Half of the period receives energy, the next half it gives it back.
- As a result, there is always a **phase difference** between v and i .

- Linear Inductor

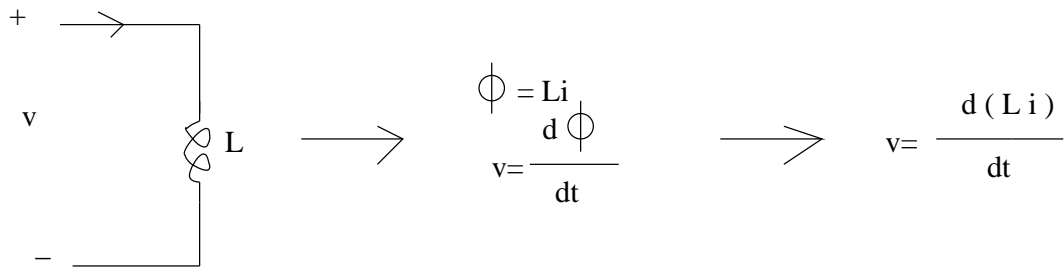

- If L is time-invariant (i.e. a **constant**) $\Rightarrow v = L \frac{di}{dt}$


The unit of L : Inductance $\Rightarrow [L] = \frac{Vs}{A} = \Omega s = H$ (Henry).

- Typical example : Toroidal Inductance

- Here, $L = \mu \frac{N^2 A}{l}$

- μ : Magnetic permeability, A : Cross-sectional area

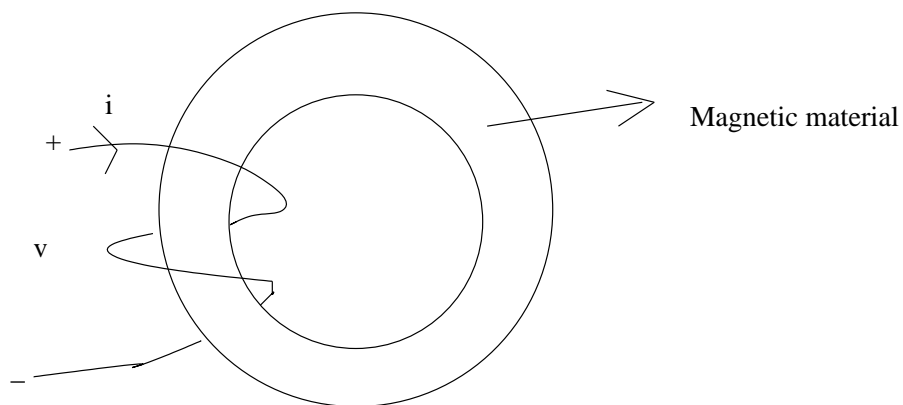- N : Number of turns, l : mid circumference



- $v = L \frac{di}{dt} \Rightarrow \frac{di}{dt} = \frac{v}{L} \Rightarrow \int_{t_0}^{t_1} i(\tau) d\tau = \frac{1}{L} \int_{t_0}^{t_1} v(\tau) d\tau \Rightarrow \dot{() = \frac{d}{dt}}$

- $i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^{t_1} v(\tau) d\tau$

- **Result 1 :** If $v(\cdot)$ is bounded on an interval, then $i(\cdot)$ is continuous...

- $i(t + \Delta t) = i(t) + \frac{1}{L} \int_t^{t+\Delta t} v(\tau) d\tau \Rightarrow i(t + \Delta t) - i(t) = \frac{1}{L} \int_t^{t+\Delta t} v(\tau) d\tau$

- $|v(\tau)| < M \Rightarrow |i(t + \Delta t) - i(t)| \leq \frac{1}{L} \int_t^{t+\Delta t} M d\tau = \frac{M}{L} \Delta t$

- $\lim_{\Delta t \rightarrow 0} i(t + \Delta t) = i(t) \Rightarrow i(\cdot) \text{ is } \mathbf{continuous}.$

- **Result 2 :** If $v(t) = 0$ on $[t_0, t_1] \Rightarrow i(t) = i(t_0) = \mathbf{constant}$ on $[t_0, t_1]$.

- **Result 3 :** If $i(t) = i(t_0) = \mathbf{constant}$ on $[t_0, t_1] \Rightarrow v(t) = 0$ on $[t_0, t_1]$ (**short circuit**)

- **Power and Energy**

- Here we assume that L is constant.

- $p(t) = v(t)i(t) = i(t)L \frac{di}{dt} \Rightarrow p(t) = \frac{d}{dt} \left(\frac{1}{2} L i^2(t) \right)$

- Since $p(t) = \frac{d}{dt} (\text{Energy}) \Rightarrow E(t) = \frac{1}{2} L i^2(t)$

- Analogous with kinetic energy of a particle mass m with velocity v .

- $W(t_0, t_1) = \text{Total power received by the element in the interval } [t_0, t_1]$

- $W(t_0, t_1) = \int_{t_0}^{t_1} p(t) dt$

- For an inductor : $W(t_0, t_1) = \int_{t_0}^{t_1} p(t) dt = \frac{1}{2} Li^2(t_1) - \frac{1}{2} Li^2(t_0) = E(t_1) - E(t_0)$

- Hence, if $i(t_1) = i(t_0) \Rightarrow W(t_0, t_1) = 0$

- Assume that the inductor operates under the periodic regime

- $\Rightarrow v(t + T) = v(t) \forall t \Rightarrow i(t + T) = i(t) \forall t$

- $\Rightarrow W(t_0, t_0 + T) = 0 !$


- Under the periodic regime, within periods, inductor does not receive total power

- \Rightarrow **Lossless device**

- Half of the period receives energy, the next half it gives it back.

- As a result, there is always a **phase difference** between v and i .

- **Parallel Connection of Capacitors**

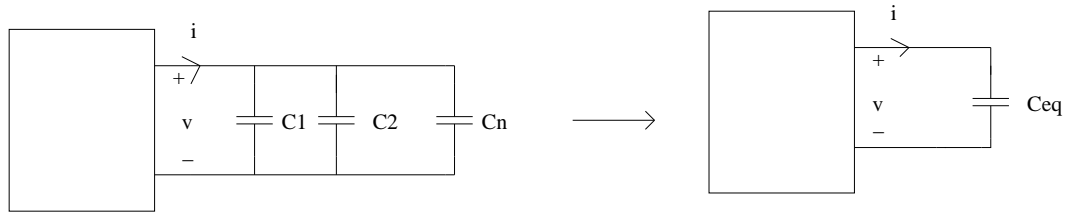


- KVL : $v_1 = v_2 = \dots = v_n = v$, KCL : $i = i_1 + i_2 + \dots + i_n$

- $i = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + \dots + C_n \frac{dv}{dt} = (C_1 + C_2 + \dots + C_n) \frac{dv}{dt}$

- $\Rightarrow C_{eq} = C_1 + C_2 + \dots + C_n$

- **Series Connection of Capacitors**

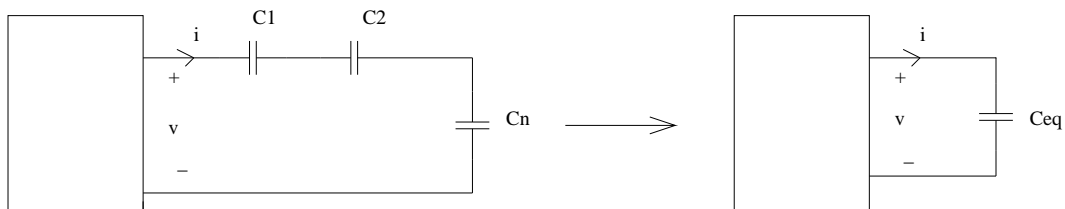


- KCL : $i_1 = i_2 = \dots = i_n = i$, KVL : $v = v_1 + v_2 + \dots + v_n$

- $v(t) = v_1(t_0) + \frac{1}{C_1} \int_{t_0}^{t_1} i(\tau) d\tau + v_2(t_0) + \frac{1}{C_2} \int_{t_0}^{t_1} i(\tau) d\tau + \dots + v_n(t_0) + \frac{1}{C_n} \int_{t_0}^{t_1} i(\tau) d\tau = (v_1(t_0) + v_2(t_0) + \dots + v_n(t_0)) + (\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}) \int_{t_0}^{t_1} i(\tau) d\tau$

- $v(t) = v(t_0) + (\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}) \int_{t_0}^{t_1} i(\tau) d\tau$

- $\frac{1}{C_{eq}} = (\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n})$

- **Series Connection of Inductors**

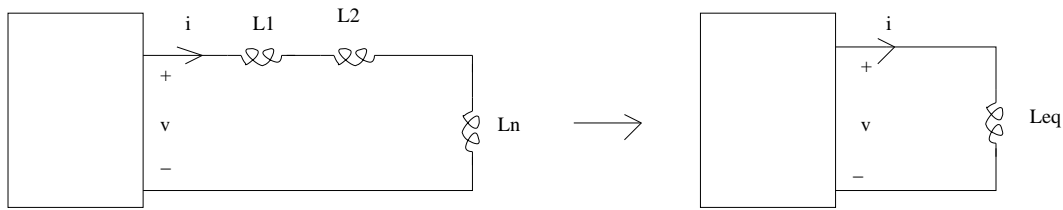


- KCL : $i_1 = i_2 = \dots = i_n = i$, KVL : $v = v_1 + v_2 + \dots + v_n$

- $v = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + \dots + L_n \frac{di}{dt} = (L_1 + L_2 + \dots + L_n) \frac{di}{dt}$

- $\Rightarrow L_{eq} = L_1 + L_2 + \dots + L_n$

- **Parallel Connection of Inductors**

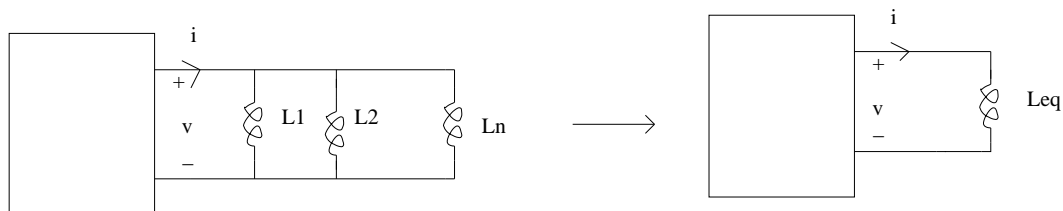


- KVL : $v_1 = v_2 = \dots = v_n = v$, KCL : $i = i_1 + i_2 + \dots + i_n$

- $i(t) = i_1(t_0) + \frac{1}{L_1} \int_{t_0}^{t_1} v(\tau) d\tau + i_2(t_0) + \frac{1}{L_2} \int_{t_0}^{t_1} v(\tau) d\tau + \dots + i_n(t_0) + \frac{1}{L_n} \int_{t_0}^{t_1} v(\tau) d\tau$
 $= (i_1(t_0) + i_2(t_0) + \dots + i_n(t_0)) + \left(\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n} \right) \int_{t_0}^{t_1} v(\tau) d\tau$

- $i(t) = i(t_0) + \left(\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n} \right) \int_{t_0}^{t_1} v(\tau) d\tau$


- $\frac{1}{L_{eq}} = \left(\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n} \right)$

- Op-amp Integrator

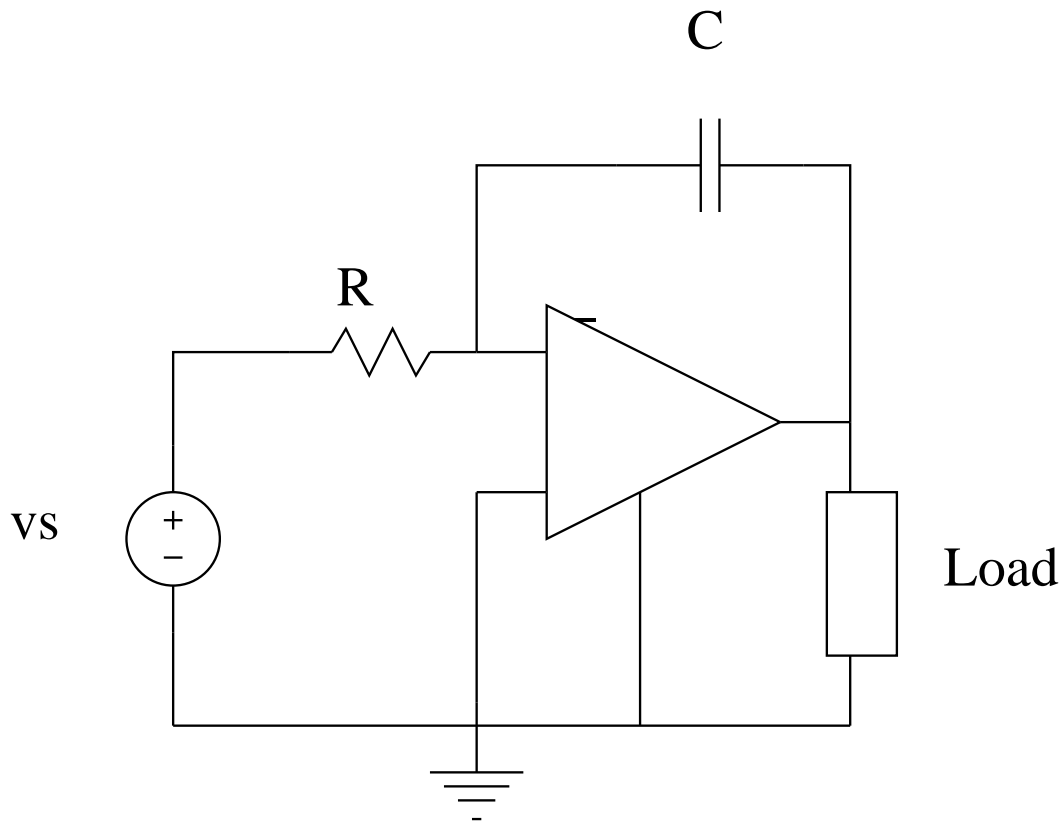

- $v_- = v_+ = 0 \rightarrow v_s = Ri_R$, $v_C = -v_0$
- $i_- = 0 \rightarrow i_R = i_C \rightarrow \frac{v_s}{R} = -C \frac{dv_0}{dt}$
- $\frac{dv_0}{dt} = -\frac{v_s}{RC}$
- $v_0(t) = v_0(t_0) - \frac{1}{RC} \int_{t_0}^t v_s(\tau) d\tau$
- Output is the integral of the input.

- Op-amp Differentiator

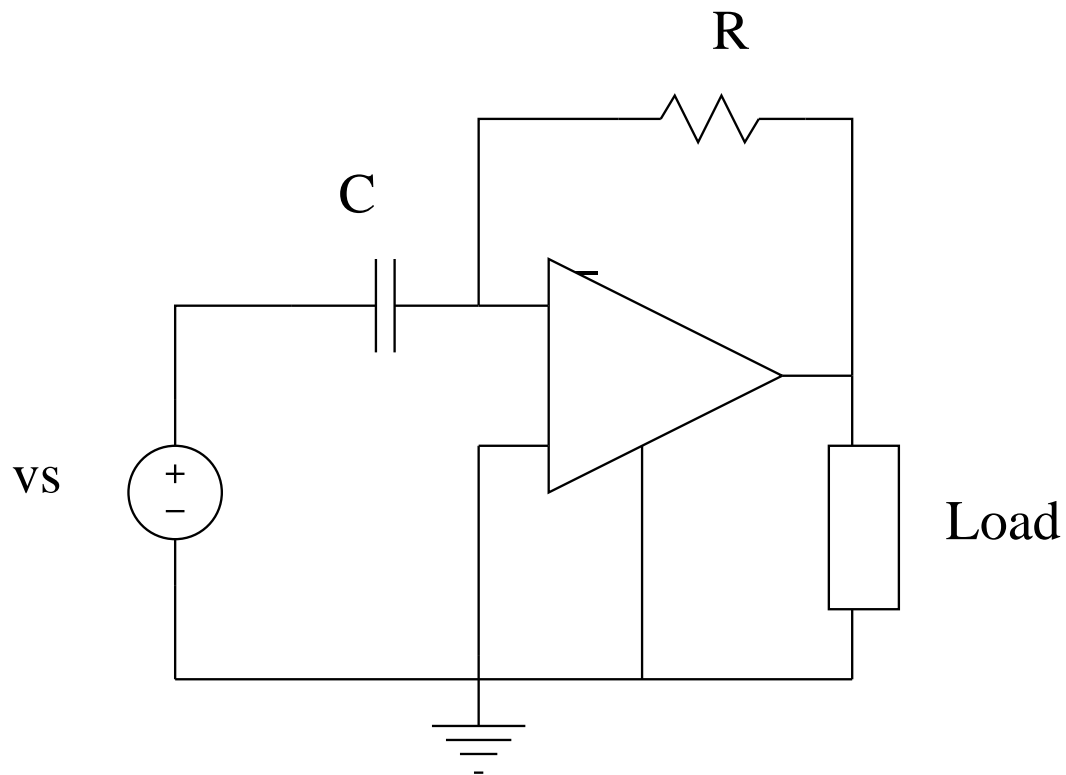

- $v_- = v_+ = 0 \rightarrow i_C = C \frac{dv_s}{dt} , v_R = -v_0$

- $i_C = i_R = - \frac{v_0}{R}$

- $v_0 = -RC \frac{dv_s}{dt}$

- Output is the differential of the input.