

EEE 314 LAB #4 MANUAL

The aim of this lab is to familiarize ourselves with the fundamental working mechanisms of MOS structures. The objective is to be able to extract the MOS parameters after certain measurements and also to examine the transition times for CMOS inverters.

PRELAB

Part1

NMOS	PMOS
$V_{thn} = 0.7V$	$V_{thp} = -0.8V$
$k_n = 0.6mA/V^2$	$k_p = 0.5mA/V^2$
$\gamma_n = 0.5 V^{1/2}$	$\gamma_p = 0.2 V^{1/2}$
$\lambda_n = 0.1 V^{-1}$	$\lambda_p = 0.2 V^{-1}$

Table 1 MOS parameters for Part1

* You may take $2\Phi_{Fn}=2\Phi_{Fp}=0.6$ Volts

a) Use the parameters given in Table 1 as inputs for a MATLAB program that plots I_{ds} as a function of V_{gs} for circuits given in Figure 1. $|V_{gs}|$ might vary in between 0 and 1.5 Volts. Attach your code. Your graphs will look like the following (Figure2). Be careful with the signs and clearly indicate the NMOS and PMOS plots. Make all necessary assumptions. Ignore the voltage drop over the resistance (RD) at the drain sides.

b) Using the given parameters above, write a MATLAB program to plot I_{ds} vs V_{ds} for the circuits given in Figure3. $V_{applied}$ might vary in between 0 and $V_{dd} = 5$ Volts. On the same figure plot for different V_{gs} voltages. $|V_{gs}|$ might take values in between 1Volt up to 3Volts. Do not forget to handle the body effect. For another $|V_{sb}|$ you may choose, comment about the influence of the body effect on I_{ds} vs V_{ds} curves. Attach your code. Your graphs will look like the following (Figure4), clearly indicate each V_{gs} voltage that you have used. Make all necessary assumptions. Ignore the voltage drop over the resistance (RD) at the drain sides. You may artificially add the effect of channel length modulation in linear region as well to avoid the discontinuity at the transition.

Part2

a) The student has an NMOS device. He builds the same circuit given in Figure3 (circuit for the NMOS transistor) to estimate the channel length modulation (λ_n) of his NMOS transistor. He assures that his transistor is in saturation ($V_{sb}=0.5$ Volts, and $V_{gs}=2$ Volts) and measures the following values for V_{ds} vs I_d (Table 2). Extract the channel length modulation.

b) Now, he builds the same circuit given in Figure1 (circuit for the NMOS transistor) to estimate the threshold voltage (V_{th}) and K_n . For the same circuit ($R_D = 50$ Ohms, $V_{dd} = 5$ Volts), he measures I_{ds} for different values of V_{gs} and notes them down (Table 3). Using the measured values in Table3, extract V_{th} and K_n for this transistor. Make all necessary assumptions.

c) Now the student knows V_{th} , K_n and λ_n . The only parameter left is the body effect. In order to find it, he builds the same circuit shown Figure 3 but now with $V_{sb}=2.5$ Volts, and $V_{gs}=2$ Volts, for the NMOS transistor and measures I_{ds} vs V_{ds} (Table 4). Extract the body effect (γ_n). You may take $2\Phi_{Fn}=2\Phi_{Fp}=0.6$ Volts.

Experiment

In this experiment, we are not going to extract the body effect, so you may use the transistors with $V_{sb}=0$ for IC 4007 configuration. Work in groups of 2 people. Every group is free to share the power supply voltages of their neighbors'.

- 1) Come up with an idea to roughly extract λ_n and λ_p of both NMOS and PMOS transistors using V_{ds} vs I_{ds} measurements. Clearly write down the value you have found.
- 2) Come up with an idea to roughly extract the V_{th} , K_n and K_p of both NMOS and PMOS transistors using V_{gs} vs I_{ds} measurements. Clearly write down the value you have found.
- 3) After having extracted all the parameters, use three different C_{load} values (560pF, 1.2nF, 10nF), measure the transition times for the inverter configuration in Figure 5. Definitions are given in Figure 6.

Ids, (mA)	Vds, (Volts)
0.4859	1.9757
0.4939	2.1753
0.5020	2.3749
0.5101	2.5745
0.5182	2.7741
0.5263	2.9737
0.5344	3.1733
0.5425	3.3729
0.5506	3.5725

Ids, (mA)	Vds, (Volts)
0.5587	3.7721
0.5668	3.9717
0.5749	4.1713
0.5830	4.3708
0.5911	4.5704
0.5992	4.7700
0.6073	4.9696

Table 2 NMOS Ids vs Vds measured values for Part2a

Ids, (mA)	Vgs, (Volts)
0	0
0	0.1
0	0.2
0	0.3
0	0.4
0	0.5
0	0.6
0	0.7
0.0045	0.8
0.0180	0.9
0.0405	1

Ids, (mA)	Vgs, (Volts)
0.0720	1.1
0.1125	1.2
0.1619	1.3
0.2203	1.4
0.2877	1.5
0.3641	1.6
0.4493	1.7
0.5435	1.8
0.6466	1.9
0.7586	2

Table 3 NMOS Ids vs Vgs measured values for Part2b

Ids, (mA)	Vds, (Volts)
0	0
0.1198	0.2940
0.1920	0.5904
0.2127	0.8894
0.2186	1.1891
0.2244	1.4888
0.2303	1.7885
0.2361	2.0882
0.2420	2.3879

Ids, (mA)	Vds, (Volts)
0.2479	2.6876
0.2537	2.9873
0.2596	3.2870
0.2654	3.5867
0.2713	3.8864
0.2771	4.1861
0.2830	4.4859

Table 4 NMOS Ids vs Vds measured values for Part2c

 


Figure 1 V_{gs} vs I_{ds} investigation for NMOS and PMOS

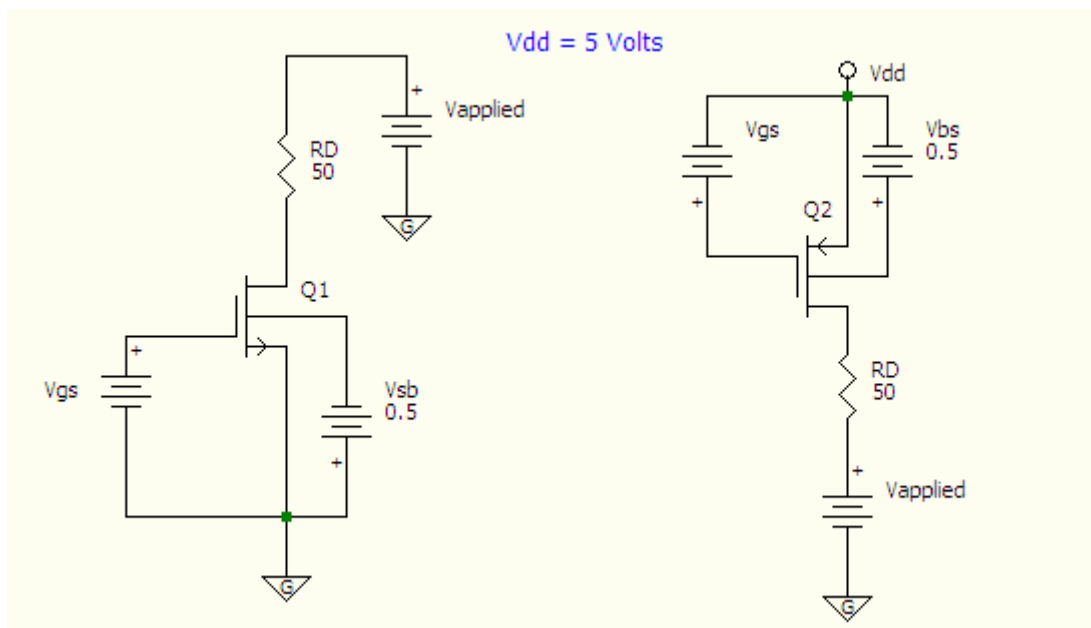


Figure 3 V_{ds} vs I_{ds} investigation for NMOS and PMOS

 


Figure2 An Exemplary V_{gs} vs I_{ds} curve

 


Figure4 An Exemplary V_{ds} vs I_{ds} curve

 


Figure 5 CMOS Inverter with loading capacitance

 


Figure 6 Transition Time Definitions

EE314 EXPERIMENT #4 DATASHEET

Date:

Name:

1)

λ_n (1/V)	λ_p (1/V)

2)

K_n (mA/V ²)	
K_p (mA/V ²)	
V_{thn} (V)	
V_{thp} (V)	

3)

Delay Times

t _{plh}	t _{phl}	t _r	T _f

Capacitance (nF)
0.56
1.2
10